
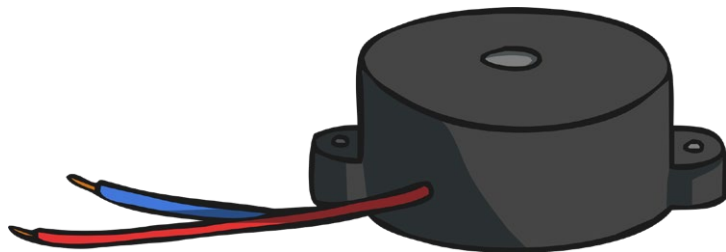



Electric Circuit

1

Can you make a complete circuit?

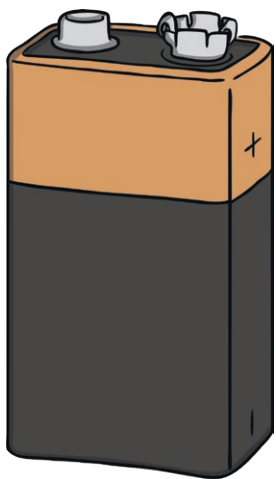



Use a battery pack
and a buzzer

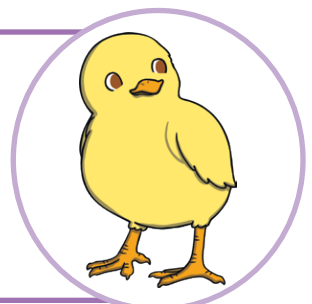


Electric Circuit

2

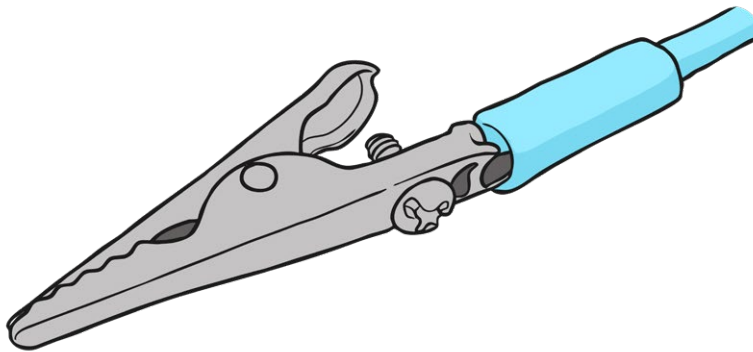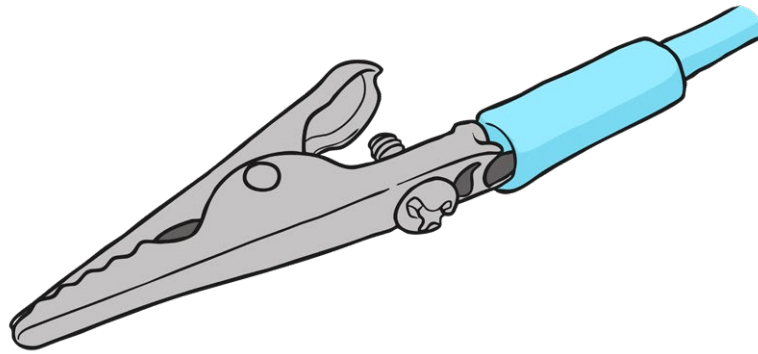Add 2 more crocodile clips to your circuit.



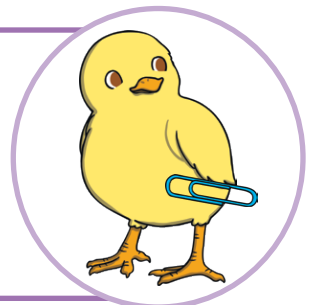
Add another object to the circuit so the buzzer will still make a noise.




Electric Circuit

3

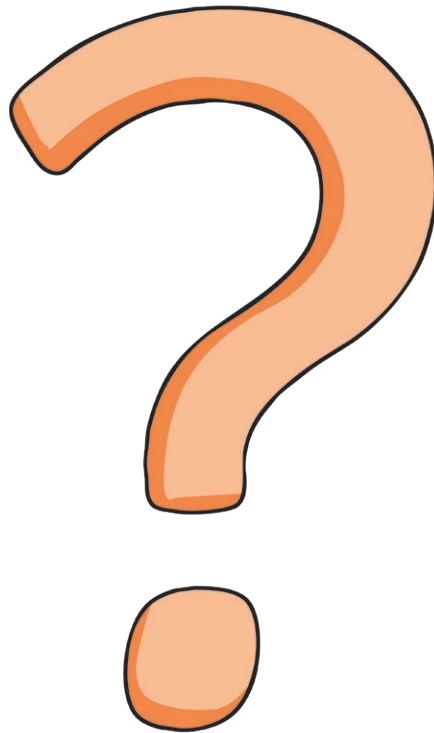What other objects could you use instead?






Try and find 4 more.

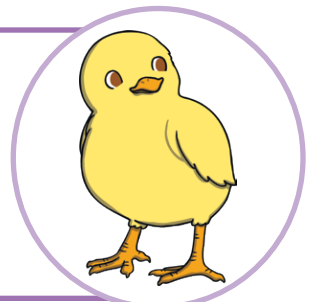


Electric Circuit

4

Use 3 buzzers this time.

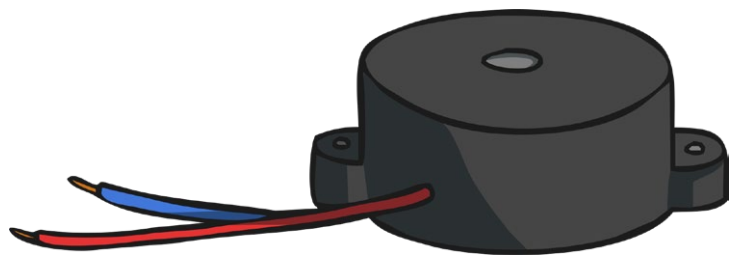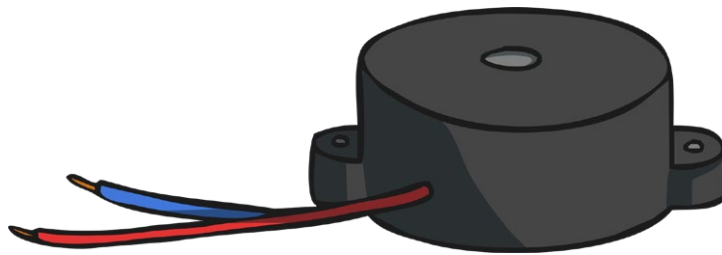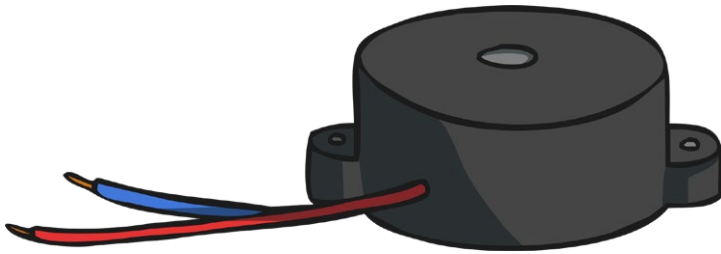


What happens?

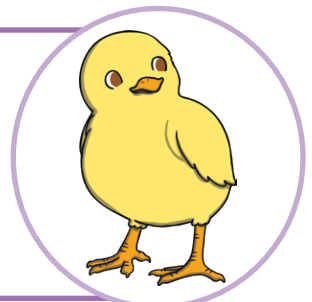

Electric Circuit

5

How could you make the sound louder?

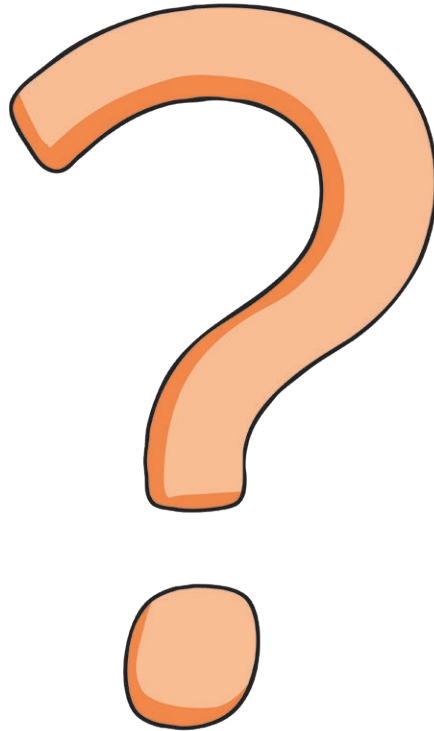

Think about the batteries!

