
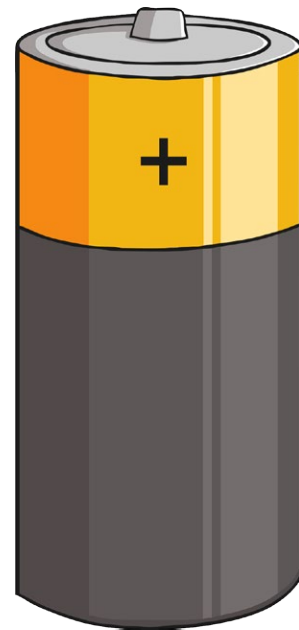


Electric Circuit

1

Can you make a complete circuit?

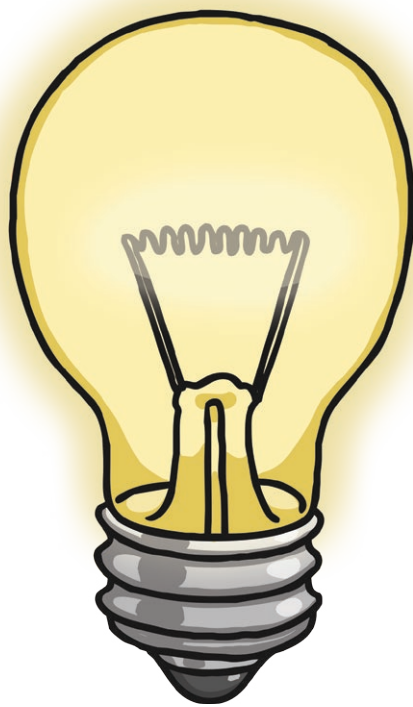


**Use a battery pack
and a lightbulb**

Electric Circuit

2

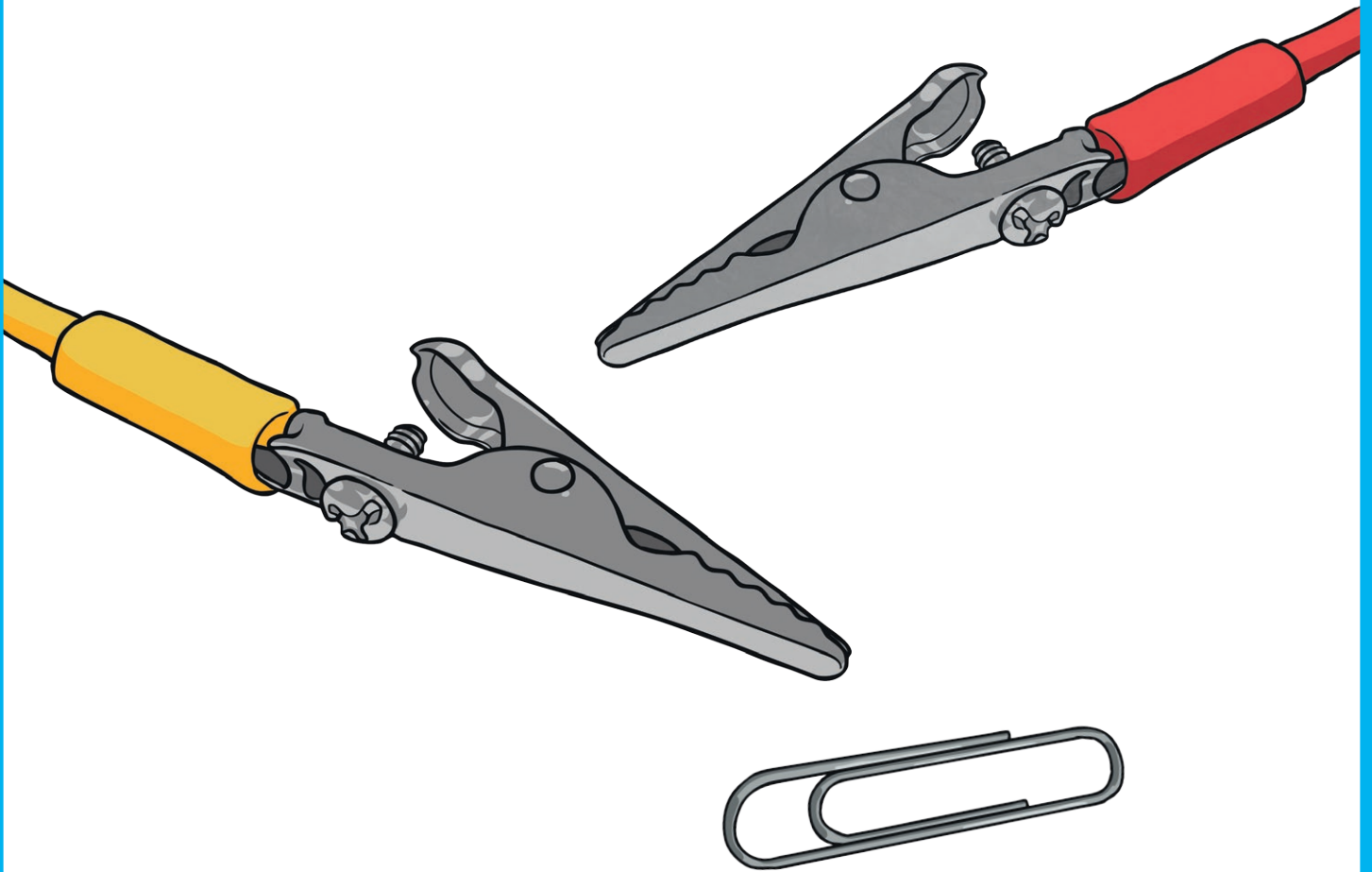Add two more crocodile clips to your circuit.




Add another object to the circuit so the lightbulb will still shine.

Electric Circuit

3

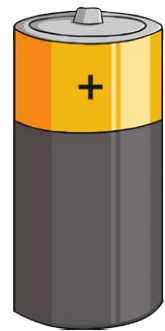What other objects could you use instead?




Try to find four more.

Electric Circuit

4

**Use three lightbulbs
this time!**

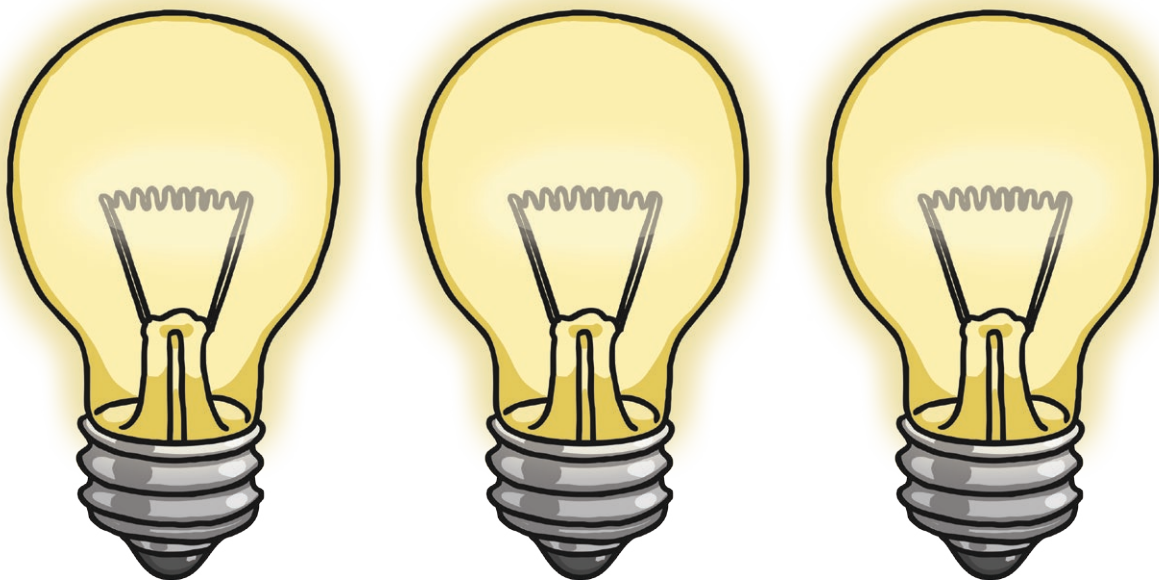


**What happens to the
brightness of the bulbs?**

Electric Circuit

5

How could you make the lights brighter?

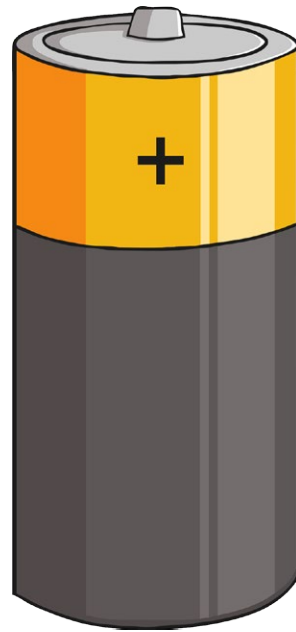

Think about the batteries!