

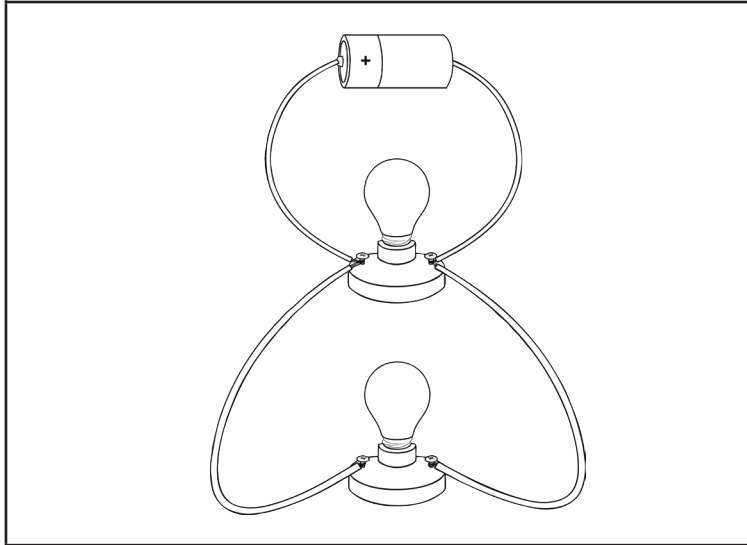


Circuits

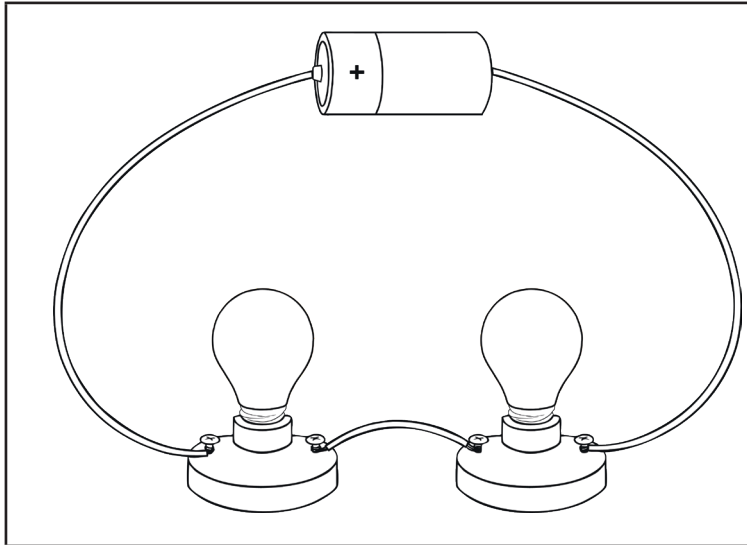
Make both of these circuits. Re-draw the series and parallel circuit using the symbols.




lamp

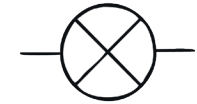



motor

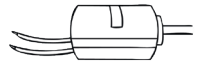

battery

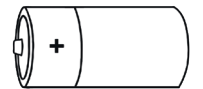

switch

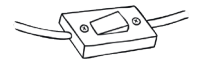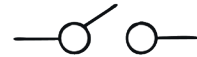

buzzer

