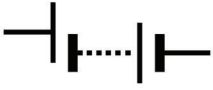












Electric Circuits

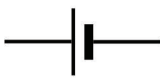






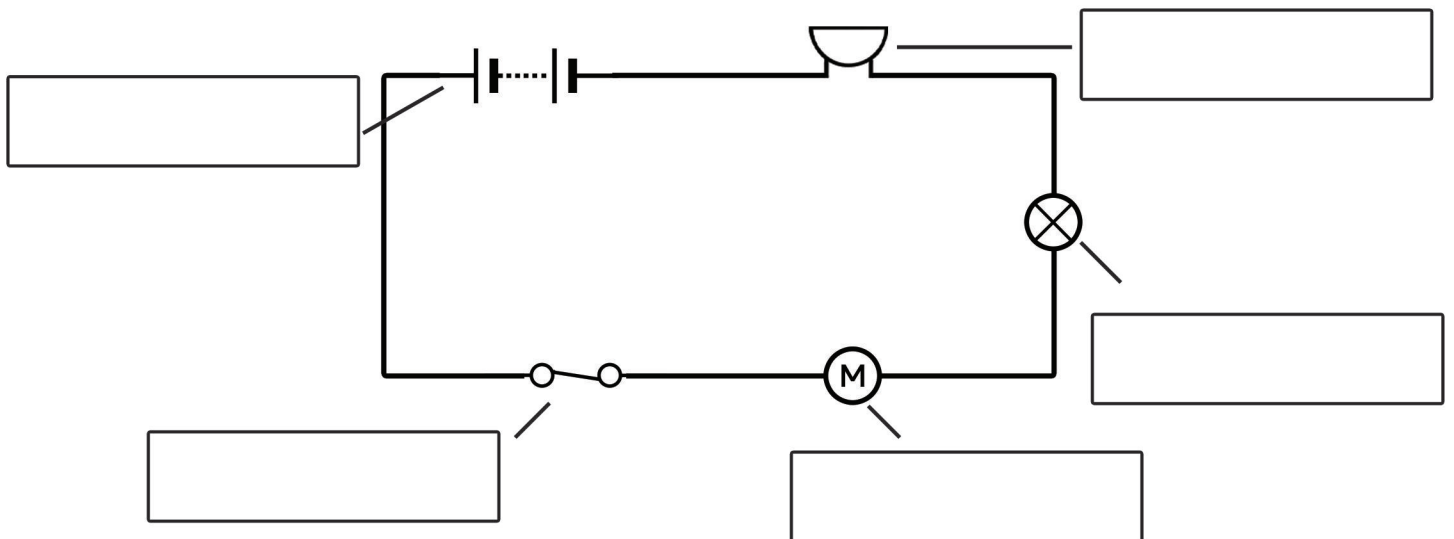


Label the circuit below.
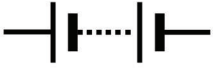
| | | | | |
|--|--|--|--|--|
|  battery |  closed switch |  open switch |  cell |  voltmeter |
|  buzzer |  lamp |  lamp |  motor |  wire |



Electric Circuits - Answers

Label the circuit below.

| | | | | |
|--|--|--|--|--|
|  battery |  closed switch |  open switch |  cell |  voltmeter |
|  buzzer |  lamp |  lamp |  motor |  wire |

