

**Circuits  
from the Lab<sup>®</sup>**  
Reference Designs

Circuits from the Lab<sup>®</sup> reference designs are engineered and tested for quick and easy system integration to help solve today's analog, mixed-signal, and RF design challenges. For more information and/or support, visit [www.analog.com/CN0518](http://www.analog.com/CN0518).

Devices Connected/Referenced	
HMC376	700 MHz to 1 GHz Low Noise Amplifier
ADG901	0 Hz to 4.5 GHz, 40 dB Off Isolation at 1 GHz, 17 dBm P1dB at 1 GHz SPST Switches
ADL5904	DC to 6 GHz, 45 dB TruPower Detector with Envelope Threshold Detection
LT8330	Low I <sub>Q</sub> Boost/SEPIC/Inverting Converter with 1 A, 60 V Switch
ADP150	Ultralow Noise, 150 mA CMOS Linear Regulator
ADM7150	800 mA, Ultra Low Noise/High PSRR LDO
ADM7170	6.5 V, 500 mA, Ultralow Noise, High PSRR, Fast Transient Response CMOS LDO
LTC6991	TimerBlox: Resettable, Low Frequency Oscillator

**USB-Powered, 915 MHz RF Low Noise Amplifier Receiver with Overpower Protection Circuit**

**EVALUATION AND DESIGN SUPPORT**

- ▶ Circuit Evaluation Boards
  - ▶ [CN0518 Circuit Evaluation Board \(EVAL-CN0518-EBZ\)](#)
- ▶ Design and Integration Files
  - ▶ [Schematics, Layout Files, Bill of Materials](#)

**CIRCUIT FUNCTIONS AND BENEFITS**

The International Telecommunication Union allocates the unlicensed 915 MHz, industrial, scientific and medical (ISM) radio frequency band for use in Region 2, geographically consisting of the Americas, Greenland, and some Eastern Pacific Islands. Advancements in wireless technologies and standards within the region have made the band popular for short range, wireless communication systems.

The 915 MHz ISM band places no restrictions on the application or duty cycle and common uses include amateur radio, supervisory

control and data acquisition (SCADA), and radio frequency identification (RFID) systems.

The circuit shown in Figure 1 is a two-stage RF low noise amplifier (LNA) optimized for receiver signal chains in the 915 MHz ISM band. At the center frequency, the circuit results in a forward gain (S<sub>21</sub>) of 25 dB and an input return loss (S<sub>11</sub>) of more than 10 dB. The RF input and output ports are designed with a 50 Ω impedance match, enabling a direct connection between the circuit and a standard 50 Ω system.

The board includes a high speed overpower cutoff that protects sensitive downstream equipment connected to the receiver system. The receiver system also automatically returns to normal operation when the RF power level drops within the acceptable range. The RF inputs and outputs are standard subminiature version A (SMA) connectors, and the entire design is powered by a single micro-USB connector.

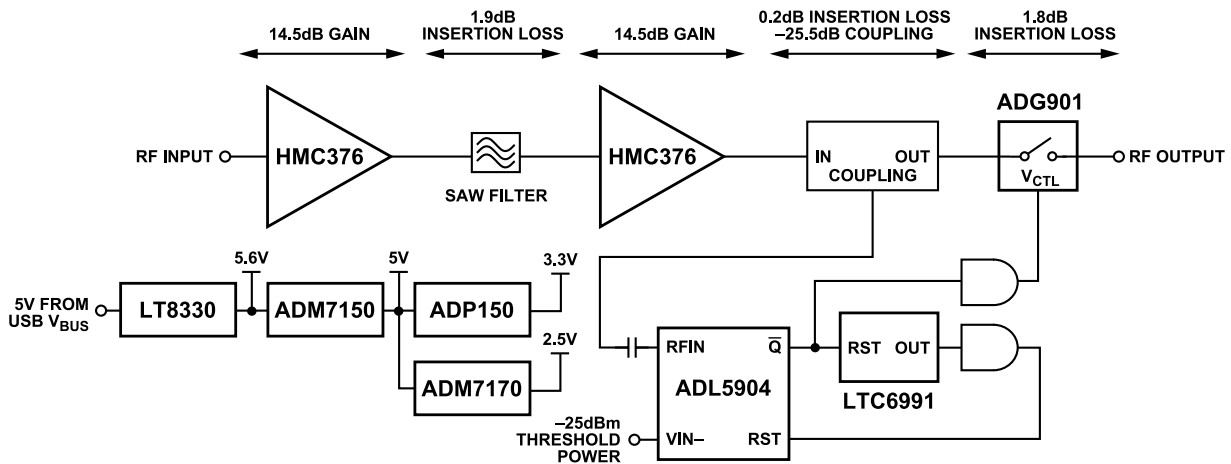


Figure 1. CN0518 Simplified Block Diagram

**CIRCUIT DESCRIPTION**

**RF LOW NOISE AMPLIFIER**

The CN0518 uses cascaded HMC376 low noise amplifiers for its RF signal path, achieving an overall gain of approximately 25 dB. The HMC376 is a gallium arsenide (GaAs), pseudomorphic high electron mobility transistor (pHEMT), high MMIC, low noise amplifier that operates from 700 MHz to 1000 MHz.

Figure 2 shows the typical S-Parameter performance, with a typical gain of 15 dB and return losses of more than 10 dB throughout the entire frequency range. The HMC376 has a typical noise figure of 0.7 dB, a 1 dB compression point (P1dB) of 21.5 dBm, and a third-order intercept point (OIP3) of 36 dBm.

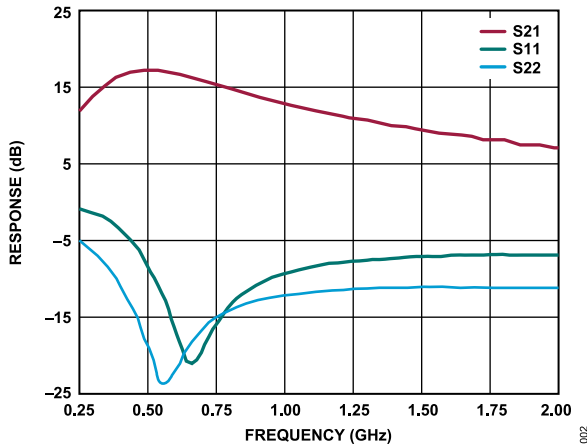


Figure 2. HMC376 Typical S-Parameters

**Impedance Matching Network**

The HMC376 RF input and output ports are internally matched for a single-ended 50 Ω impedance. This internally matched topology allows the HMC376 to be readily ported between any printed circuit board material regardless of its dielectric constant, thickness, or composition. The RFOUT also has an integrated DC-blocking capacitor that eliminates the need for an external capacitor. The only requirement needed is an inductor in parallel with the RF input with respect to the ground.

Figure 3 shows the basic configuration and implementation of two cascaded HMC376 amplifiers.

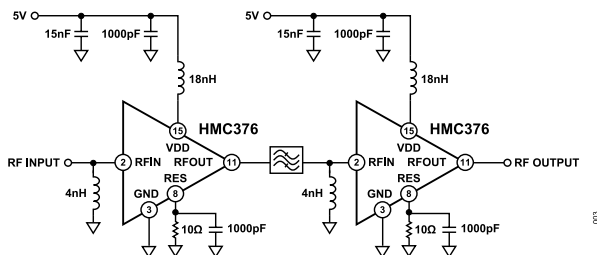


Figure 3. Basic Connections for Cascading HMC376 Amplifiers

**RF SAW FILTER**

The first stage amplifier output of the CN0518 is filtered by a surface wave acoustic (SAW) filter, which eliminates unwanted out-of-band amplification. When selecting a filter, a balance must be struck between the band flatness and the out-of-band rejection. SAW filters are also a source of insertion loss, which reduces the overall gain of the signal chain and needs to be considered during selection.

The filter used has a pass band of 902 MHz to 928 MHz, with a return loss of 21 dB and an insertion loss of 1.9 dB at 915 MHz center frequency.

**RF DIRECTIONAL COUPLER**

The CN0518 includes a multilayer RF directional coupler. This device has an operating frequency of 698 MHz to 2.62 GHz with a coupling factor of 25.5 at 915 MHz. It has an input and output port impedance of 50 Ω and a typical insertion loss of 0.2 dB.

**RF SWITCH**

The ADG901 is a wideband RF switch that uses a CMOS process to provide high isolation and low insertion loss. It is an absorptive (matched) switch with 50 Ω terminated shunt legs. The switch enables the user to pass DC signals up to 0.5 V without the use of a DC-blocking capacitor.

The ADG901 operates at DC up to 4.5 GHz at -3 dB frequency. At the 915 MHz center frequency, this device has a typical insertion loss of approximately 1.8 dB at "ON state" as shown in Figure 4, and a typical isolation loss of approximately 30 dB at "OFF state" as shown in Figure 5.

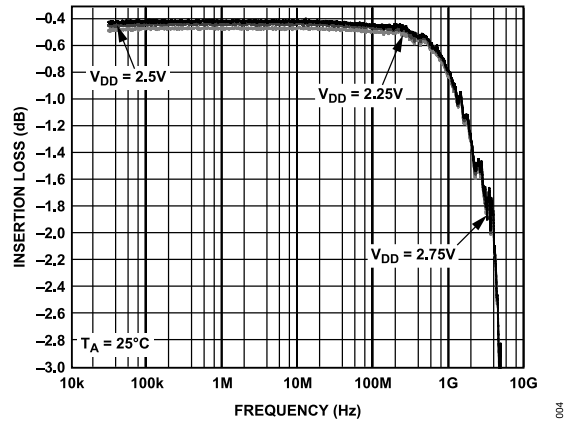


Figure 4. ADG901 Insertion Loss Performance at ON State

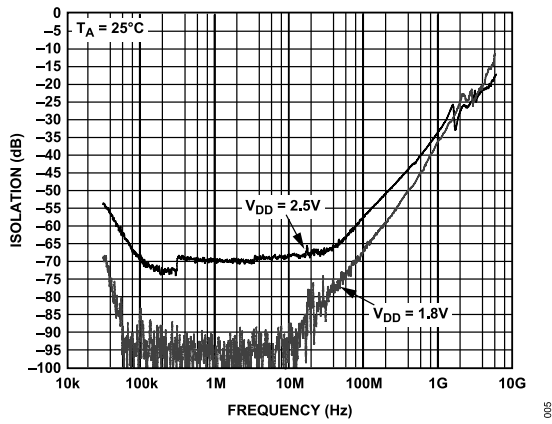


Figure 5. ADG901 Isolation Loss Performance at OFF State

Combining the insertion loss from the filter, coupler, and the RF switch results in a total insertion loss of approximately 3.9 dB at the output of the RF switch in normal operating conditions.

### RF PERFORMANCE

The resulting S-parameters, phase noise measurements, spurious-free dynamic range (SFDR), noise figure, and stability measure of the CN0518 are shown in the figures below.

At the center frequency of 915 MHz, the CN0518 achieves a gain of 25 dB with input and output return losses of greater than 10 dB. Figure 6 shows the S-Parameters across the operating frequency range.

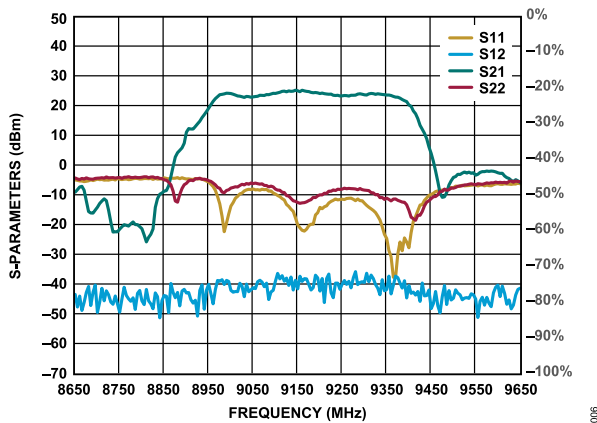


Figure 6. CN0518 S-Parameters vs. Frequency

Figure 7 shows the single sideband phase noise at 915 MHz, with approximately -91 dBc/Hz, -125 dBc/Hz, -129 dBc/Hz, and -142 dBc/Hz at frequency offsets of 10 Hz, 1 kHz, 100 kHz, and 1 MHz offset, respectively.

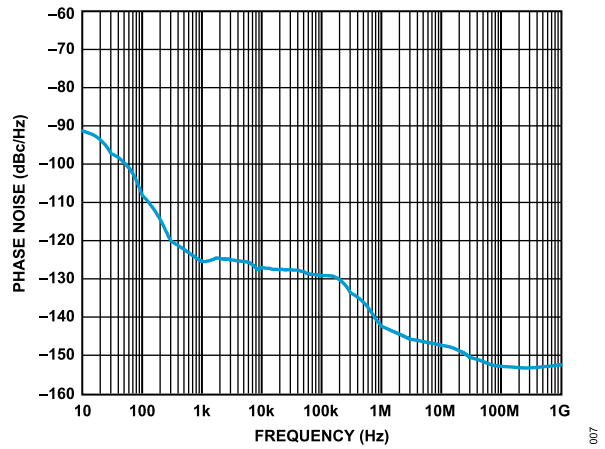


Figure 7. CN0518 Single Sideband Phase Noise at 915 MHz

Figure 8 shows the narrow-band single-tone RF output with an SFDR of 76 dBFS.

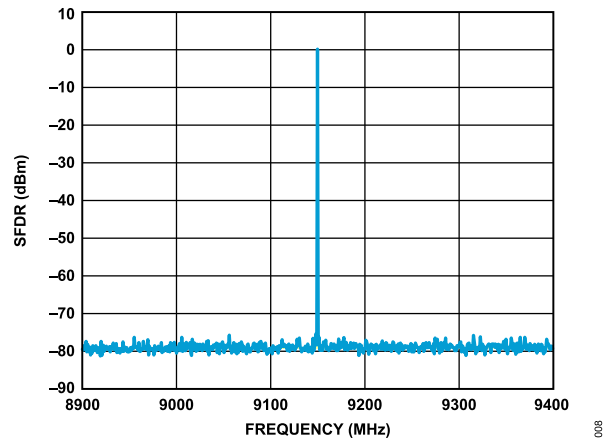


Figure 8. CN0518 Narrow-Band Single Tone RF Output

Figure 9 shows the corresponding noise figure of approximately 0.8 dB over the entire frequency range.

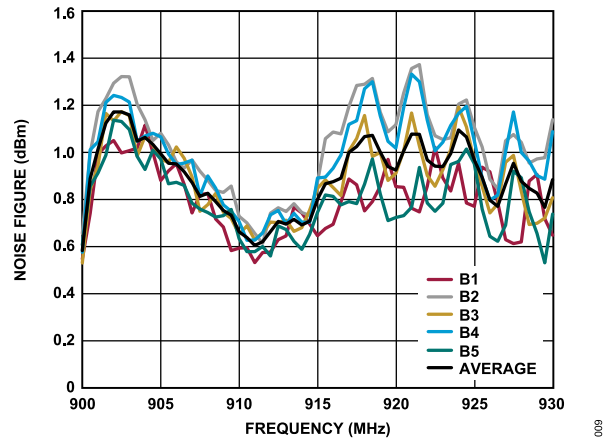


Figure 9. CN0518 Noise Figure vs. Frequency

The system is stable across the entire 915 MHz ISM frequency bandwidth with the Rollet's stability factor ( $k$ ) being above 1 and the

supplementary stability measure (B1) being above 0, as shown in Figure 10. This makes the CN0518 unconditionally stable for any source and load impedance combination.

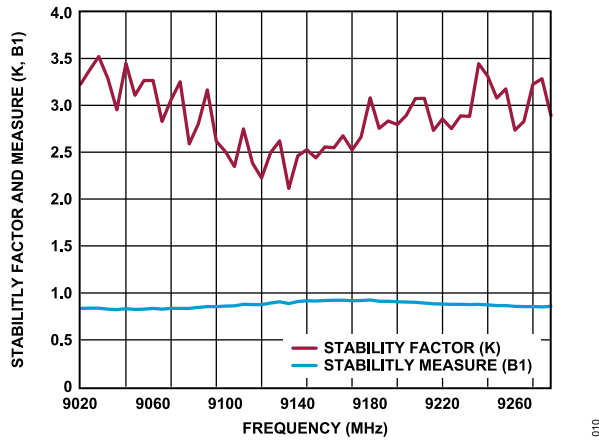


Figure 10. CN0518 Stability Factor and Measure vs. Frequency

### OVERPOWER PROTECTION

An overpower management feature is implemented in CN0518 wherein the RF path of the board is automatically isolated when the output power reaches the preset threshold. This feature is performed using an ADL5904 RF power detector.

The ADL5904 provides a resistor-programmable detection threshold, which compares the voltage from an internal envelope detector with a user-defined input voltage. When the voltage from the envelope detector exceeds the user-defined threshold voltage at the  $V_{IN-}$  pin, an internal comparator captures and latches the event to a set/reset (SR) flip-flop. Figure 11 shows the overpower protection circuitry for the CN0518.

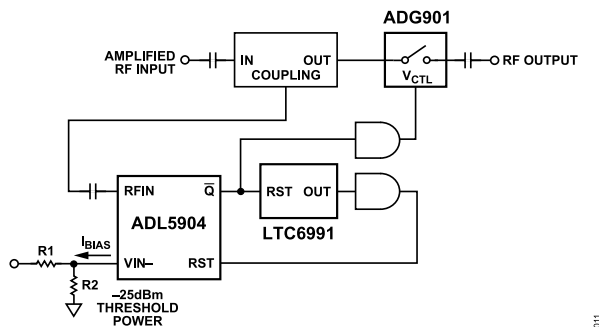


Figure 11. CN0518 Overpower Protection Circuit

As shown in Figure 11, the amplified RF input is sampled by a 25.5 dB RF directional coupler. This power is forwarded to the RFIN pin of the ADL5904, which is then sampled by the internal envelope detector. The ADL5904 threshold voltage level on  $V_{IN-}$  pin is set by a resistor divider network, which value can be computed using Equation 1:

$$V_{IN-} = \left[ \frac{3.3 \times R_2}{(R_2 \times R_1)} \right] + \left[ \frac{(R_1 \times R_2)}{(R_1 + R_2)} \times I_{BIAS} \right] \quad (1)$$

where:

$V_{IN-}$  is the voltage level at the  $V_{IN-}$  pin of the ADL5904.

$R_1$  is the user-defined resistance value.

$R_2$  is the user-defined resistance value.

$I_{BIAS}$  is the input bias current.

The CN0518 was set at -25 dBm input threshold power, which is equivalent to 0 dBm RF output to protect any sensitive downstream equipment connected to the receiver system. Table 1 can be found in the ADL5904 data sheet and shows the -25 dBm threshold power corresponds to a  $V_{IN-}$  voltage level of 17 mV when operating at 900 MHz.

Table 1. Recommended Typical Values for Threshold Voltage ( $V_{IN-}$ ) When Operating Uncalibrated

Input Threshold Power (dBm)	Threshold Voltage (mV)		
	100 MHz	900 MHz	1900 MHz
-25	18	17	16
-24	20	18	17
-23	22	20	19
-22	24	22	21
-21	26	25	23

The threshold level on  $V_{IN-}$  is set by a resistor divider. The value of  $R_1$  is primarily chosen to minimize loading on the 3.3 V rail, and  $R_2$  is chosen for an output impedance that is insensitive to leakage and bias currents. Setting  $R_1$  to 10 k $\Omega$  and using the power threshold value of 17 mV, the  $R_2$  value is calculated using Equation 1:

$$V_{IN-} = 17 \text{ mV}$$

$$I_{BIAS} = 20 \text{ }\mu\text{A}$$

$$R_1 = 10 \text{ k}\Omega$$

$$17 \text{ mV} = \left[ \frac{3.3 \times R_2}{10 \text{ k}\Omega \times R_2} \right] + \left[ \frac{10 \text{ k}\Omega \times R_2}{10 \text{ k}\Omega + R_2} \times 20 \text{ }\mu\text{A} \right]$$

$$R_2 = 48.8 \text{ }\Omega \text{ or } 49.9 \text{ }\Omega \text{ (using standard resistor value)}$$

Solving Equation 1 using the closest standard resistor value sets the  $V_{IN-}$  voltage level at 17 mV. This user-defined  $V_{IN-}$  voltage is then compared to the output voltage of the internal envelope detector, which is driven by the RF input level. When the power exceeds the threshold value, an overpowering event occurs which opens or isolates the RF path. The series combination of  $R_1$  and  $R_2$  results in a negligible divider current of 328  $\mu\text{A}$ .

The ADL5904 introduces an error level of up to +2.5 dBm on its RF threshold power and can vary from device-to-device. If an accurate threshold power is required, a simple calibration routine must be performed to compensate for the device-to-device variation. Refer to the ADL5904 data sheet for more information on the calibration routine.

### Automatic Reset Feature

The CN0518 also includes an automatic reset circuitry that activates when the power level returns within the acceptable range. This feature is done through the LTC6991, a programmable low frequency timer.

As shown in Figure 12, the  $\bar{Q}$  output of the ADL5904 holds the LTC6991 in reset mode during normal operation. When an overpowering event occurs, the LTC6991 is enabled and a 4 ms delay begins. The ADL5904 resets after 4 ms, effectively resampling the power level. If the overpowering condition persists, the ADL5904 trips again and the control signal of the RF switch enters the low state. This shift in signal isolates the RF input and output of the ADG901 switch. Once the overpower event subsides, the ADL5904 starts to resample the power level and then returns to its normal operation.

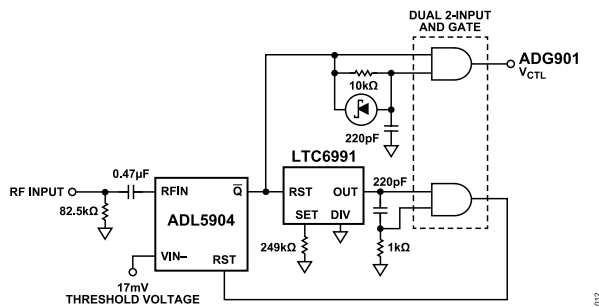


Figure 12. CN0518 Automatic Reset Circuitry

### Overpower Protection Test

Figure 13 presents the setup used to test the overpower protection functionality of the CN0518. In this test, the RF signal generator is set to 915 MHz center frequency and the power to the input is ramped up from -25 dBm to -15 dBm. The CN0518 output power is monitored using a high speed oscilloscope, which shows the response time from the overpowering event to the output power being attenuated.



Figure 13. RF Overpower Response Test Setup

Figure 14 shows the overpowering protection response time. Based on the figure, the output of the CN0518 has a response time of approximately 10 ns from its normal operation to the RF output power being attenuated.

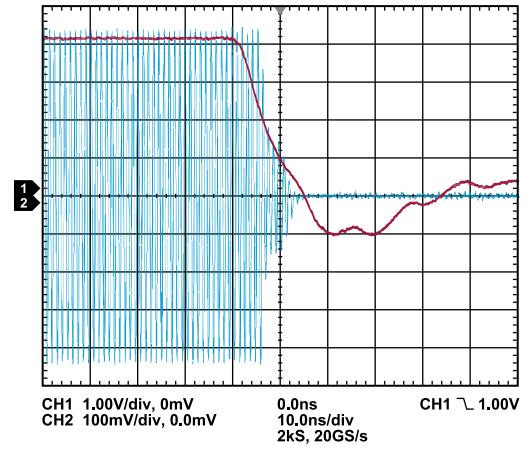


Figure 14. Typical Overpower Protection Response Time

Figure 15 shows the recovery time from when the overpowering condition subsides, and the power level returns back to its acceptable range. The data demonstrate a 5 ns delay from the attenuated RF output to its normal operation.

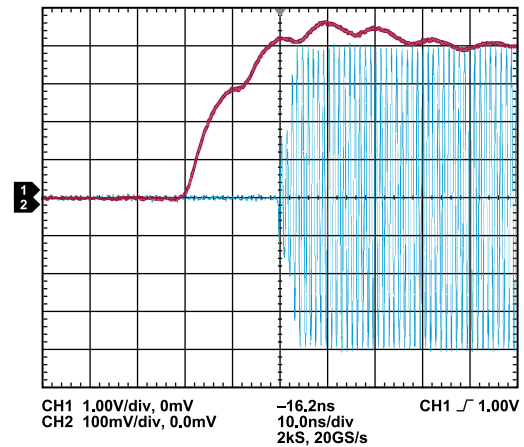


Figure 15. Typical Recovery Time after an Overpower Event

### USB POWER MANAGEMENT

The CN0518 sources its power through a micro-USB adapter, which typically provides a 5 V, 1 A supply via the micro-USB port. The nominal 4.75 V to 5.25 V input from the USB port is boosted to 5.6 V, then post-regulated to 5.0 V, 3.3 V, and 2.5 V. The circuit requires an overall current of approximately 260 mA from the USB supply during normal operation.

Figure 16 shows the complete CN0518 power tree.



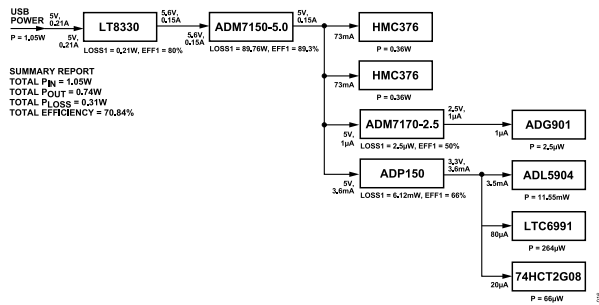


Figure 16. CN0518 Power Supply Architecture

### SEPIC Converter

The **LT8330** is a current-mode DC/DC converter capable of generating either positive or negative output voltages. It can be configured as boost, SEPIC, or inverting converter consuming as low as 6 µA of quiescent current. **Figure 17** shows the basic configuration needed to set the LT8330 for a 5.6 V output.

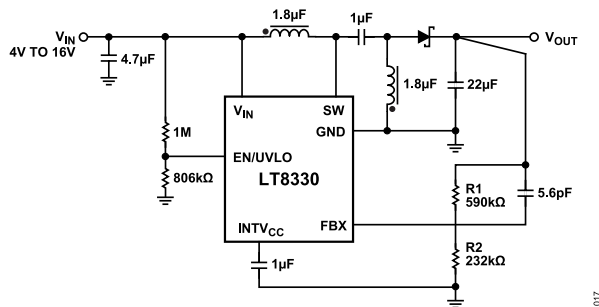


Figure 17. LT8330 Configuration for a 5.6 V Output

The output voltage is programmed with resistor divider from the output to the FBX pin of the LT8330. **Equation 2** shows how to calculate a desired output voltage with the user-defined resistor values:

$$R_1 = R_2 \left( \frac{V_{OUT}}{1.60} - 1 \right) \tag{2}$$

where:

$V_{OUT}$  is the desired output voltage in Volts.  
 $R_1, R_2$  are the user-defined resistor values.

For the required output voltage of 5.6 V, the equation results with  $R_1 = 590 \text{ k}\Omega$  and  $R_2 = 232 \text{ k}\Omega$ .

### Ultralow Noise Linear Regulator

The 5 V output from the **ADM7150** is used to power the two **HMC376** LNAs. The **ADM7150** is a low dropout linear regulator with a typical noise of 1 µV rms from 100 Hz to 100 kHz for fixed output voltage options and <1.7 nV/√Hz noise spectral density above 10 kHz.

The **ADP150** is used to generate 3.3 V for powering the RF detector and auto retry circuit. It is a high performance low dropout linear regulator featuring an ultralow noise and ultra high PSSR architecture for powering noise sensitive RF applications.

An **ADM7170-2.5** LDO regulator is used to generate the supply voltage required by the **ADG901** RF switch. This device has an input voltage range of 2.3 V to 6.5 V and a fixed output voltage of 2.5 V. The **ADM7170-2.5** only requires capacitors for proper operation. Particularly, the **ADM7170-2.5** is compatible to use small decoupling capacitors of 4.7 µF on its input and output pins.

### COMMON VARIATIONS

The **ADL5523** can be used as an alternative low noise amplifier for applications using the 915 MHz ISM band. This device offers a slightly higher gain (S21) and a low noise figure at a cost of having lower return losses (S11, S22), output third-order intercept, and 1 dB compression point.

The **ADG902** can also be used as the RF switch, this device is pin-compatible and shares the same specifications as the **ADG901**, but it is a reflective switch and offers lower isolation loss.

Analog Devices, Inc. also offers a similar reference design for receiver amplifiers operating in the 433.92 MHz, 2.4 GHz, and 5.8 GHz ISM bands. For more information, please refer to the **CN0555**, **CN0521**, and **CN0534** circuit notes.

If you are working in the 915 MHz ISM band and needs a transmit signal chain solution, refer to the **CN0522** reference design.

### CIRCUIT EVALUATION AND TEST

This section describes the setup and procedure for the CN0518 circuit evaluation. For complete details, refer to the **CN0518 User Guide**.

### EQUIPMENT NEEDED

- ▶ EVAL-CN0518-EBZ circuit evaluation board
- ▶ Signal generator (Rohde & Schwarz® SMA100B)
- ▶ Signal analyzer (Keysight® E5052B)
- ▶ Vector network analyzer (Keysight N5242A PNA-X)
- ▶ 5 V, ≥0.5 A AC/DC power adapter with micro-USB cable
- ▶ SMA cables

### SETUP AND TEST

**Figure 18** shows the functional block diagram for the S-Parameter and noise figure test setup.

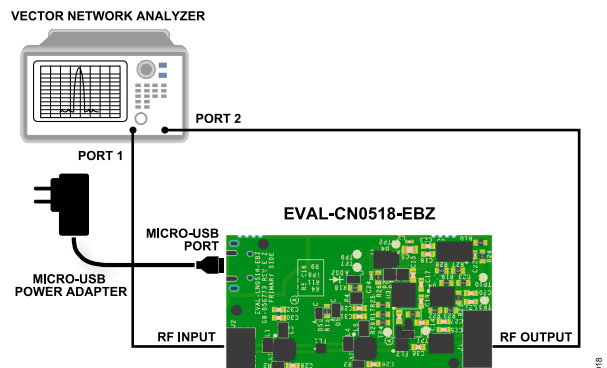


Figure 18. S-Parameter and Noise Figure Test Setup

The procedure for measuring S-Parameters and the noise figure are as follows:

1. Set the measurement conditions of the vector network analyzer as follows:
  - a. Set the frequency span from 902 MHz to 928 MHz.
  - b. Set the frequency step size to 10 kHz.
  - c. The power level must be less than or equal to -30 dBm.
2. Perform a full 2-port calibration of the vector network analyzer using a calibration kit. Note that the RF output of the EVAL-CN0518-EBZ can be connected directly to a test port, so that only one measurement cable is needed for the test setup.
3. Connect the EVAL-CN0518-EBZ across the test ports of the vector network analyzer using the calibrated test setup.
4. Power up the EVAL-CN0518-EBZ using the 5 V power adapter.
5. Set the vector network analyzer to display the traces of the individual S-Parameters and the noise figure.
6. Compare the measurements to the expected values. At 915 MHz center frequency, the values for input and output return losses are approximately -20 dB and -12 dB, respectively. For the gain and noise figure readings, values should be approximately 25 dB and 0.8 dB, respectively.
5. Power up the EVAL-CN0518-EBZ using the 5 V power adapter.
6. Execute a measurement run on the signal analyzer.
7. Using the signal analyzer, get the phase noise value and verify if it is approximately -129 dBc/Hz at 100 kHz offset.
8. Run the SFDR test and compare the readings; expected value is approximately 76 dBFS.

Figure 19 shows the functional block diagram for the phase noise and SFDR test setup.

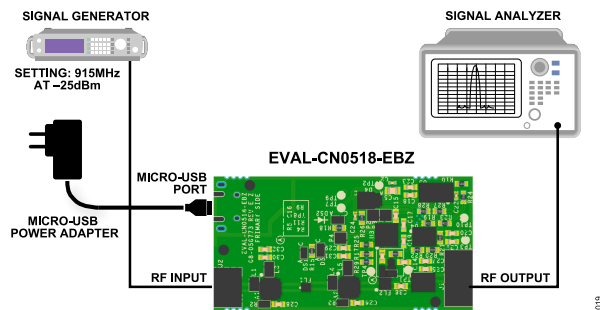


Figure 19. Phase Noise and SFDR Test Setup

To perform the phase noise and SFDR tests, follow the steps below:

1. Set the measurement configuration of the signal analyzer as follows:
  - a. For SFDR measurement, set the center frequency to 915 MHz, the frequency span to 902 MHz to 928 MHz, and the RF amplitude to -30 dBm.
  - b. For phase noise measurement, set the center frequency to 915 MHz and the offset frequency range to 10 Hz to 30 MHz.
2. Set the power level of the signal generator between -30 dBm to -20 dBm with a center frequency set at 915 MHz.
3. Connect the signal generator output to the RF input of the EVAL-CN0518-EBZ.
4. Connect the RF output of the EVAL-CN0518-EBZ to the signal analyzer.

## LEARN MORE

[CN0518 Design Support Package](#)

[ADIsimRF™ RF Signal Chain Calculator](#)

[LTspice® SPICE Simulation Software](#)

[LTpowerCAD® Design Tool](#)

[MT-031 Tutorial, \*Grounding Data Converters and Solving the Mystery of “AGND” and “DGND”\*, Analog Devices.](#)

[MT-073 Tutorial, \*High Speed Variable Gain Amplifiers \(VGAs\)\*, Analog Devices.](#)

[MT-101 Tutorial, \*Decoupling Techniques\*, Analog Devices.](#)

[Whitlow, Dana. \*Design and Operation of Automatic Gain Control Loops for Receivers in Modern Communications Systems\*. Chapter 8. Analog Devices Wireless Seminar. 2006.](#)

[ADG901 Evaluation Board](#)

[ADL5904 Data Sheet](#)

[ADL5904 Evaluation Board](#)

[LT8330 Data Sheet](#)

[LT8330 Evaluation Board](#)

[ADP150 Data Sheet](#)

[ADP150 Evaluation Board](#)

[ADM7150 Data Sheet](#)

[ADM7150 Evaluation Board](#)

[ADM7170 Data Sheet](#)

[ADM7170 Evaluation Board](#)

[LTC6991 Data Sheet](#)

[LTC6991 Evaluation Board](#)

## DATA SHEETS AND EVALUATION BOARDS

[HMC376 Data Sheet](#)

[HMC376 Evaluation Board](#)

[ADG901 Data Sheet](#)

## REVISION HISTORY

**05/2023—Revision 0: Initial Version**



### ESD Caution

**ESD (electrostatic discharge) sensitive device.** Charged devices and circuit boards can discharge without detection. Although this product features patented or proprietary protection circuitry, damage may occur on devices subjected to high energy ESD. Therefore, proper ESD precautions should be taken to avoid performance degradation or loss of functionality.

(Continued from first page) Circuits from the Lab circuits are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the Circuits from the Lab circuits in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab circuits. Information furnished by Analog Devices is believed to be accurate and reliable. However, Circuits from the Lab circuits are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any Circuits from the Lab circuits at any time without notice but is under no obligation to do so.

