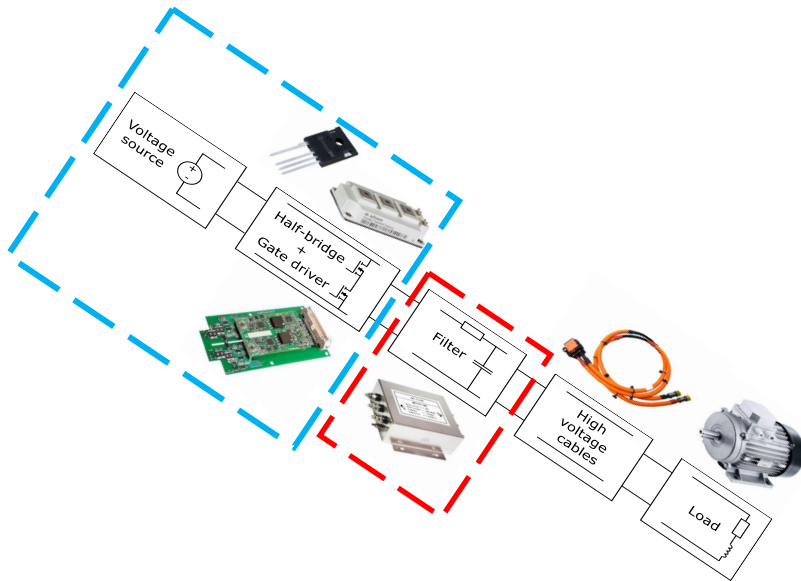


# Double pulse testing

Philip Abrahamsson



IMZ120R140M1H  
CoolSiC™ 1200V SiC Trench MOSFET  
Electrical Characteristics



## 3.3 Switching characteristics

Table 6 Switching characteristics, inductive load *						
Parameter	Symbol	Conditions	Value			Unit
			min.	typ.	max.	
<b>MOSFET Characteristics, <math>T_a = 25^{\circ}\text{C}</math></b>						
Turn-on delay time	$t_{\text{dson}}$	$V_{\text{DS}} = 800\text{V}$ , $I_{\text{D}} = 6\text{A}$ , $V_{\text{GS}} = 0/18\text{V}$ , $R_{\text{DS(on)}} = 2\Omega$ , $L_{\text{d}} = 40\text{nH}$ ,	-	5	-	ns
Rise time	$t_r$	diode:	-	2	-	
Turn-off delay time	$t_{\text{dsoff}}$	body diode at $V_{\text{GS}} = 0\text{V}$ see Fig. E	-	10.3	-	
Fall time	$t_f$		-	11.6	-	
Turn-on energy	$E_{\text{on}}$		-	62	-	$\mu\text{J}$
Turn-off energy	$E_{\text{off}}$		-	12	-	
Total switching energy	$E_{\text{sw}}$		-	74	-	
<b>Body Diode Characteristics, <math>T_a = 25^{\circ}\text{C}</math></b>						
Diode reverse recovery charge	$Q_{\text{rr}}$	$V_{\text{DS}} = 800\text{V}$ , $I_{\text{D}} = 6\text{A}$ , $V_{\text{GS}}$ at diode = $0\text{V}$ , $dI_{\text{D}}/dt = 1000\text{A}/\mu\text{s}$ , $Q_{\text{rr}}$ includes also $Q_{\text{r1}}$ , see Fig. C	-	100	-	nC
Diode peak reverse recovery current	$I_{\text{rrm}}$		-	2	-	A



Other applications

# Power Transistor



- It takes some time for the current and voltage to fall/rise
- Losses are generated during a switching event

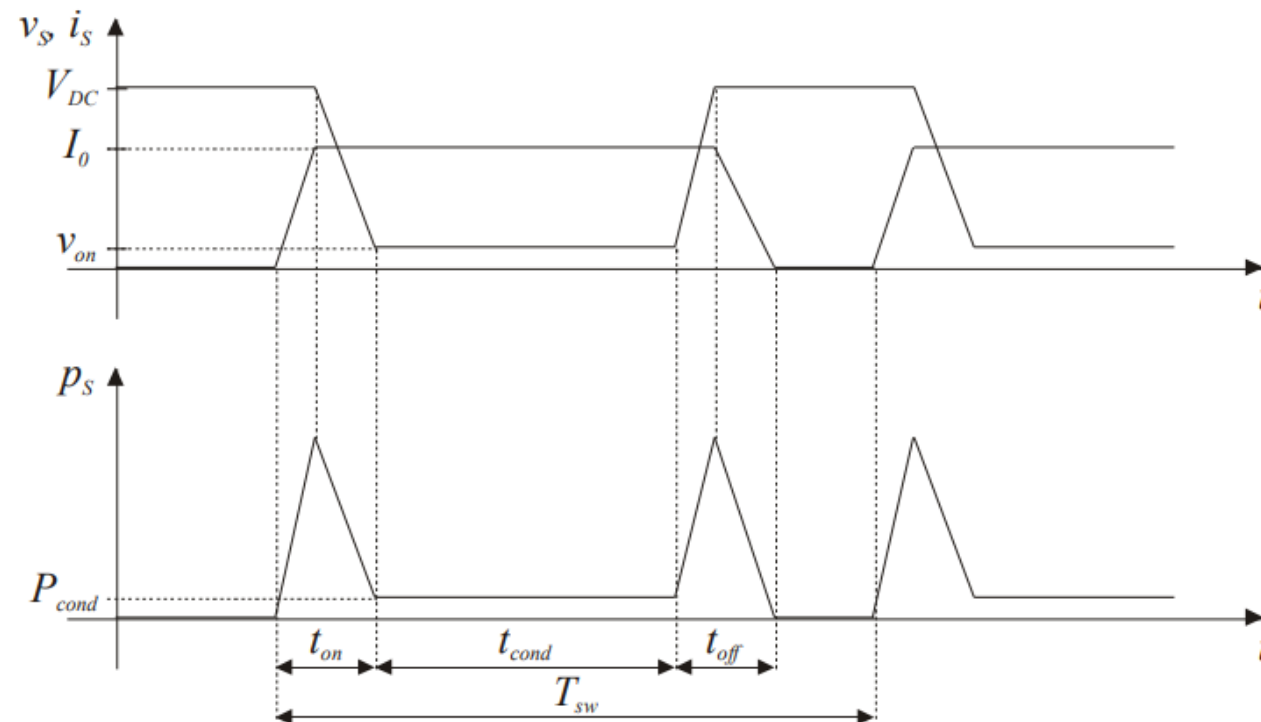


Figure 6.2: Approximate switching waveforms for the switch  $S$ .

# Measure switching characteristics

- Measure current and voltage during turn on and off events.
- Double pulse testing

IMZ120R140M1H

CoolSiC™ 1200V SiC Trench MOSFET


Electrical Characteristics





## 3.3 Switching characteristics

Table 6 Switching characteristics, Inductive load <sup>4</sup>



Parameter	Symbol	Conditions	Value			Unit
			min.	typ.	max.	
MOSFET Characteristics, $T_{vj} = 25^{\circ}\text{C}$						
Turn-on delay time	$t_{d(\text{on})}$	$V_{DD} = 800\text{V}$ , $I_D = 6\text{A}$ , $V_{GS} = 0/18\text{V}$ , $R_{G,\text{ext}} = 2\Omega$ , $L_{\sigma} = 40\text{nH}$ , diode: body diode at $V_{GS} = 0\text{V}$ see Fig. E	-	5	-	ns
Rise time	$t_r$		-	2	-	
Turn-off delay time	$t_{d(\text{off})}$		-	10.3	-	
Fall time	$t_f$		-	11.6	-	
Turn-on energy	$E_{\text{on}}$		-	62	-	$\mu\text{J}$
Turn-off energy	$E_{\text{off}}$		-	12	-	
Total switching energy	$E_{\text{tot}}$		-	74	-	
Body Diode Characteristics, $T_{vj} = 25^{\circ}\text{C}$						
Diode reverse recovery charge	$Q_{rr}$	$V_{DD} = 800\text{V}$ , $I_{SD} = 6\text{A}$ , $V_{GS}$ at diode = $0\text{V}$ , $di/dt = 1000\text{A}/\mu\text{s}$ , $Q_{rr}$ includes also $Q_C$ , see Fig. C	-	100	-	nC
Diode peak reverse recovery current	$I_{rrm}$		-	2	-	A

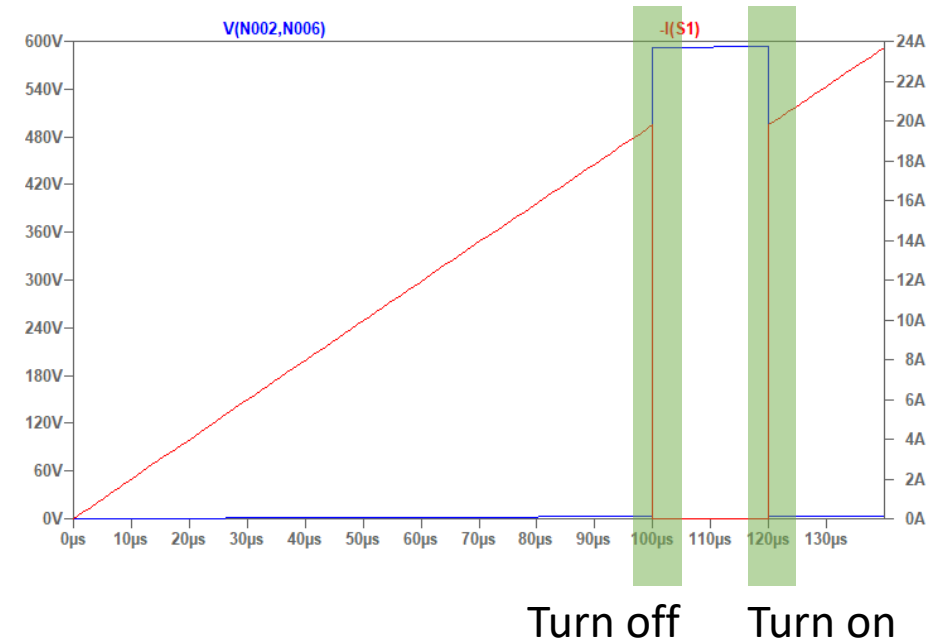

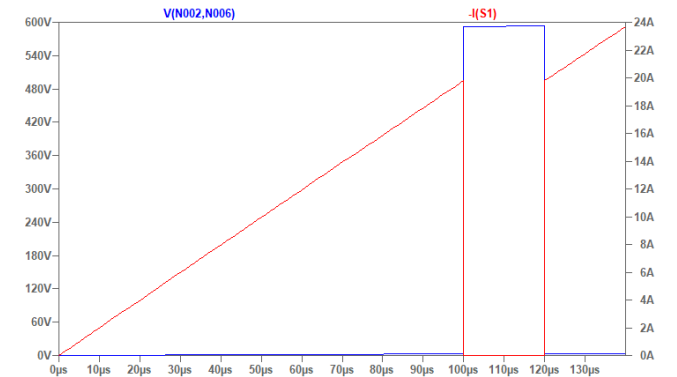
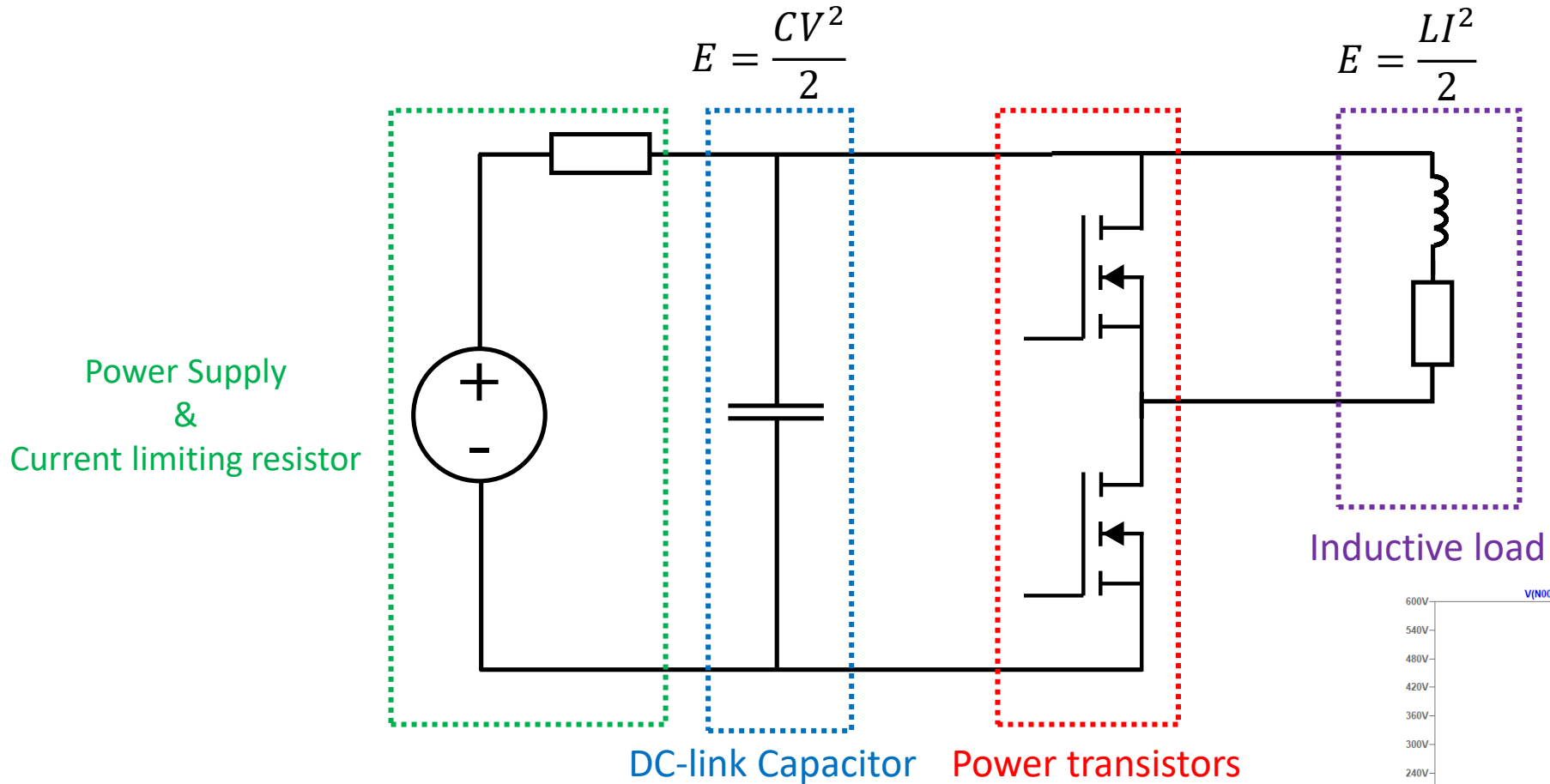
# Double pulse tester – The different parts





# Double pulse tester – How it works

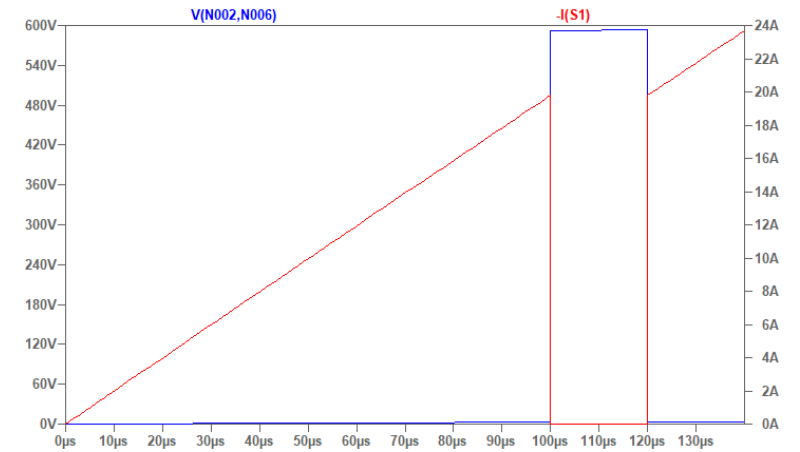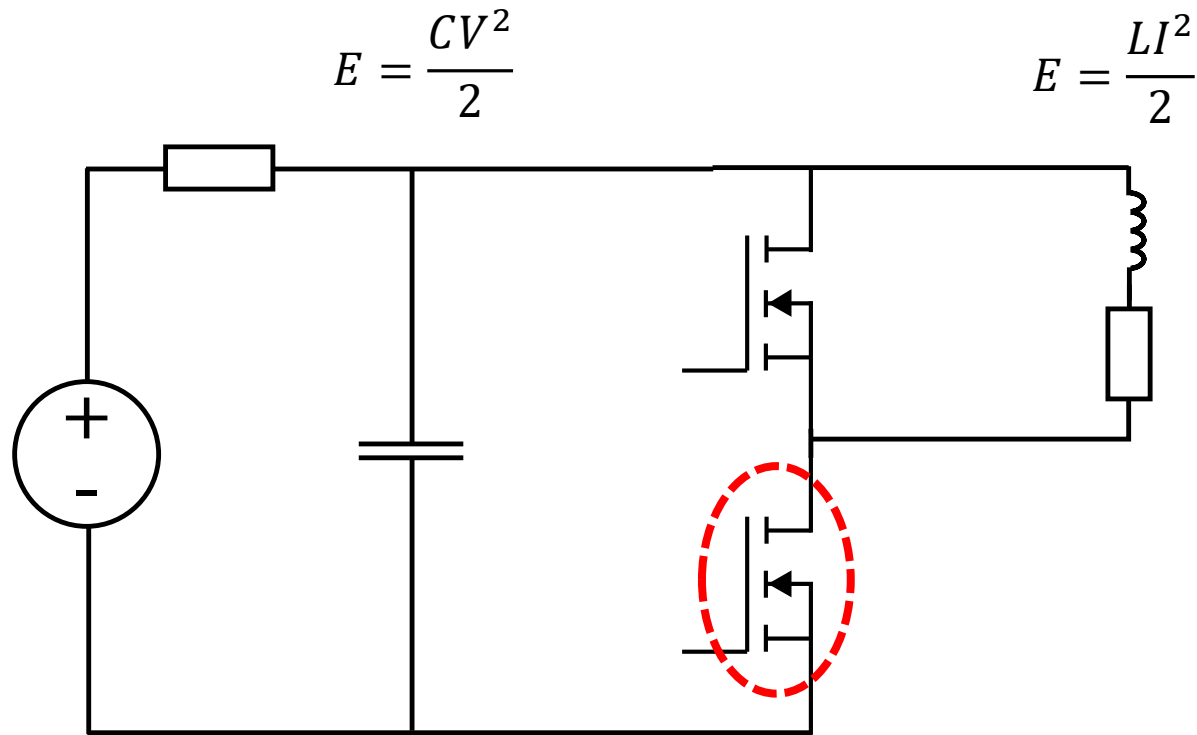



# Double pulse tester – How it works

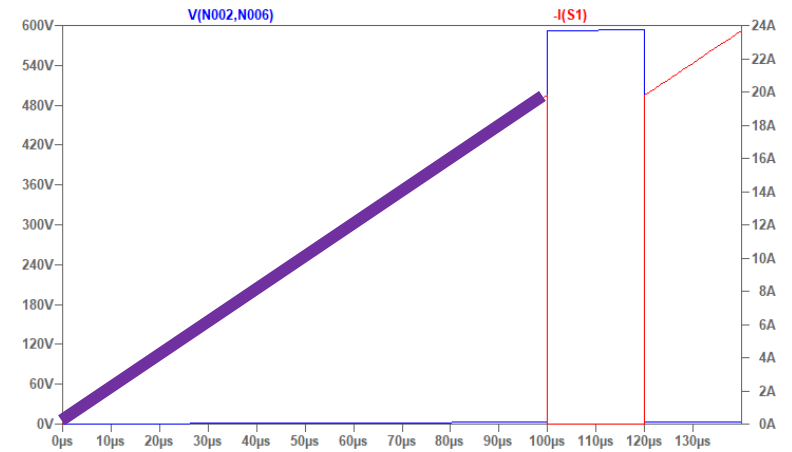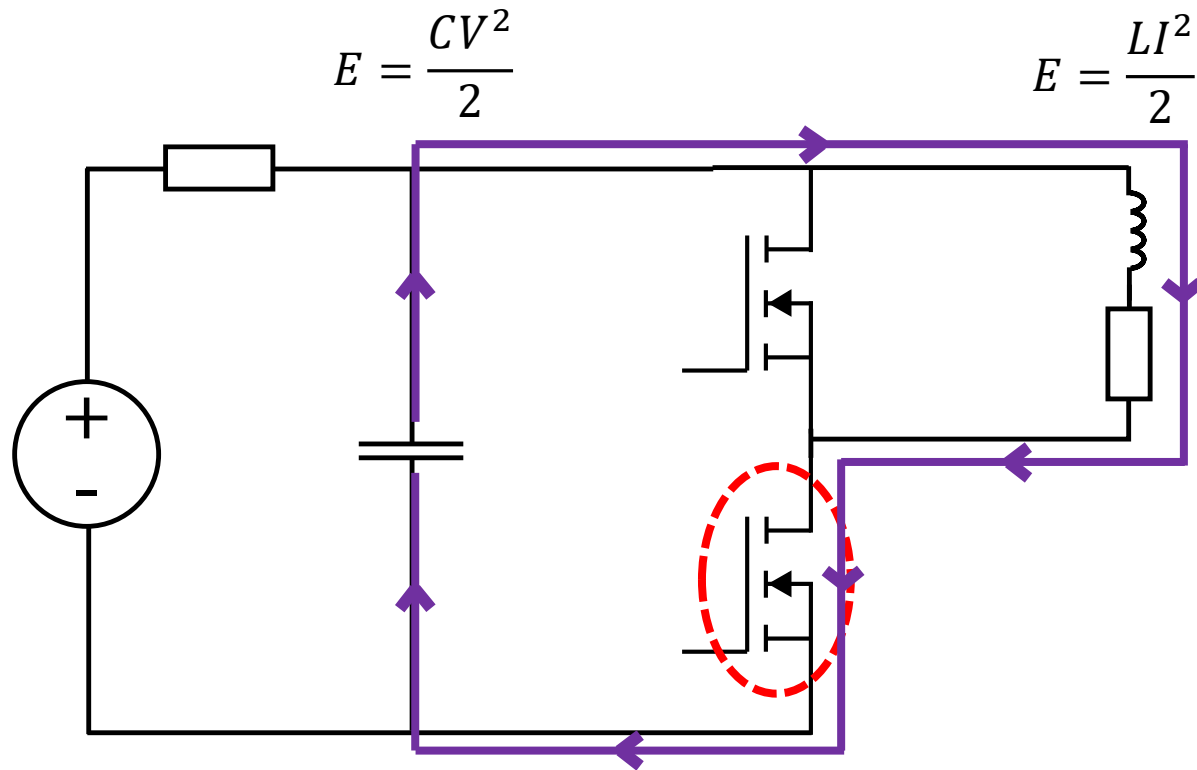

# Double pulse tester – How it works

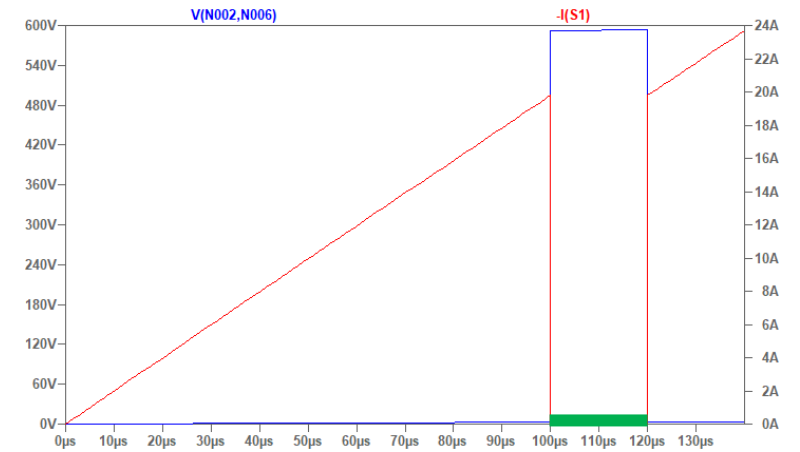
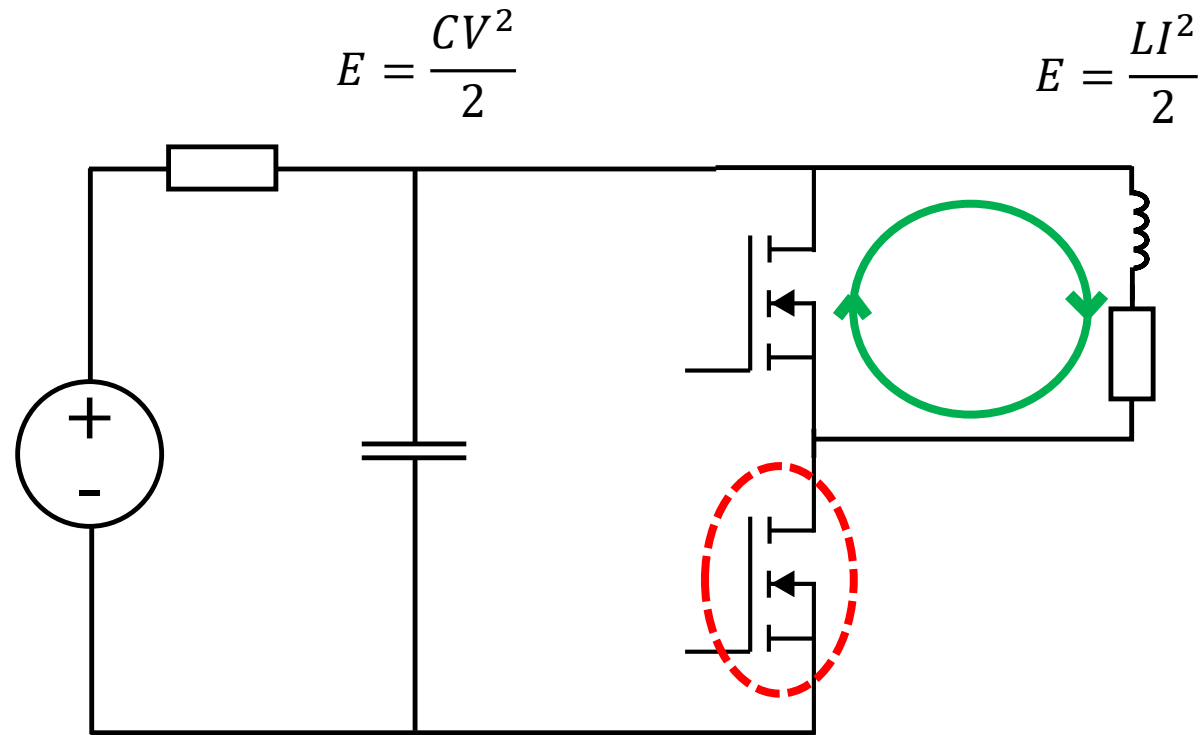


# Double pulse tester – How it works

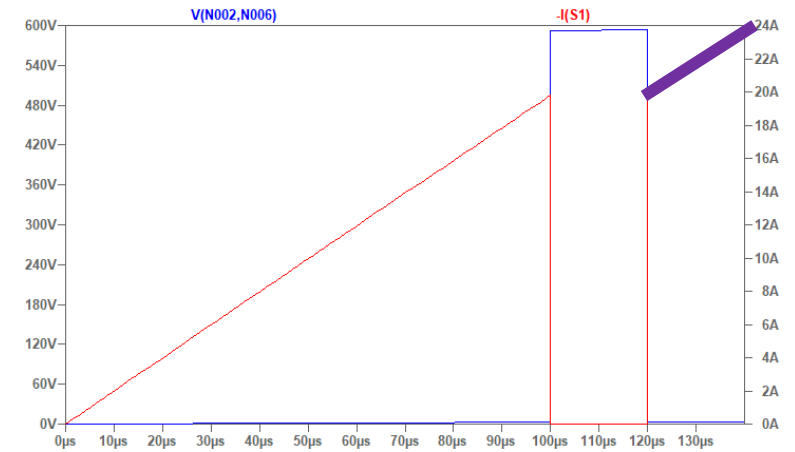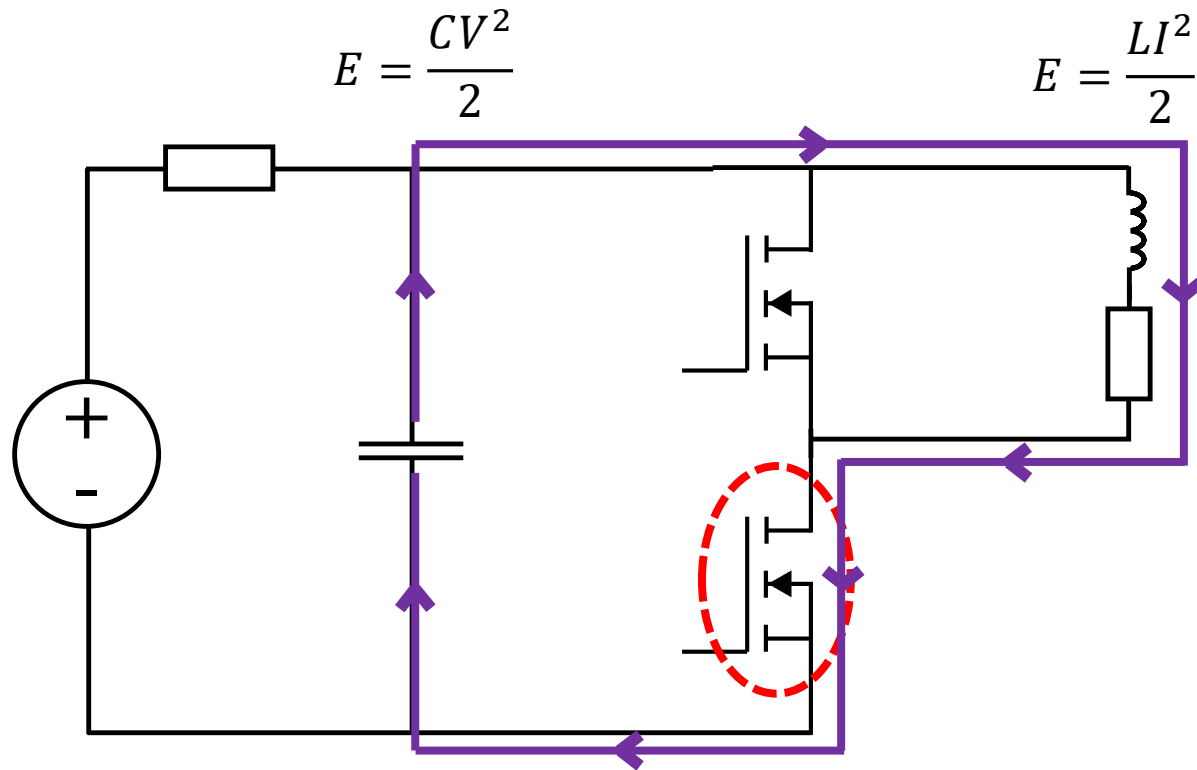





# Double pulse tester – How it works

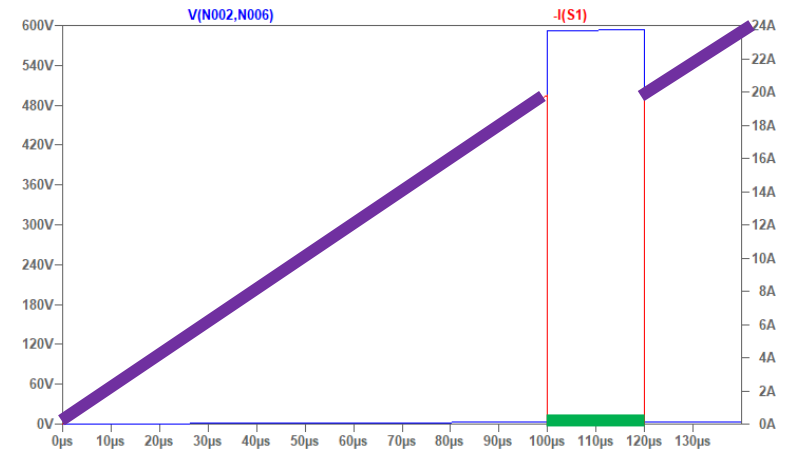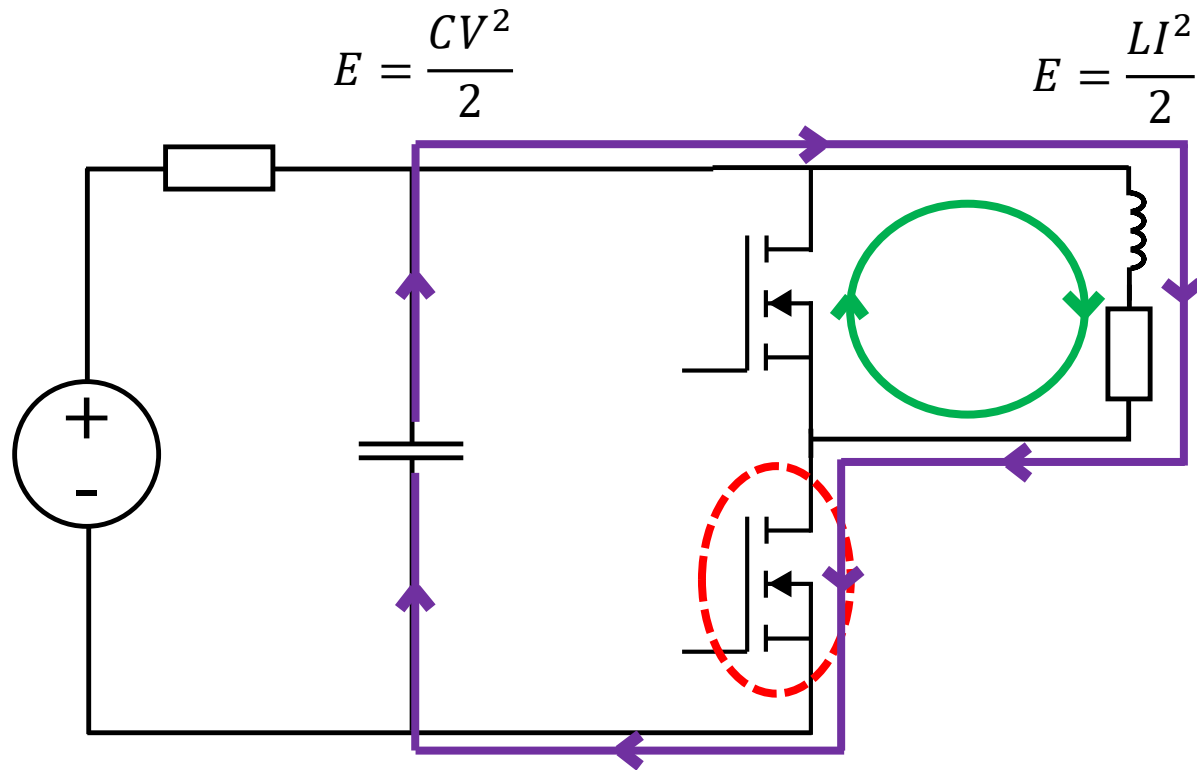
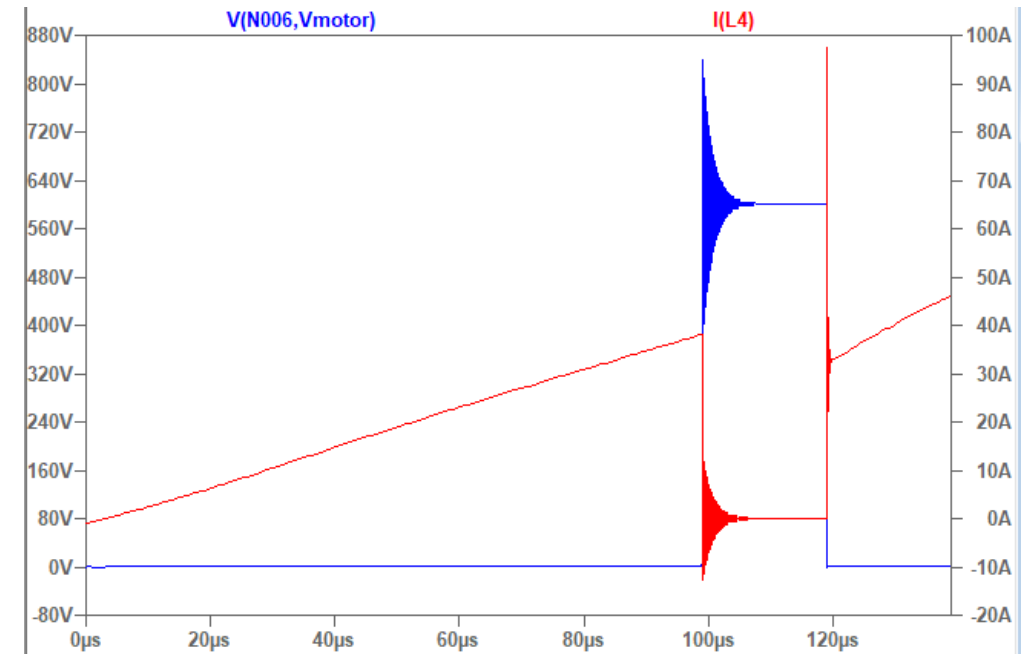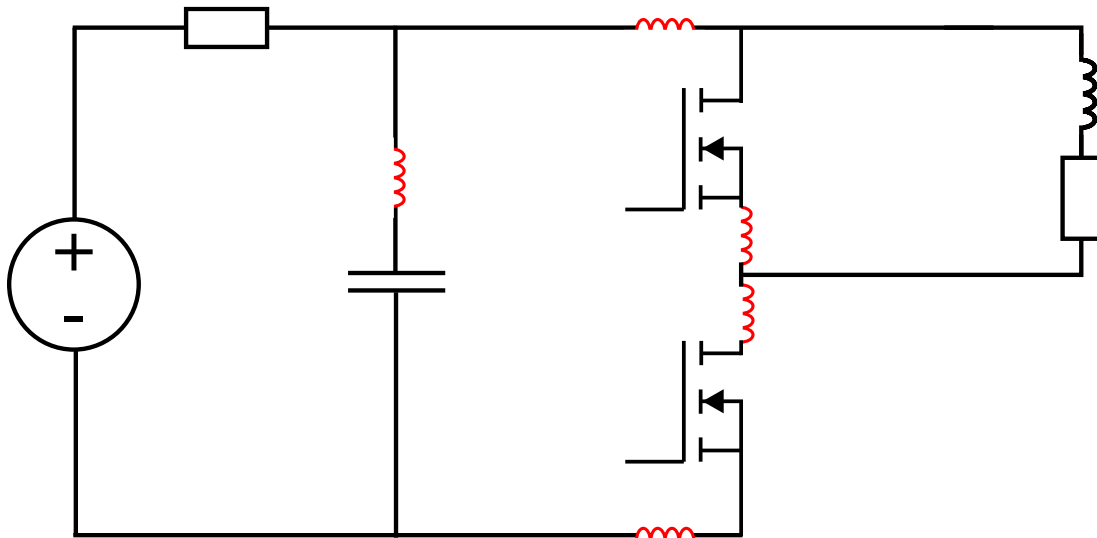
# Double pulse tester – Parasitics

- Parasitics are present in any real circuit
- Non ideal switching events



# PCB design

- A good PCB design can reduce stray inductance

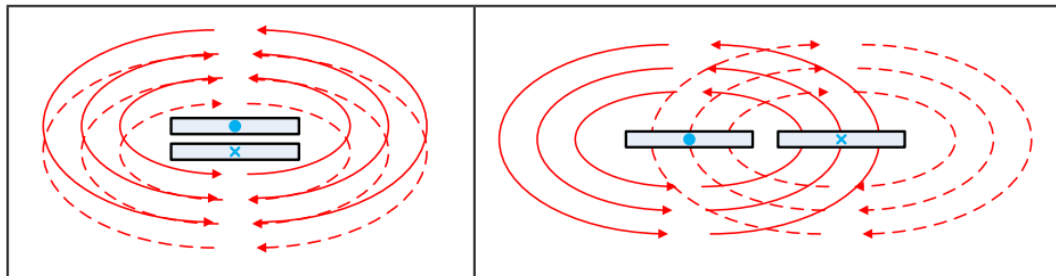
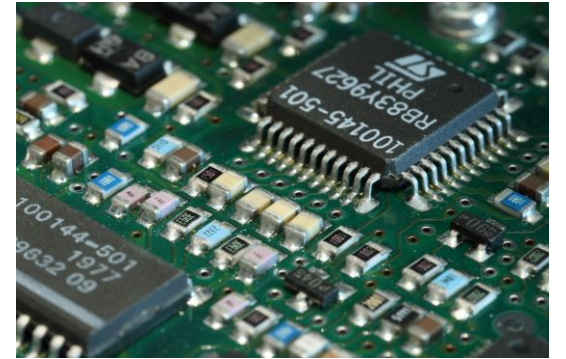


Figure 6: Parallel plate overlap

Figure 7: Coplanar plate overlap



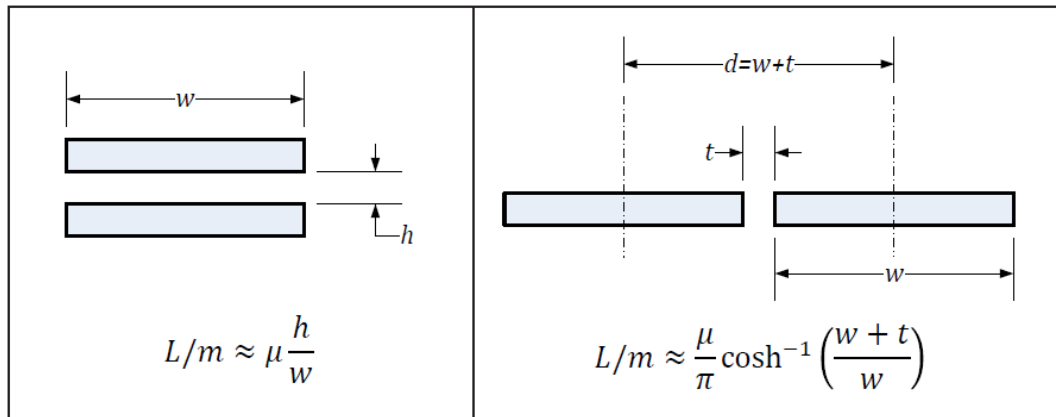
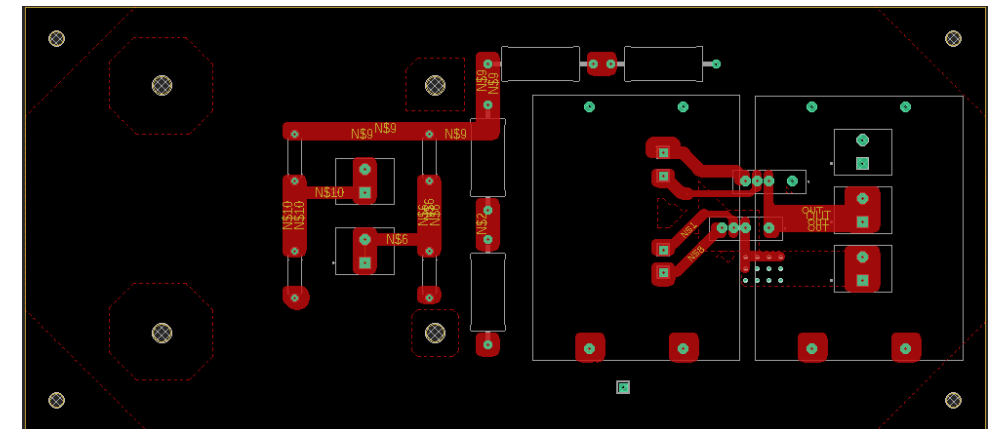


Figure 8: Parallel plate inductance approximation

Figure 9: Coplanar plate inductance approximation

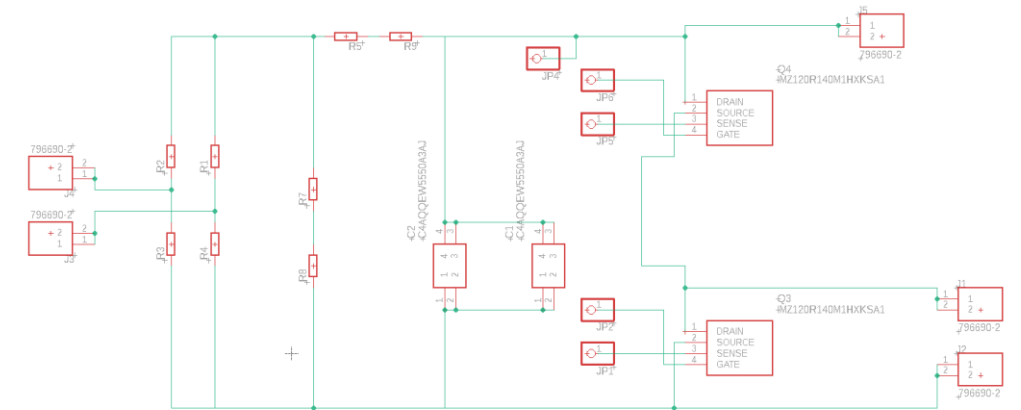

# Results – PCB (Prototype 1 only 30V)

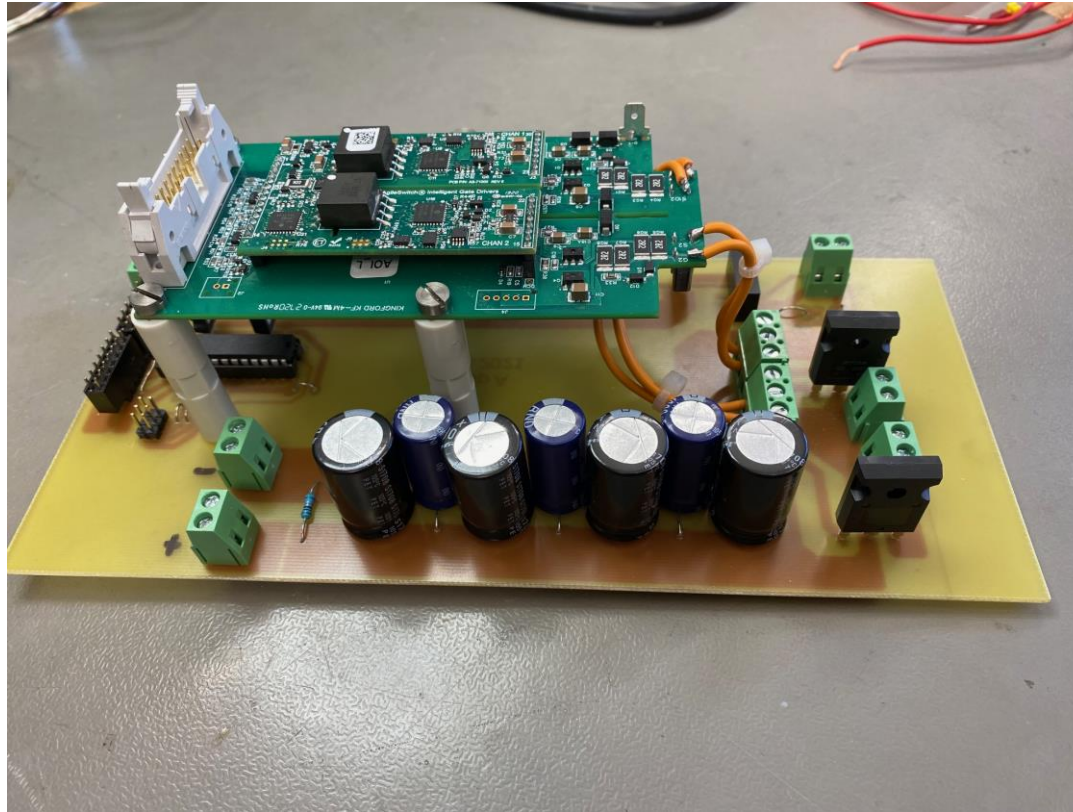


# Results

- Video from the lab
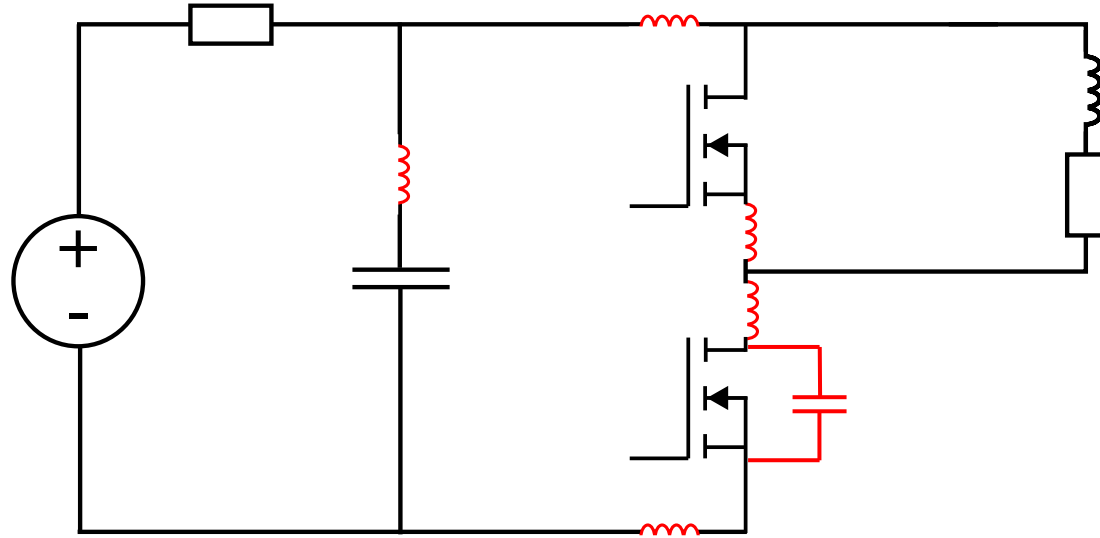
# Results

- Ringing is also caused by capacitance in the circuit



# Results - Measurements

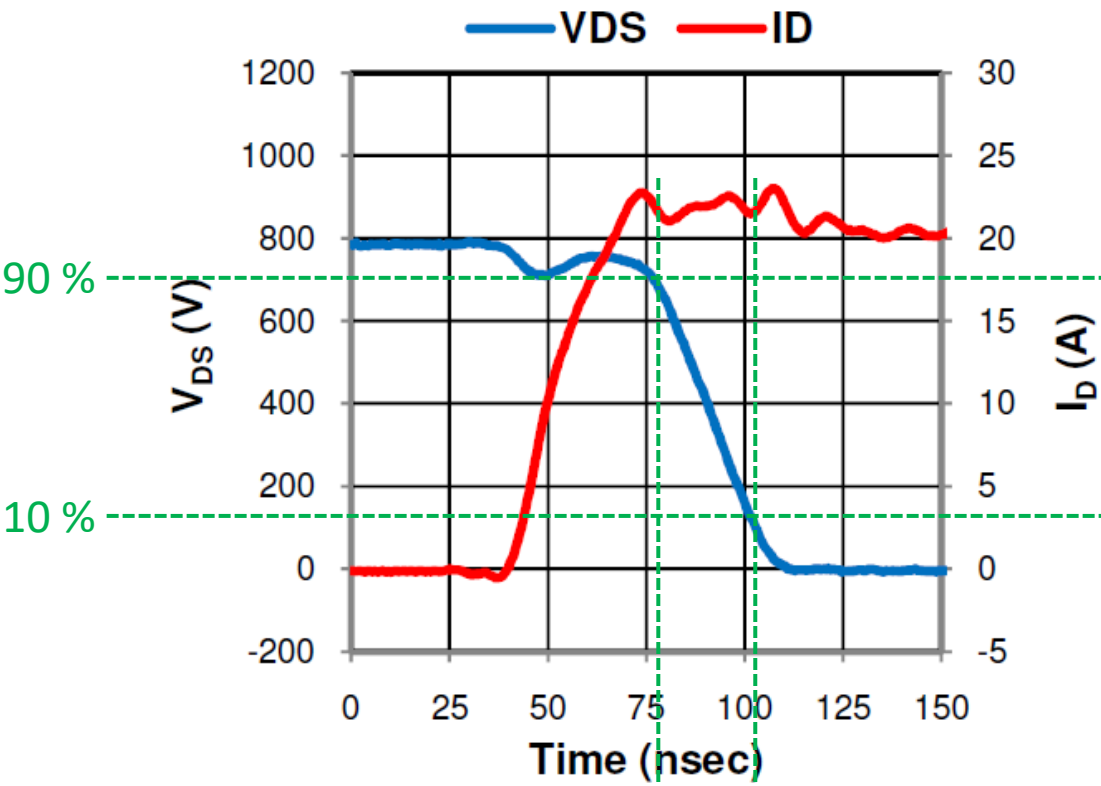


Figure 9: Turn-On Waveforms


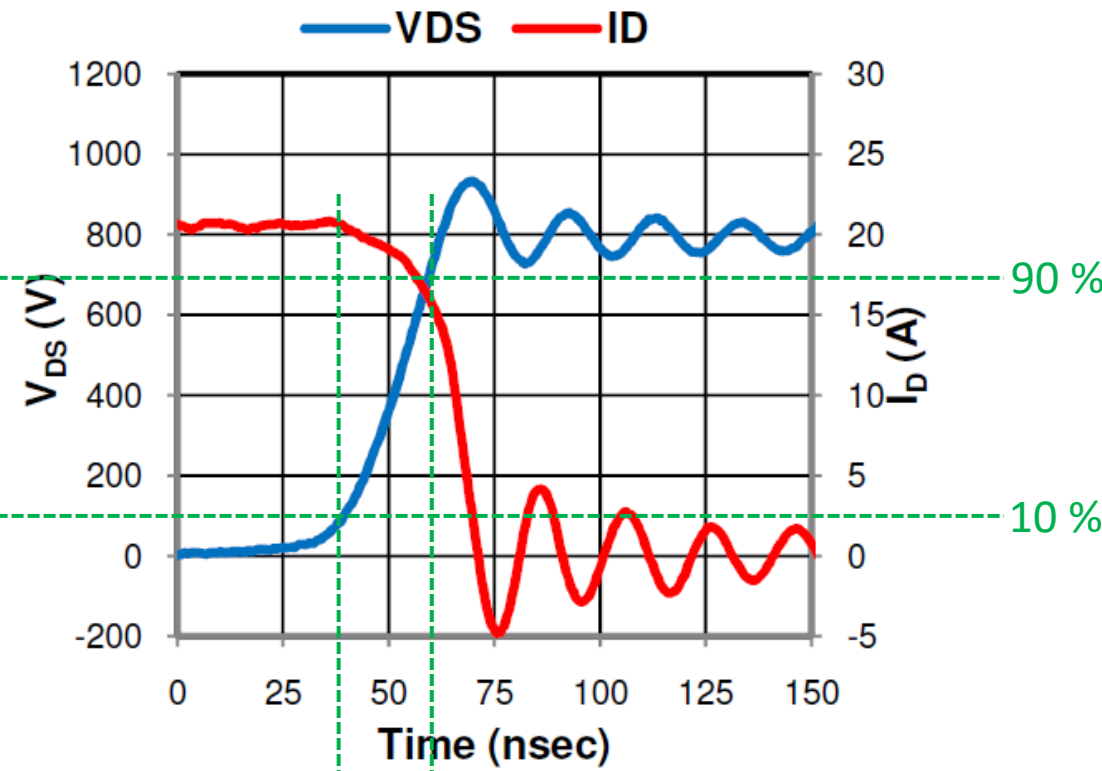


Figure 10: Turn-Off Waveforms

# Measurement equipment - Properties

- Bandwidth
- Delay
- Accuracy

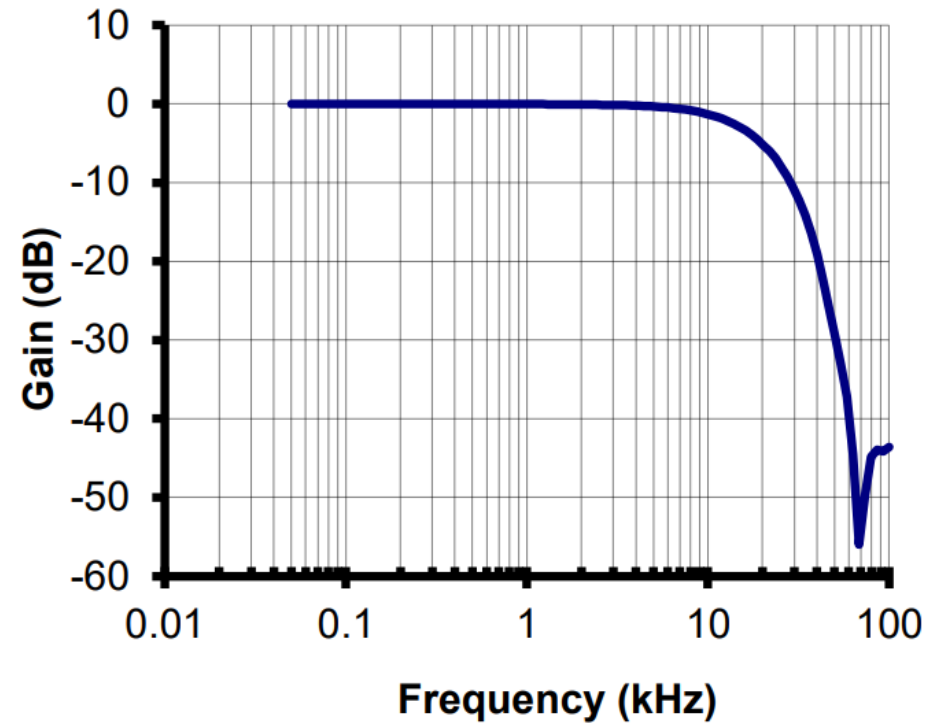




# Measurement equipment – Examples of probes

Single ended



Differential

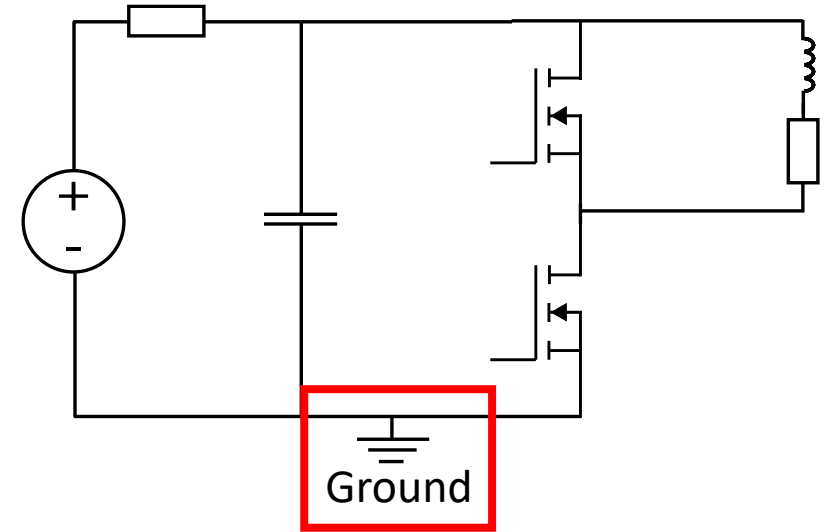

# Measurement equipment – Examples of probes


Resistor



Rogowski coil



Source Current (A)

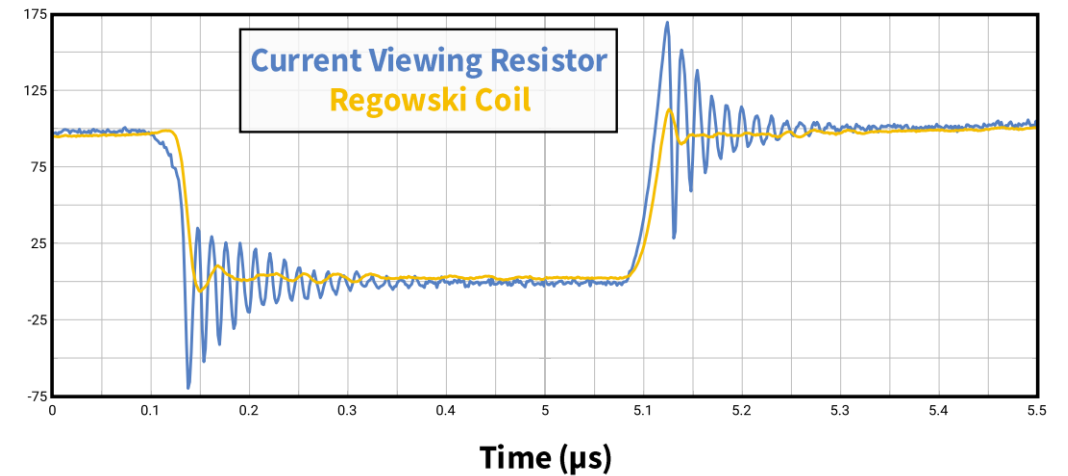


# What else can the double pulse tester be used for?

Investigate how switching events effect electric insulation


- Switching events cause high  $dV/dt$
- High  $dV/dt$  can break down insulation in electric machines






# Test of electric insulation

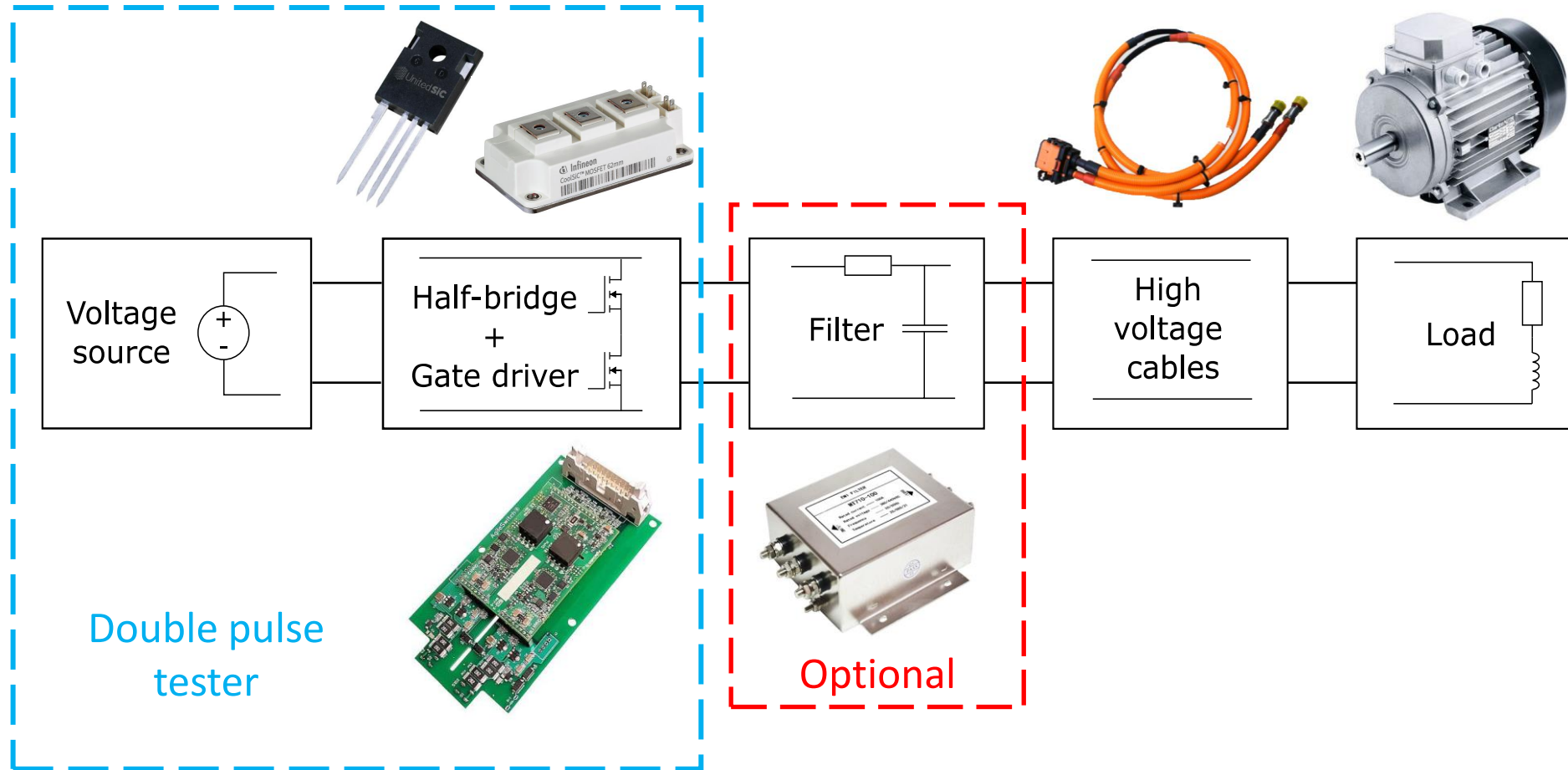

# Programmable gate driver

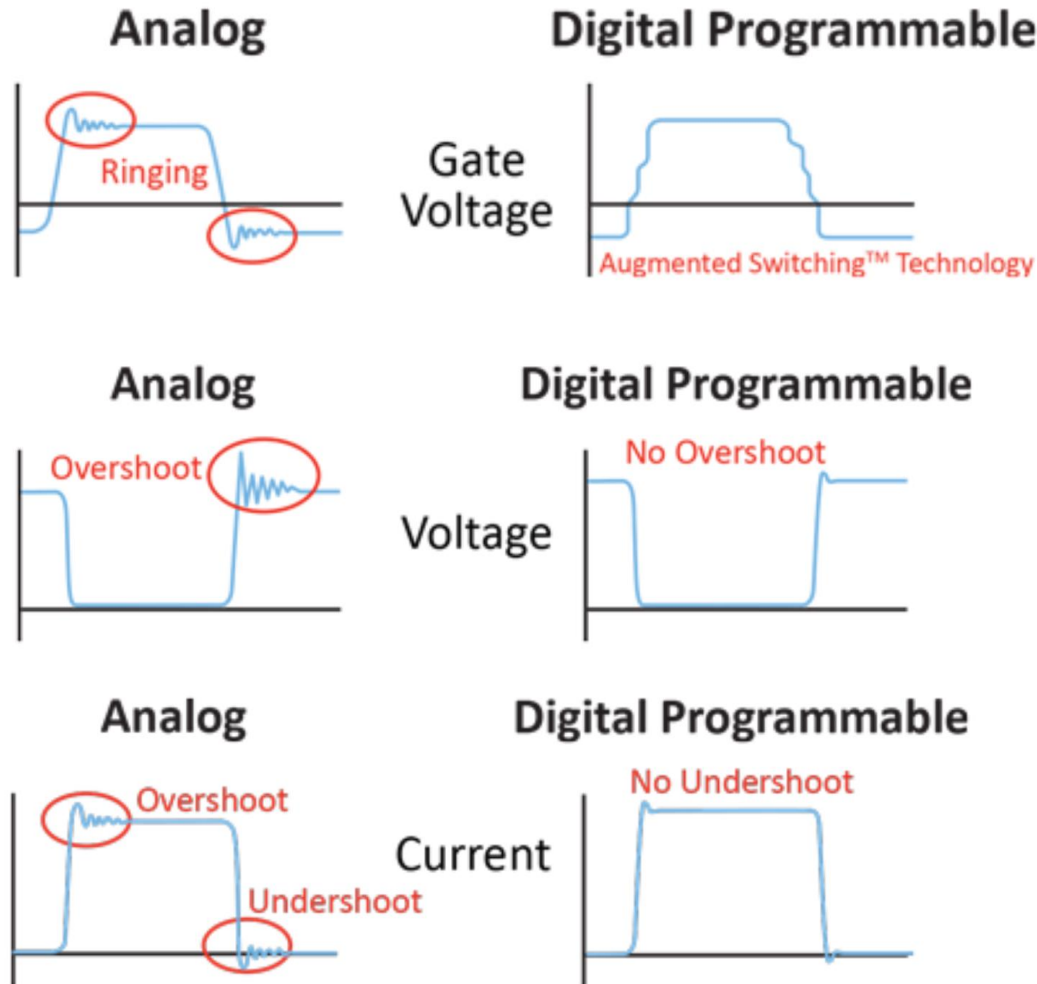

# Filter - Reduce $dV/dt$

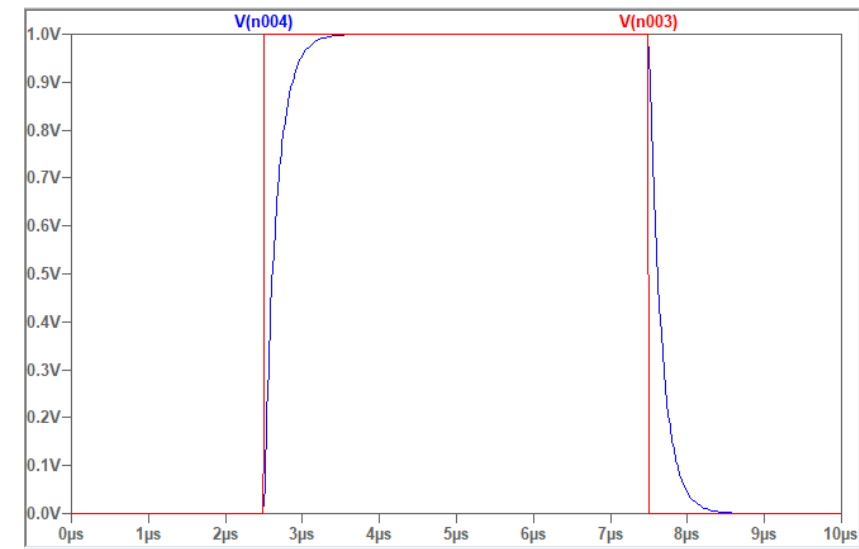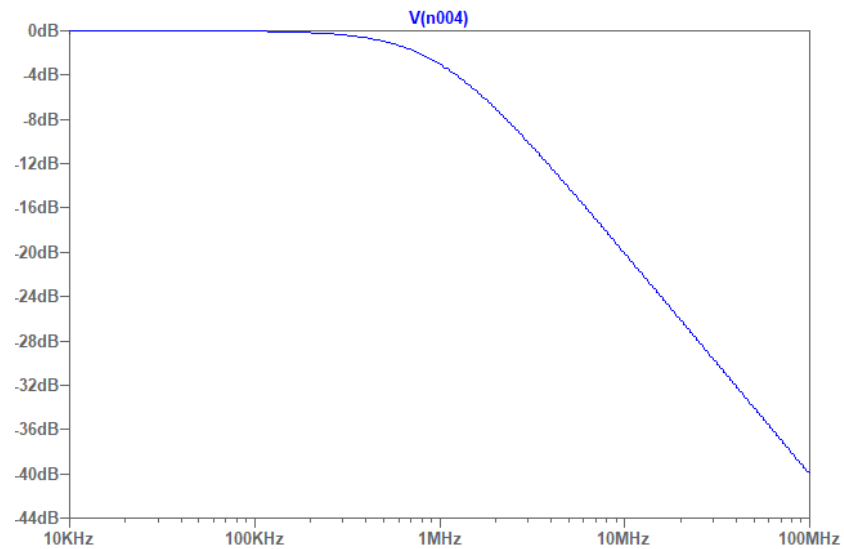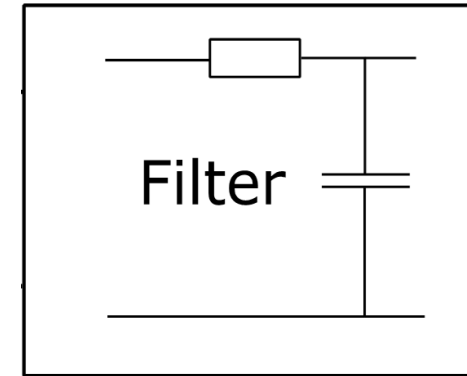

# Summary

- A double pulse tester can be used to characterize power transistors
- PCB design is important for proper switching performance
- High bandwidth is needed for the measurement equipment

# Questions?