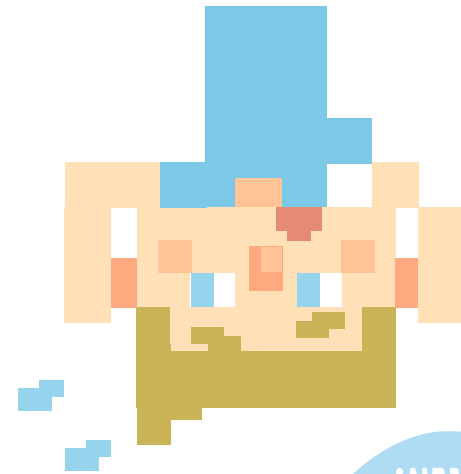





Author: Mauro César Zanella
English Version: Marco Aurélio Lotz
Design: Ricardo Enz



Pressure (Voltage) What is that?

Battery

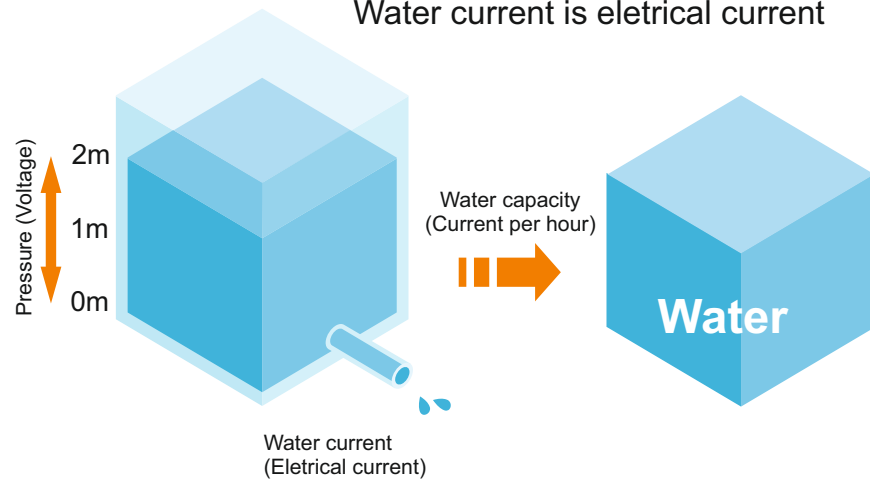
Pressure is the voltage
Volume is the capacity
Water current is electrical current




Pressure (Voltage) Capacity?

Battery



Same voltages
But different capacities

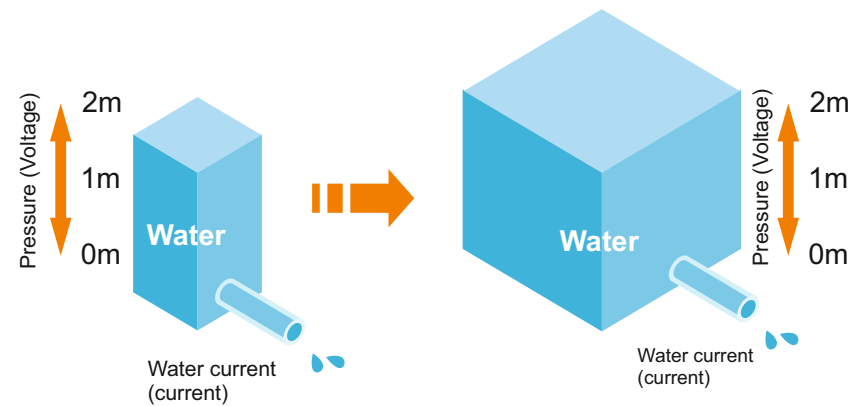


Pressure (Voltage)

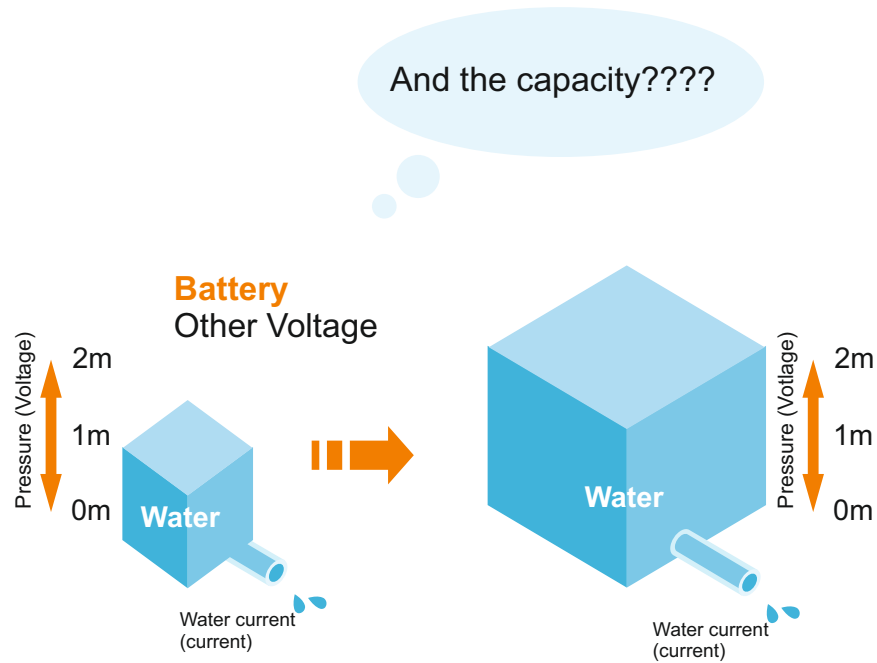

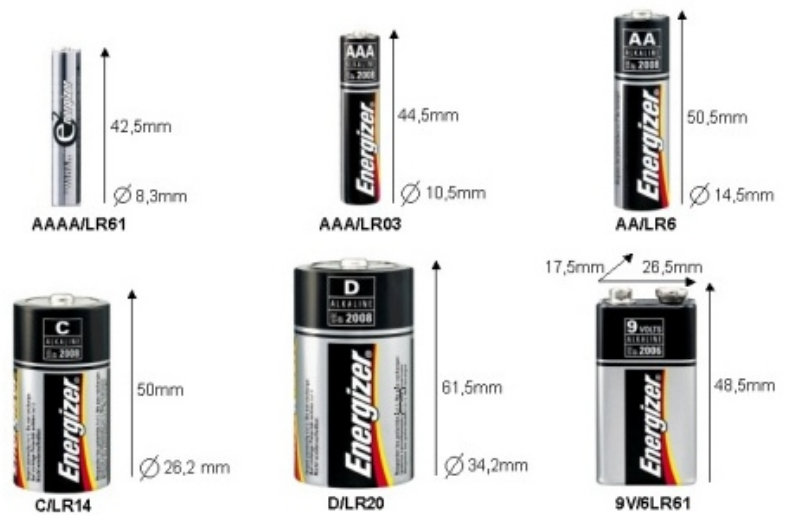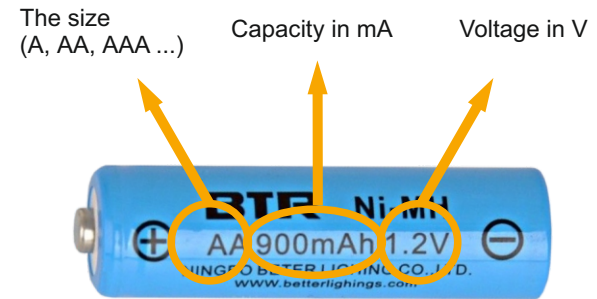Do I understand the batteries from the supermarket?




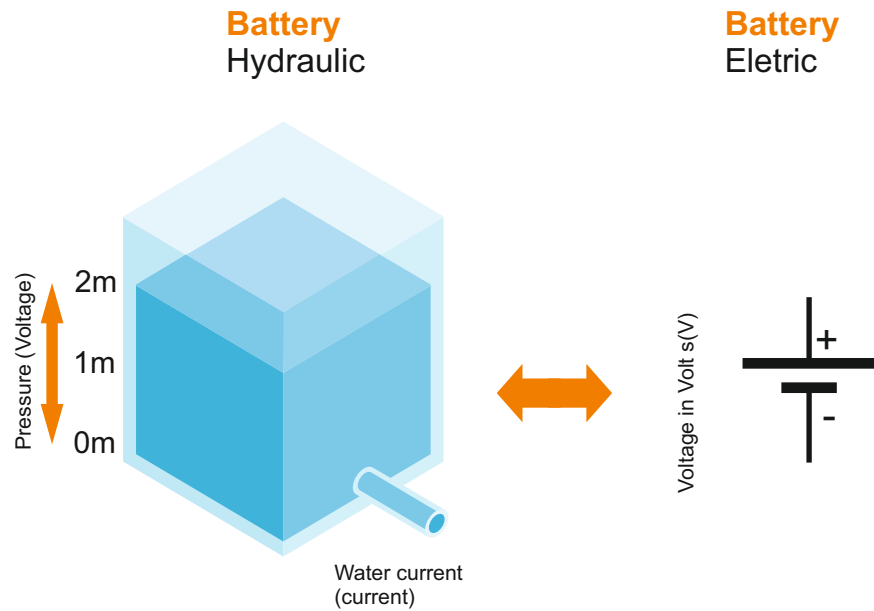Pressure versus Voltage Hydraulic versus Electric




Connections


Connecting Elements Hydraulic

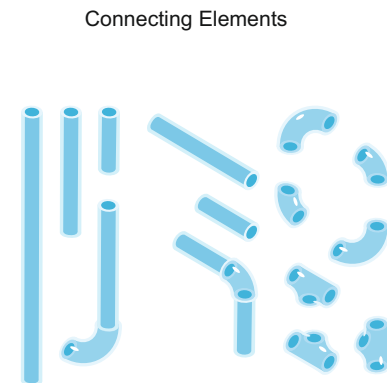


Connecting Elements Electric

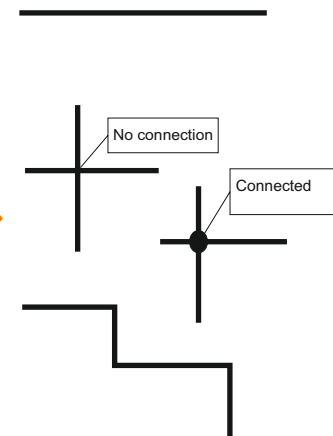

The Resistance

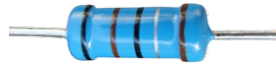

Resistance Hydraulic

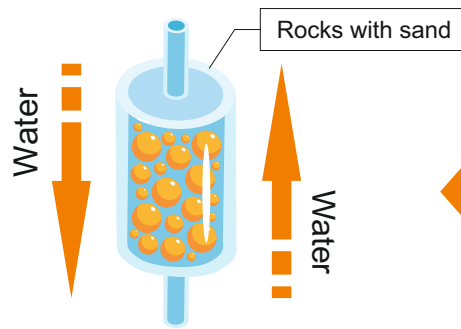

The water can flow in both directions


Resistance Electric



resistance in Ohms (Ω)

Small and large resistance

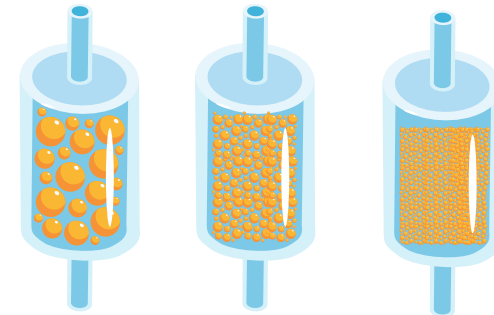Resistance Hydraulic - Are all the resistors equal?




Which one has the largest resistance?



Diode




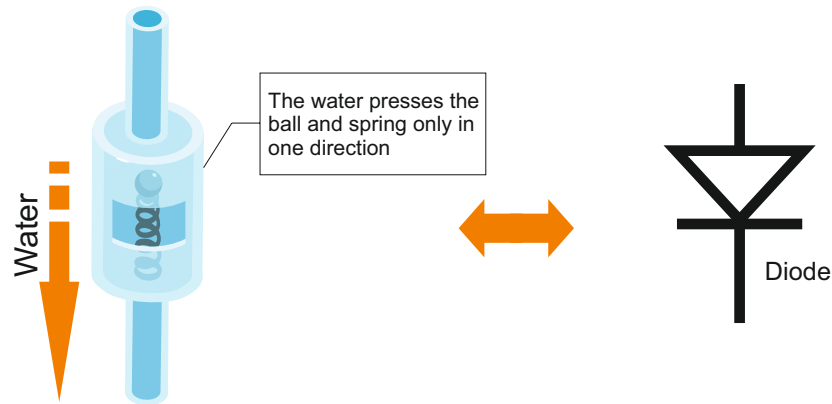Directional Barrier
How can I determine
the water direction?




Directional Barrier
Electric

LED

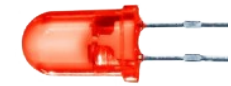

Directional Barrier
And a LED???

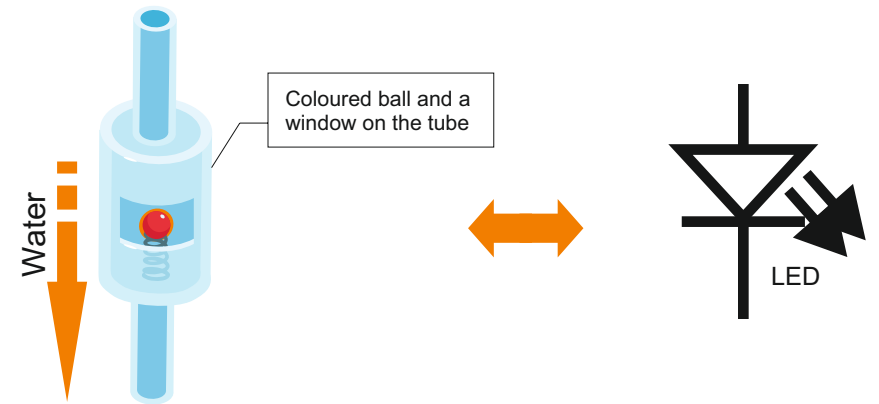

Directional Barrier
Electric




The Capacitor




Pression Memory

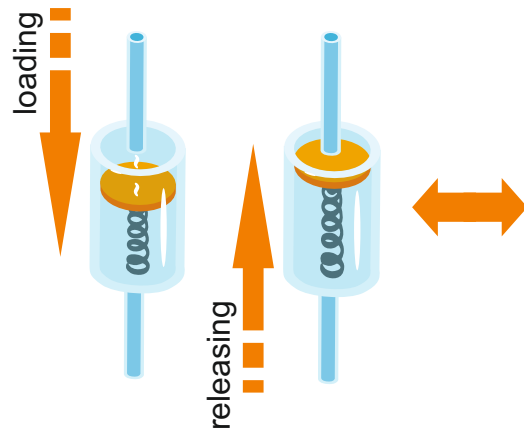The pression will be loaded and then released



Voltage Memory

Electric

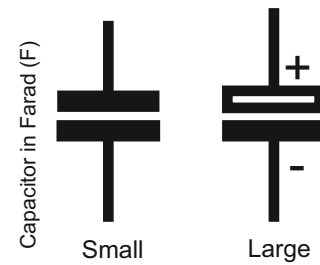


The Button





Water Barrier

Water On/Off

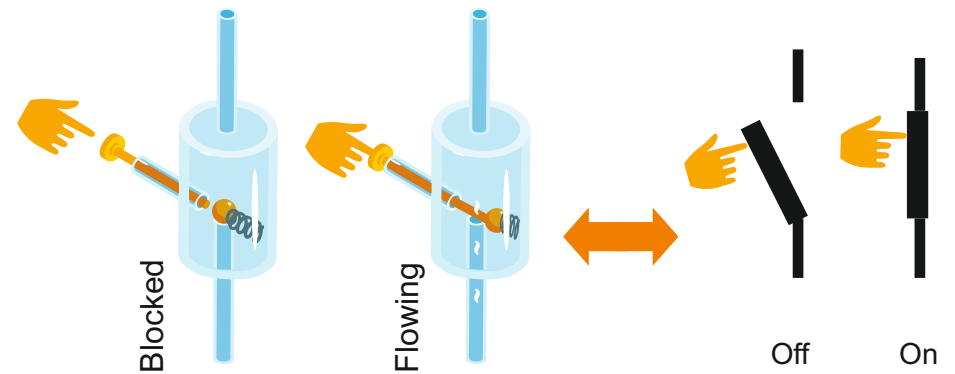

The Transistor

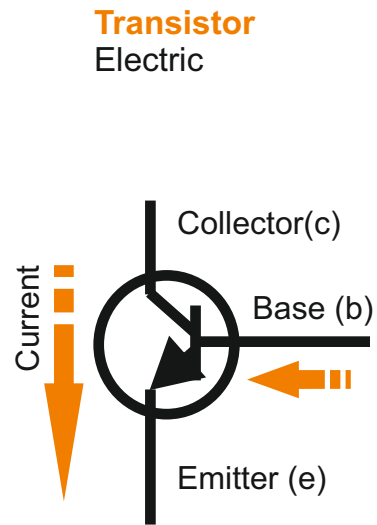
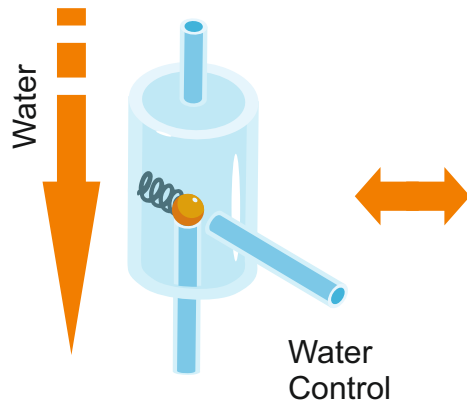
Water Barrier
Water On/Off
Automatically???



The "Mr" NPN Bc549





Transistor
Electric

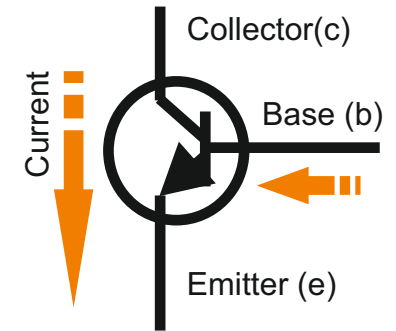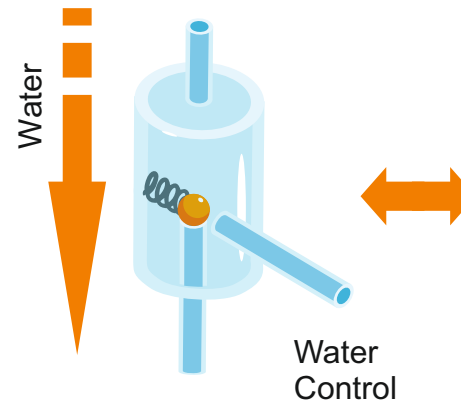

Take a Note:




WARNING!
This can be dangerous

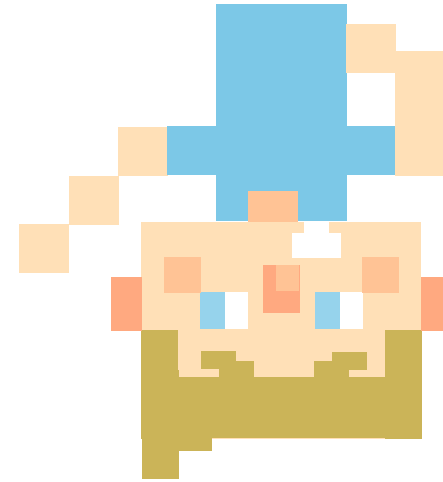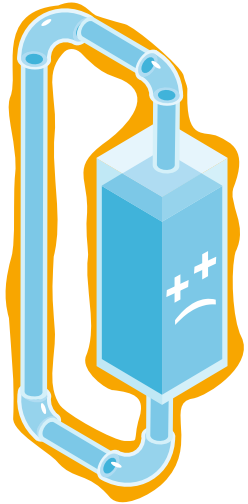

Experiment 01

Theorie: Turning on a LED

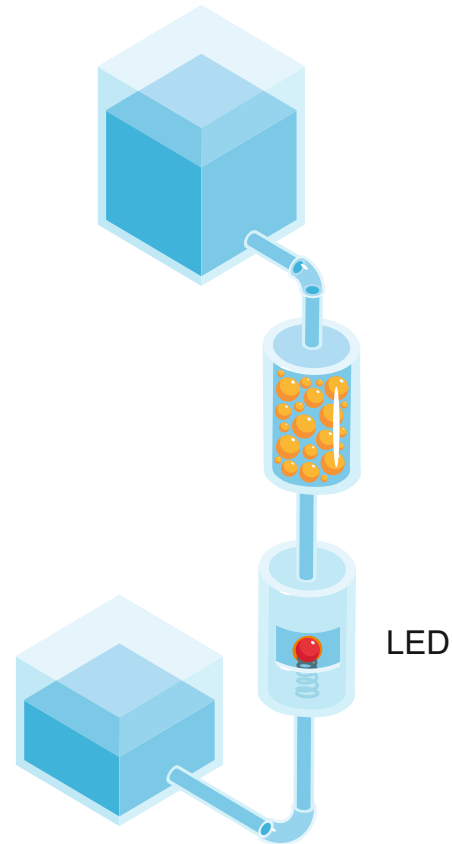

Questions:

What happens when the LED is connected differently?

What happens when we don't use the resistor?

What happens when the pressure is too high?

What happens when the resistance is too small?


What happens when the resistance is too large?

Questions, questions and more questions...



Experiment 01

Practic: Turning on a LED

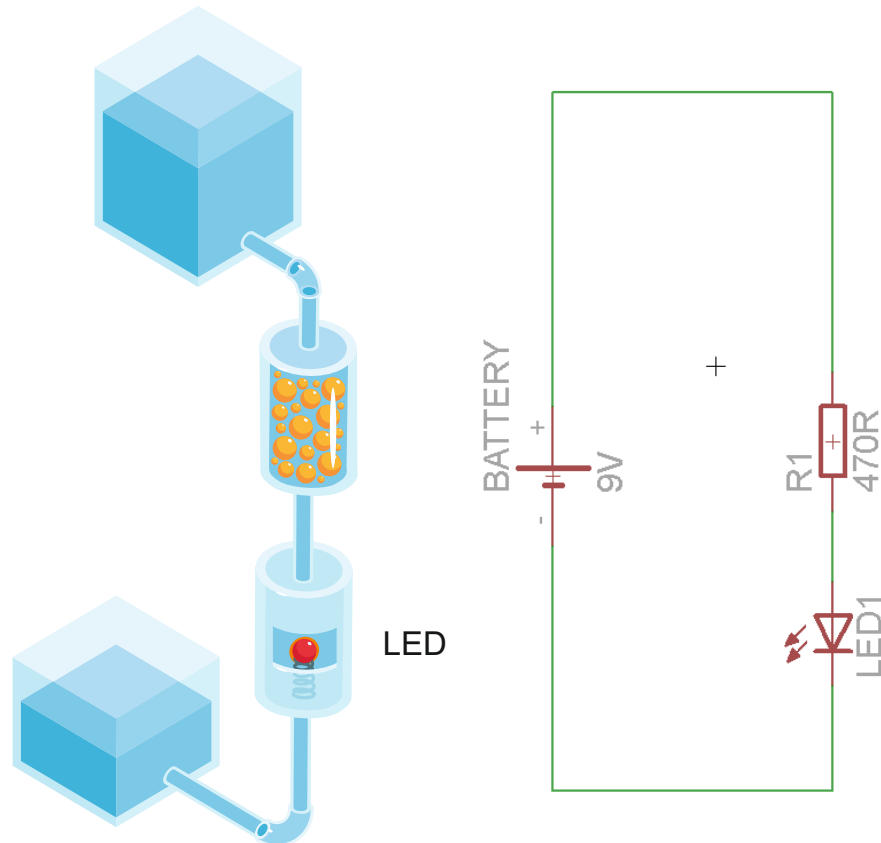

Task $V = R \cdot I$

Building the circuit.

Did it work?

The turn the LED orientation.

Change the resistance from 470 Ohms to 1000 Ohms.

What happened? Why are we using 470 Ohms?

Is it clear to you, that the LED depends on both the current and the voltage?

Then we write that:

- The voltage from the Battery cannot be changed
- The Battery we buy already assembled in the supermarket.
- The LED we also buy ready. (The "spring force" is known by the manufacturer, and its value is measured in current - A)

The voltage and the current we know, GREAT! Now only the resistance is missing.

So it comes that:



The resistance of R1 = Voltage (in V) / Current (in A)

Try to do it yourself :-). If it is not easy, you can use a calculator.





Test

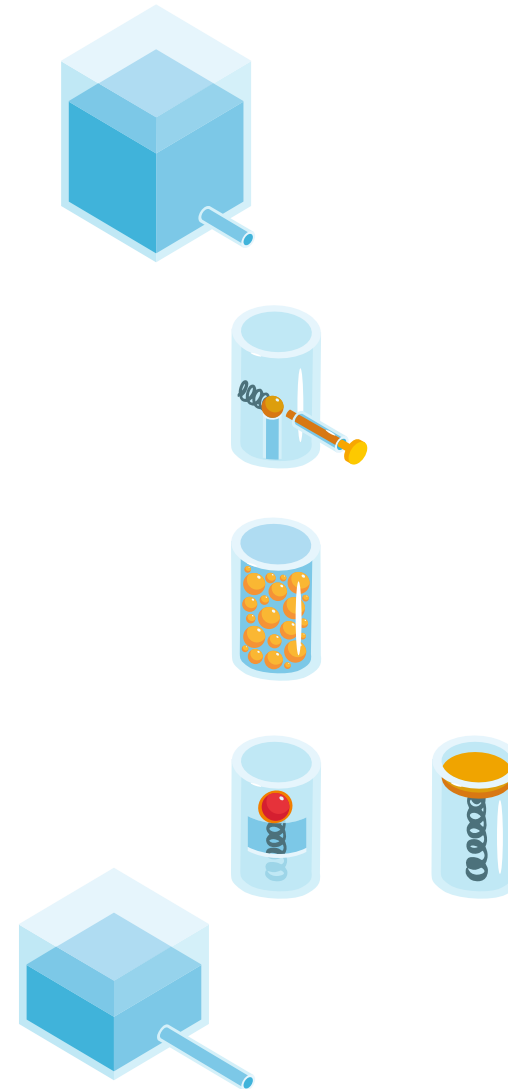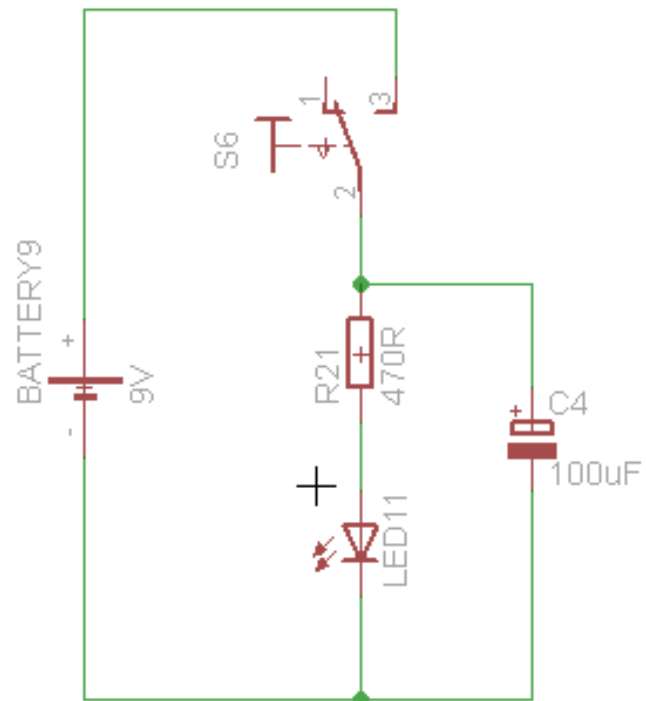
Can you make the hydraulic model of the following circuit?
And say what this circuit makes?





Is there a difference here?

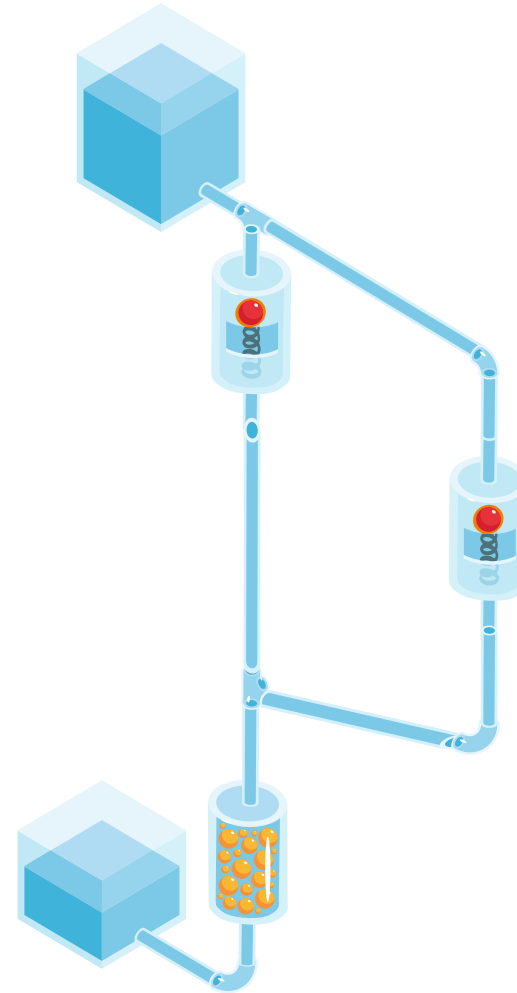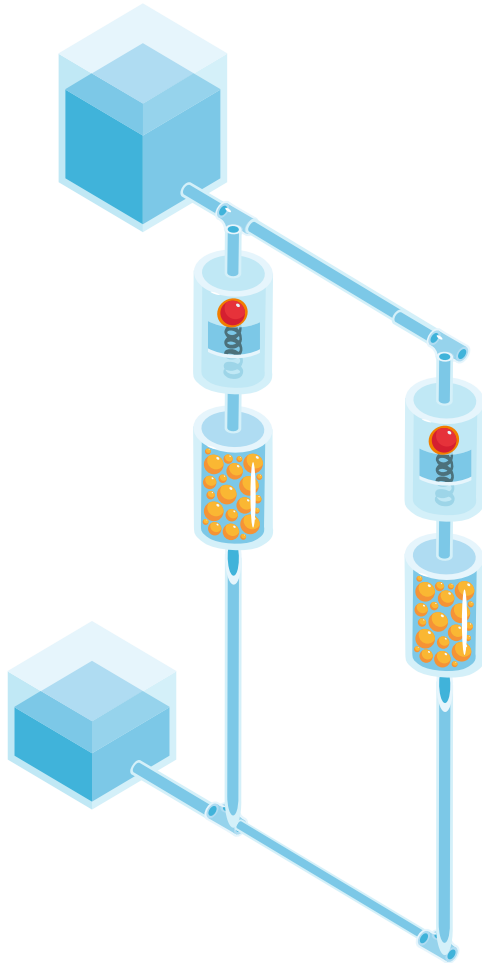

And what makes this circuit?


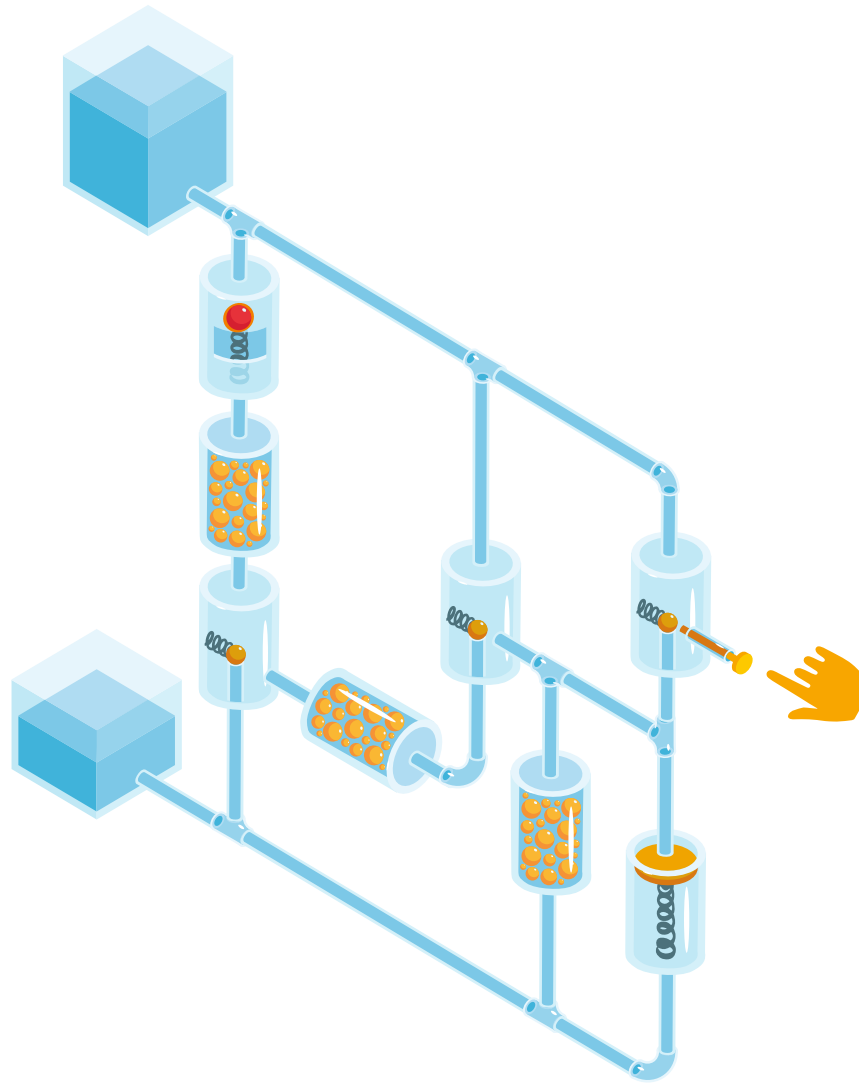


Timer

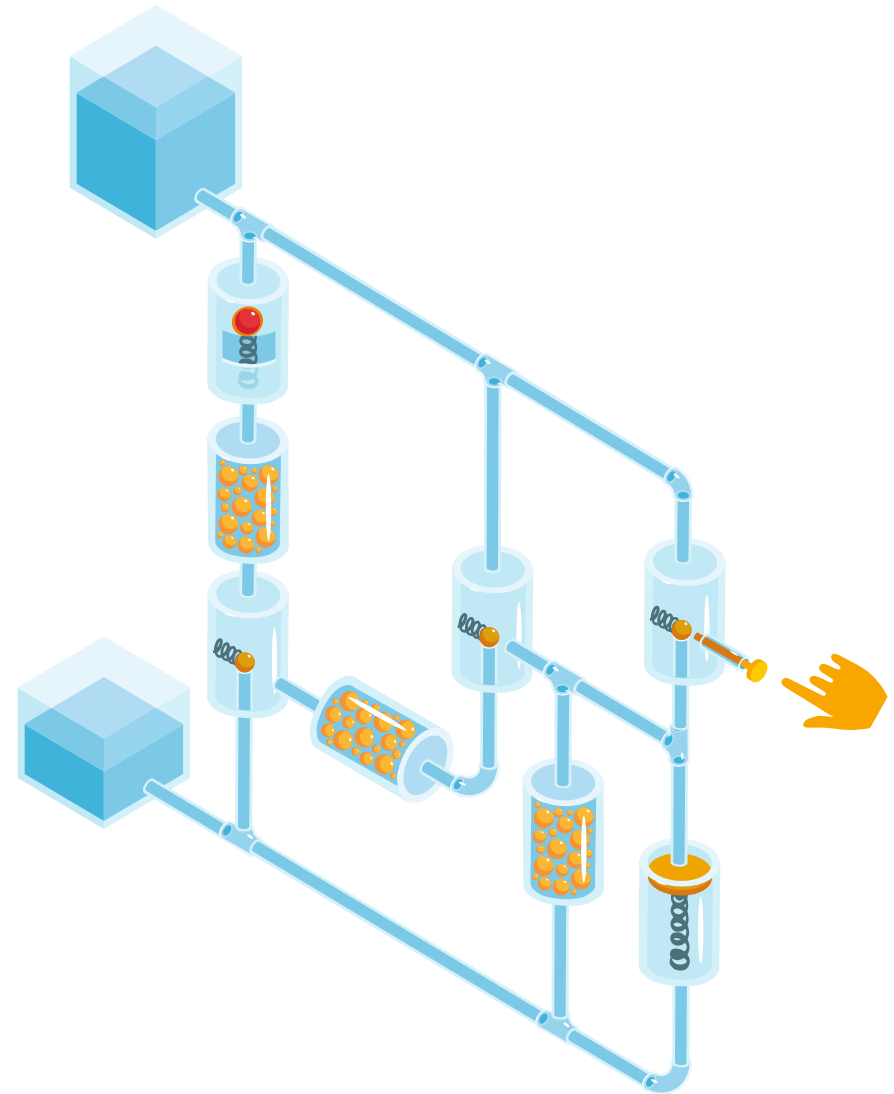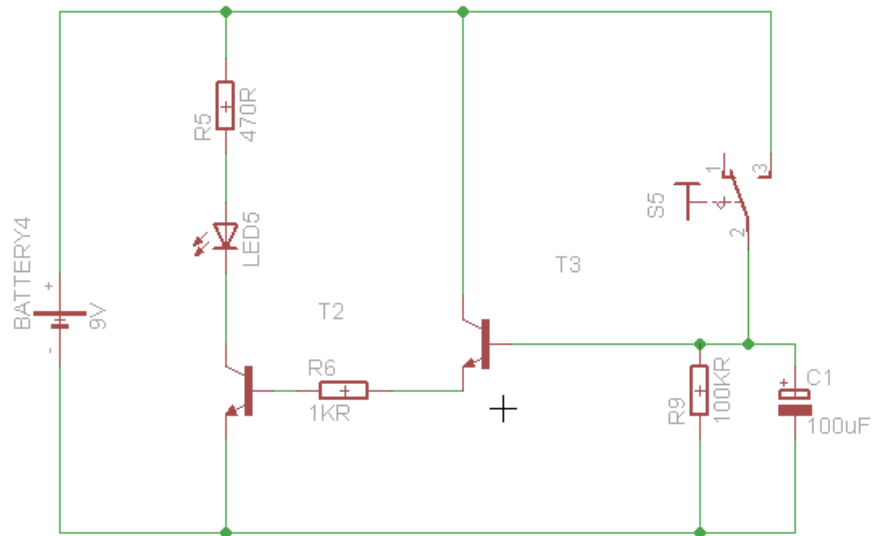



The Transistor

Can you finish it?
And explain?

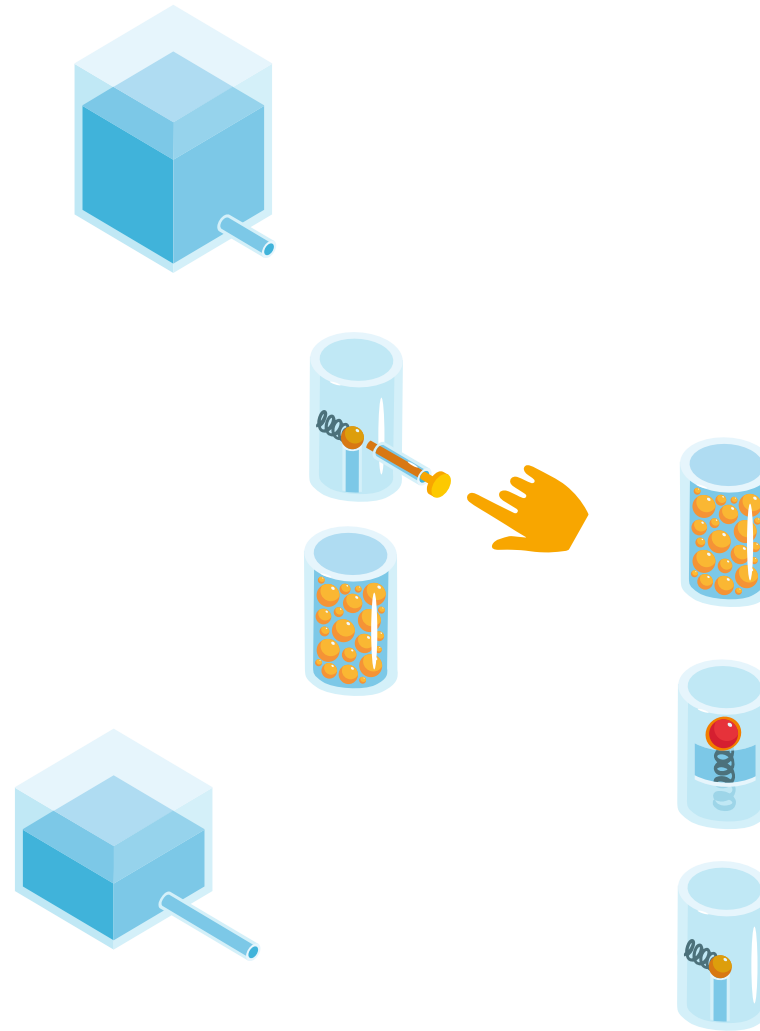
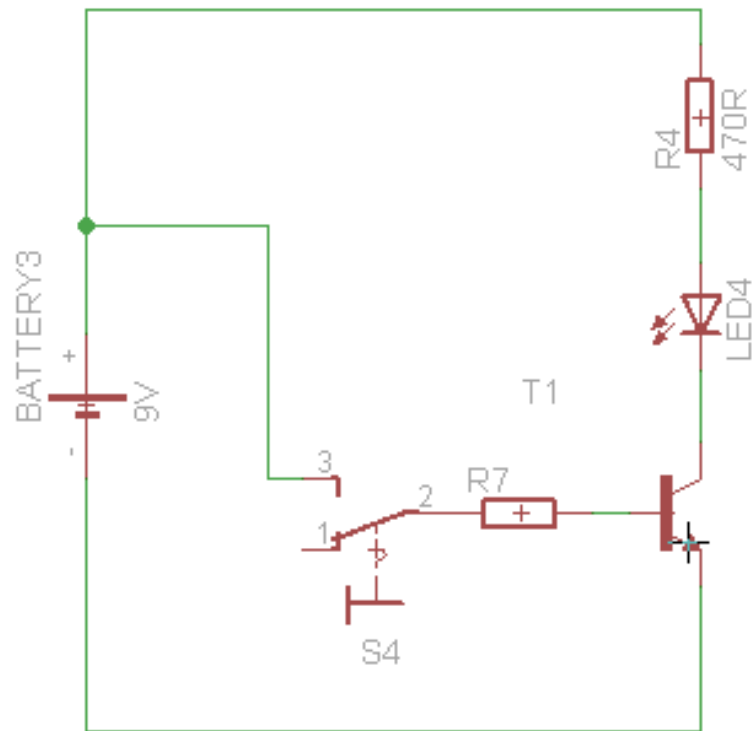


Watering flowers detector



Can you finish it?
And explain it?

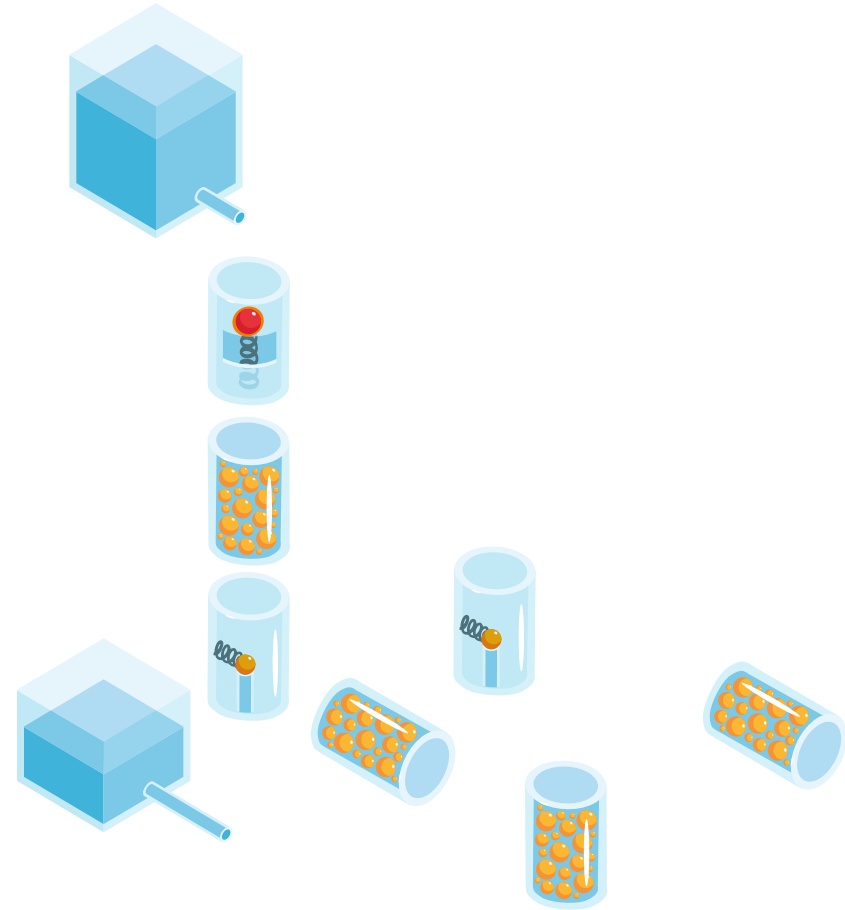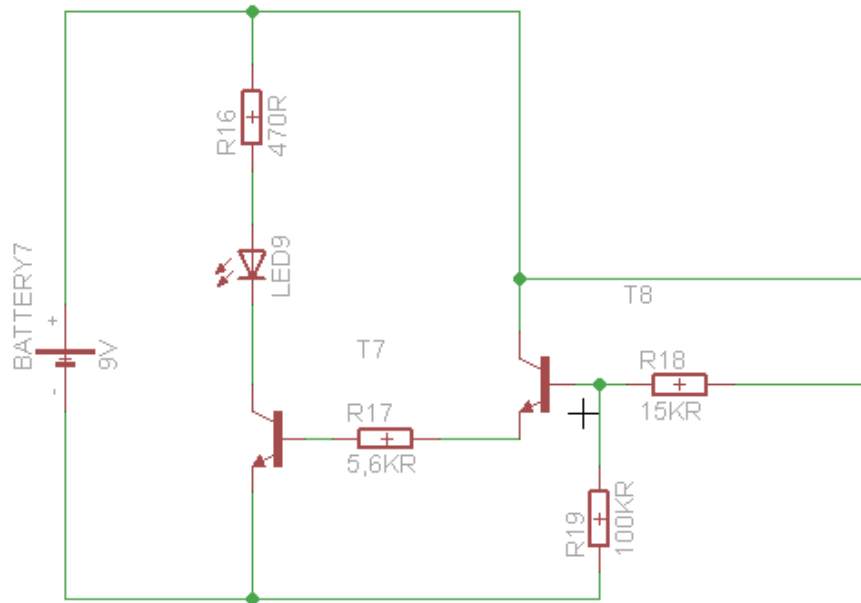


LED On

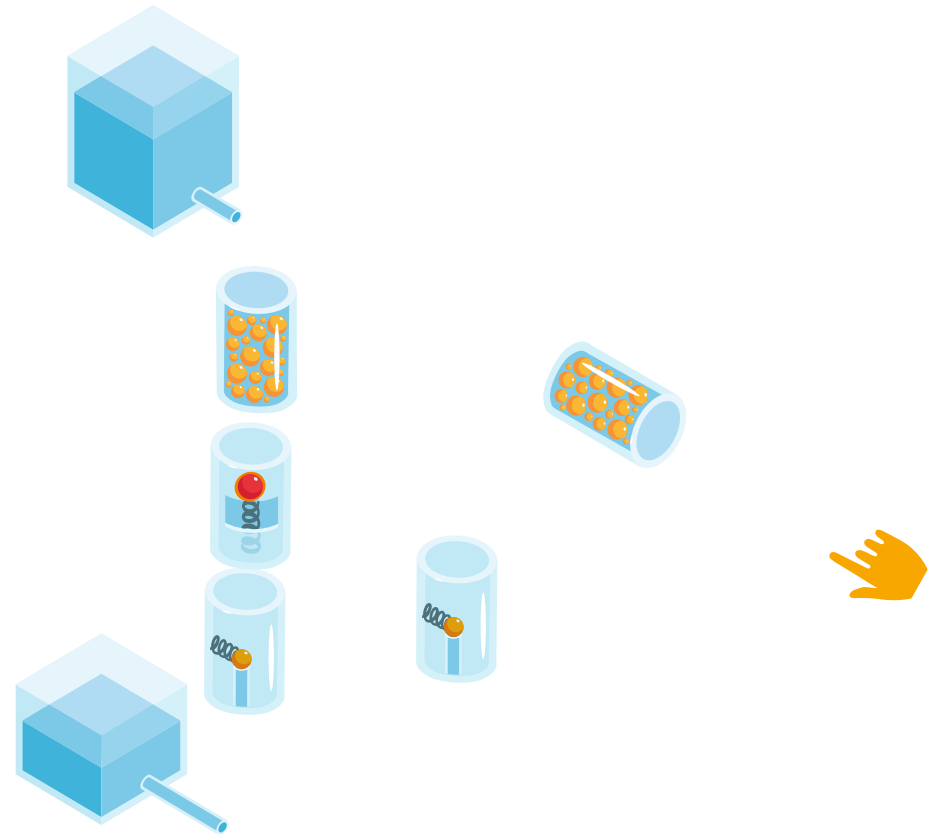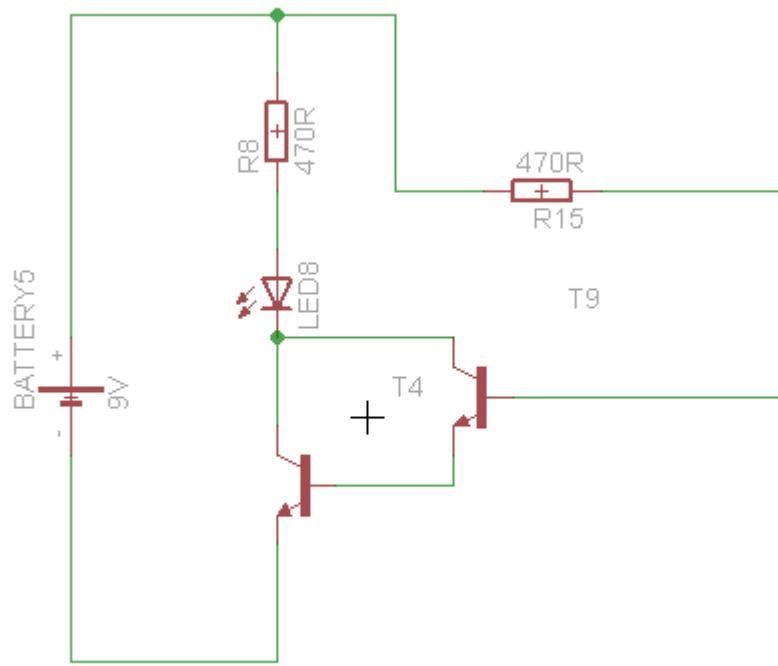


LED Off

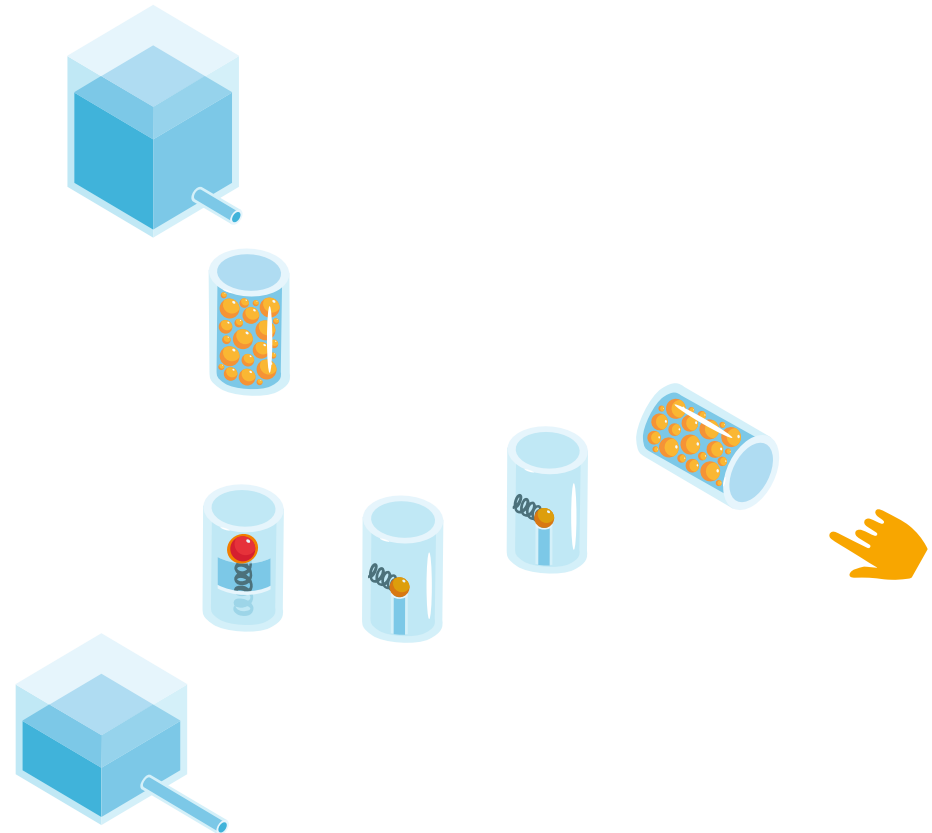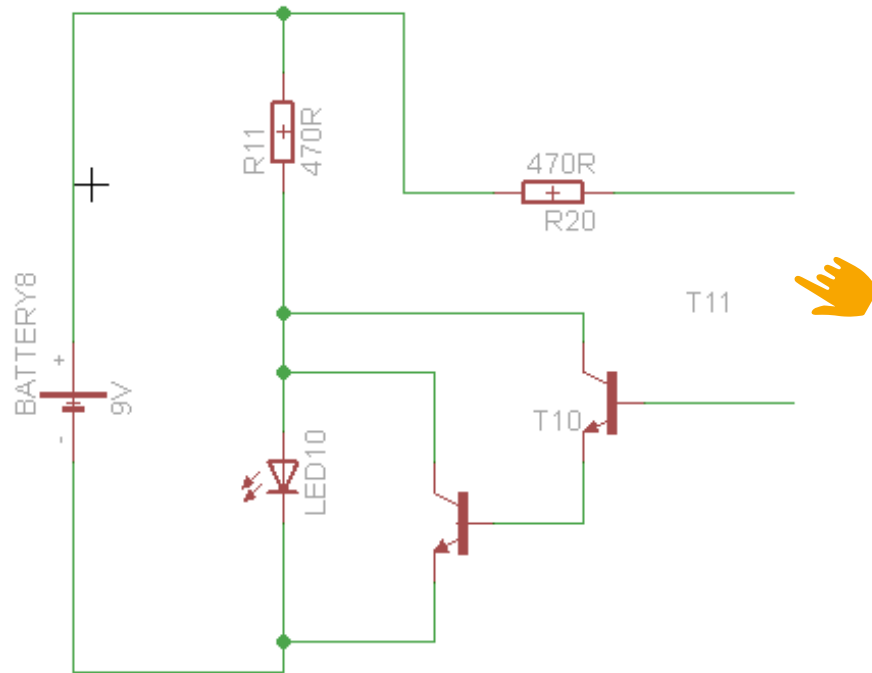

Blinker

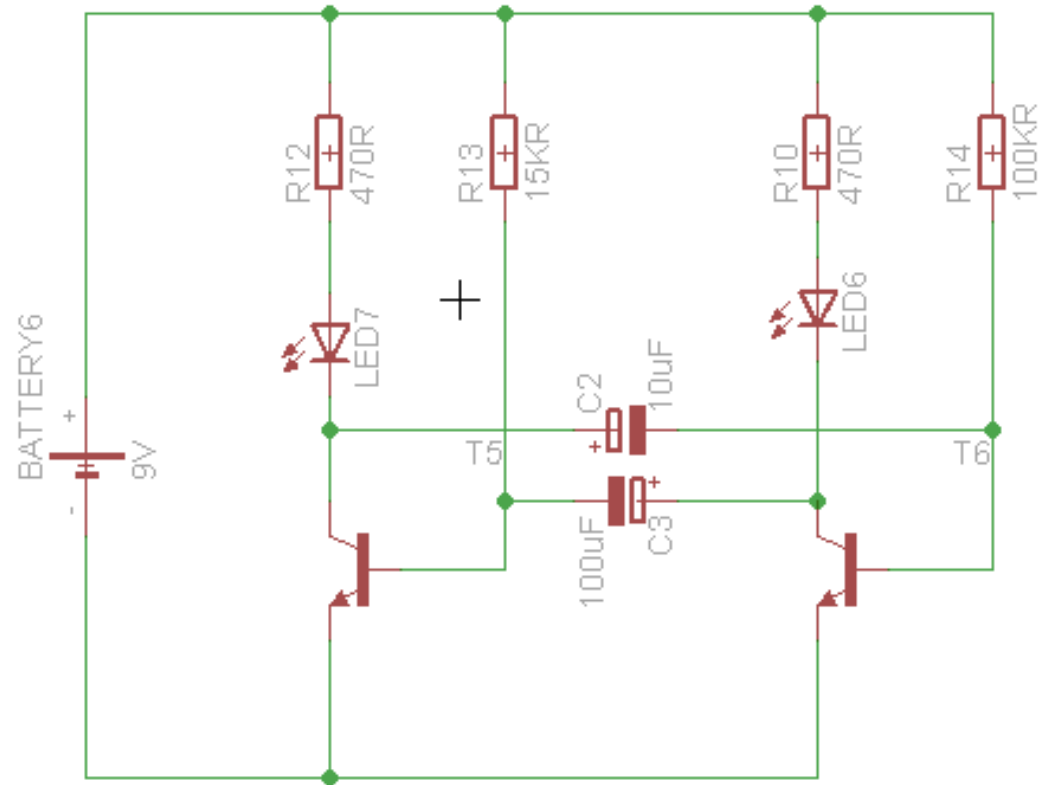

Resistors

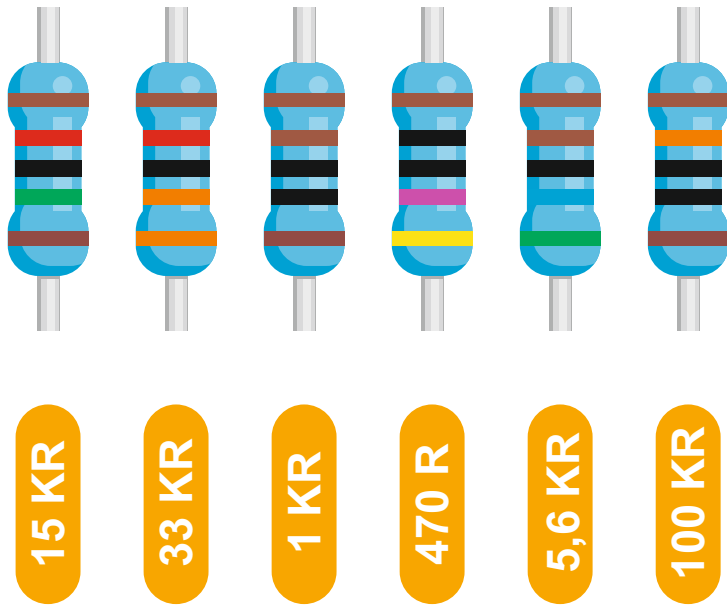

| COLOR | 1 ST BAND | 2 ND BAND | 3 RD BAND | MULTIPLIER | TOLERANCE |
|--------|----------------------|----------------------|----------------------|---------------|-----------------|
| Black | 0 | 0 | 0 | 1 Ω | |
| Brown | 1 | 1 | 1 | 10 Ω | \pm 1% (F) |
| Red | 2 | 2 | 2 | 100 Ω | \pm 2% (G) |
| Orange | 3 | 3 | 3 | 1K Ω | |
| Yellow | 4 | 4 | 4 | 10K Ω | |
| Green | 5 | 5 | 5 | 100K Ω | \pm 0.5% (D) |
| Blue | 6 | 6 | 6 | 1M Ω | \pm 0.25% (C) |
| Violet | 7 | 7 | 7 | 10M Ω | \pm 0.10% (B) |
| Grey | 8 | 8 | 8 | | \pm 0.05% |
| White | 9 | 9 | 9 | | |
| Gold | | | | 0.1 Ω | \pm 5% (J) |
| Silver | | | | 0.01 Ω | \pm 10% (K) |

