



# Basic Electronics Series

## Ohm's Law and Watt's Law



# Ohm's Law Basics

- In an electric circuit, the three primary factors, voltage, current, and resistance are related through a concept known as Ohm's Law.
- Ohm's Law holds that the current flowing in a circuit is equal to the voltage applied to that circuit divided by the resistance through the circuit.



# Ohm's Law Basics

- There are three forms in which Ohm's Law can be expressed, all of which are simple mathematical rearrangements of the basic rule:
  - Current equals voltage divided by resistance;
  - Resistance equals voltage divided by current; and
  - Voltage equals current multiplied by resistance.



# Ohm's Law Basics

- Formulaically, we use specific symbols to represent the basic values:
  - I is used for current;
  - E (and sometimes V) is used for voltage; and
  - R is used for resistance.
- These symbols are used in formulas, but are *not* always the abbreviations commonly used for these values.



# Ohm's Law Basics

- The unit of measure of current is the *ampere*, abbreviated *A*.
- The unit of measure of voltage is the *volt*, abbreviated *V*.
- The unit of measure of resistance is the *ohm*, abbreviated  $\Omega$ .
- Each of these values is measured with a specific instrument or meter.



# Ohm's Law Basics

- The units of measure may be modified to easily express much larger or smaller units...
  - 1 milliampere (mA) equals 0.001 amperes;
  - 1 microampere ( $\mu$ A) equals 0.000001 milliamperes;
  - 1 kilovolt (kV) equals 1,000 volts;
  - 1 millivolt (mV) equals 0.001 volts;
  - 1 microvolt ( $\mu$ V) equals 0.000001 volts;
  - 1 kilohm equals 1,000 ohms; and
  - 1 megohm equals 1,000,000 ohms.



# Ohm's Law Basics

- Current, in amperes, is measured using an *ammeter*, which is connected in series with the circuit under test.
- Voltage, in volts, is measured using a *voltmeter*, which is connected in parallel to the circuit segment under test.
- Resistance, in ohms, is measured with an *ohmmeter*, which is *always* connected to a de-energized circuit or component.



# Ohm's Law Equations


- The three forms of Ohm's Law, stated using the symbolic representations for the values, are as follows:
  - $I = E / R$
  - $R = E / I$
  - $E = I \times R$
- If we know two of the values, we can easily calculate the third value.





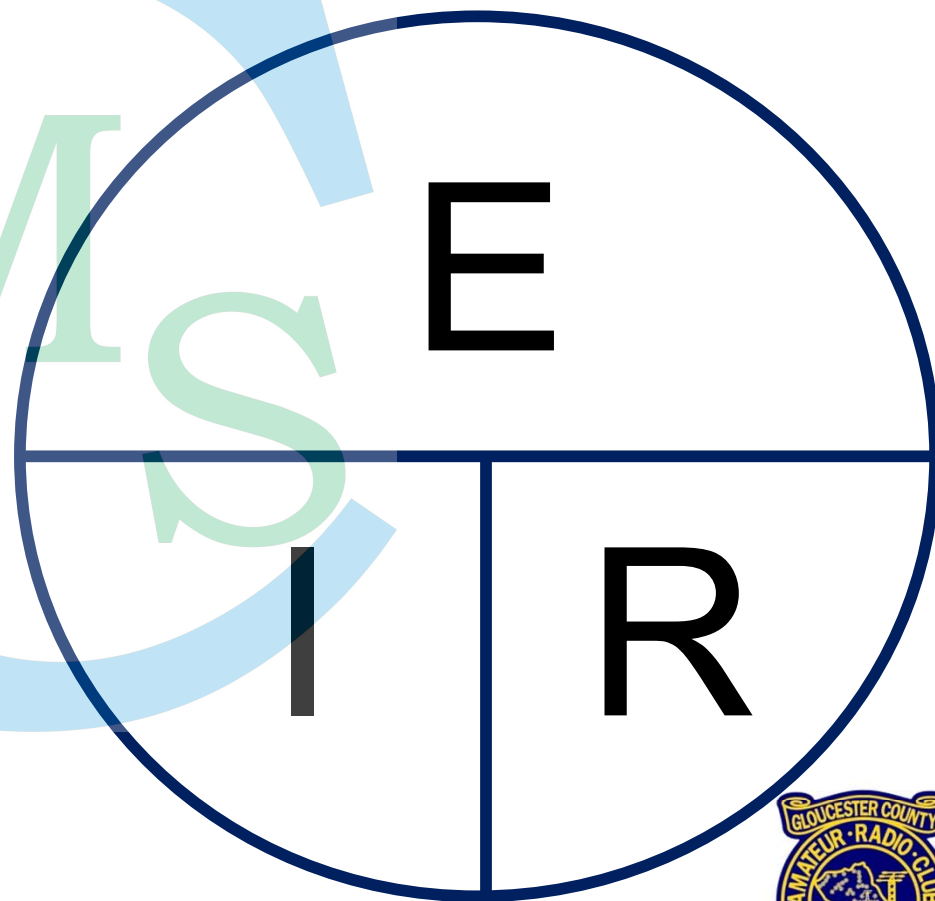
# Ohm's Law Wheel

- The Ohm's Law wheel helps us to remember the equations by showing the equation parts in a graphical form, and the graphic gives us the equations if we cover one part.



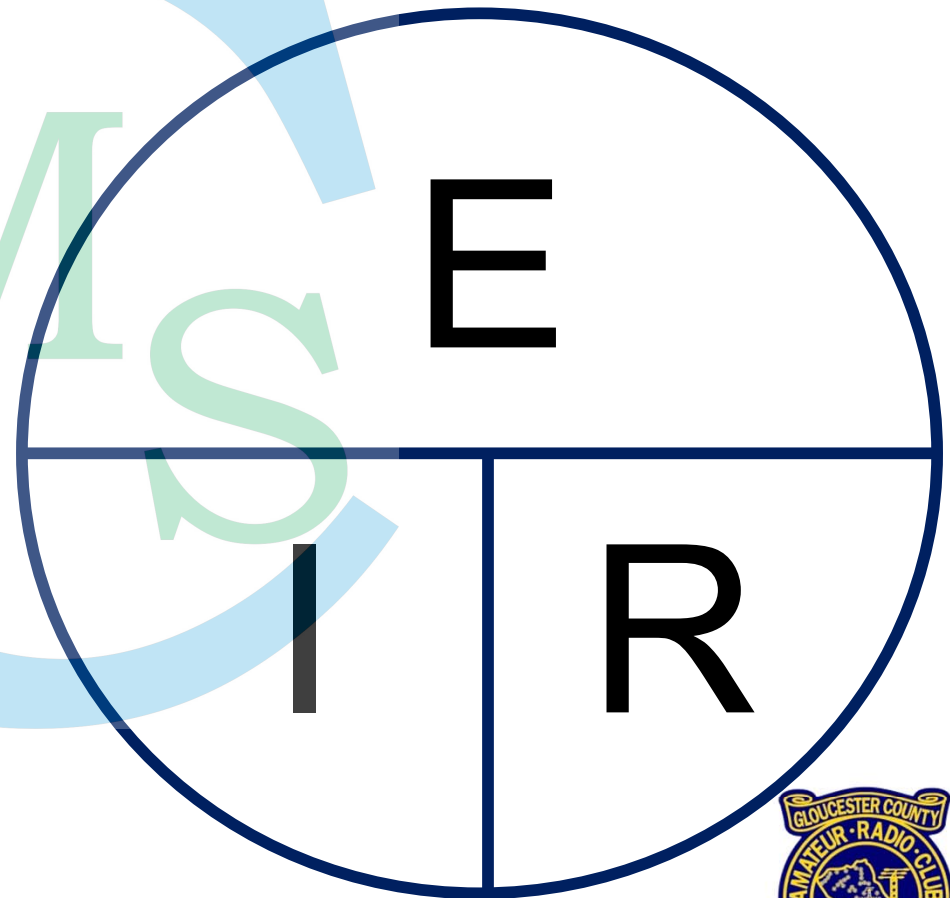
# Ohm's Law Wheel

- If we cover the part that we need to solve for, the remaining parts will then be displayed in the form of the appropriate equation for finding the missing part.


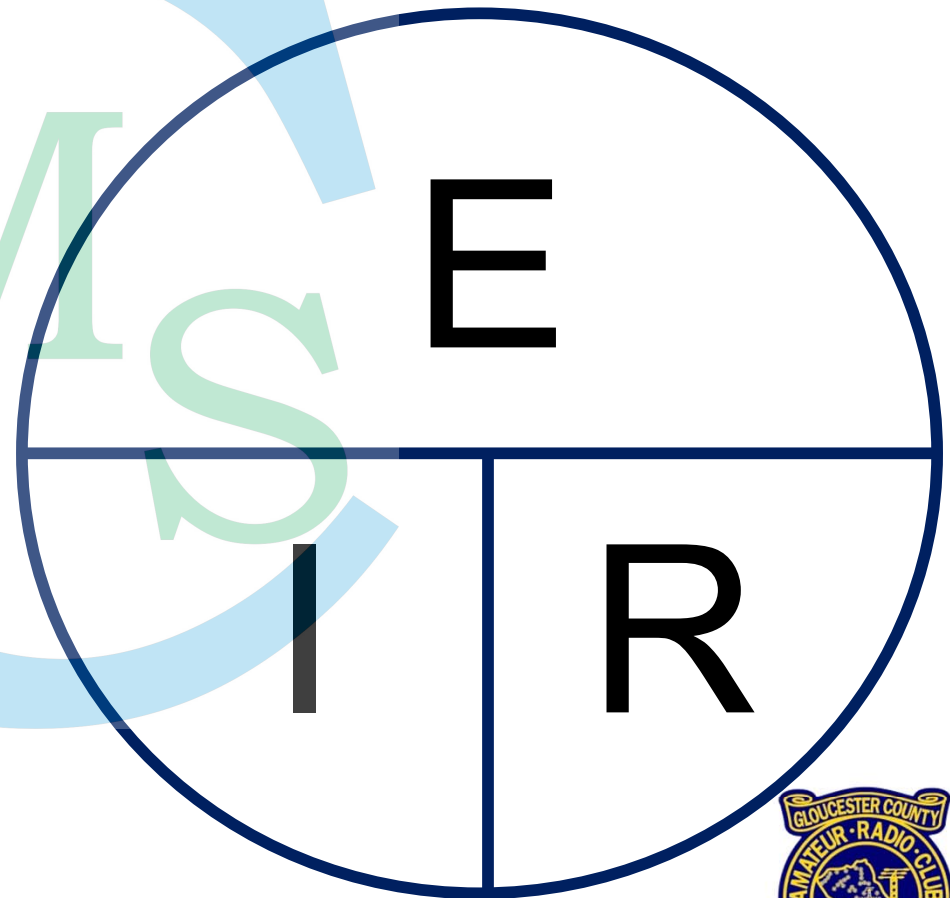
# Ohm's Law Wheel

- Cover the E and get I next to R ( $E = I \times R$ ).
- Cover the I and get E over R ( $I = E / R$ ).
- Cover the R and get E over I ( $R = E / I$ ).
- This is a handy tool that is easy to use and to remember.



# Ohm's Law Example 1

- Solve for the current in milliamperes for a circuit where 12 volts applied across a resistance of 470 ohms...
  - $I = E / R$ 
    - $I = 12V / 470\Omega$
    - $I = 0.02553A$
    - $I = 25.53mA$



# Ohm's Law Example 2

- Find the resistance in a circuit where a current of 275 milliamperes flows when 7.5 volts are applied.
  - $R = E / I$
  - $R = 7.5V / 275mA$
  - $R = 7.5V / 0.275A$
  - $R = 27.27\overline{27}\Omega$



# Ohm's Law Example 3

- What is the voltage applied in a circuit in which 1795 milliamperes is flowing through a resistance of 2.7k $\Omega$ ?
  - $E = I \times R$
  - $E = 1795\text{mA} \times 2.7\text{k}\Omega$
  - $E = 1.795\text{A} \times 2700\Omega$
  - $E = 4,8465.5\text{V}$



# Power

- When a current flows through a resistive circuit, work is done in that the current flow through the resistor causes the resistor to radiate some amount of heat.
- The work that is done can be measured, and the rate at which the work is done is known as *power*.
- Power, in general, is abbreviated  $P$ .



# Power

- Power is a function of voltage and current, and can be calculated using the equation

$$\text{POWER} = \text{CURRENT} \times \text{VOLTAGE.}$$

- As before, we can symbolize the current and voltage to give us  $\text{POWER} = I \times E$ .
- This equation is a representation of Watt's Law.
- The unit of measure of power is the *watt*.
- One watt is the amount of power consumed when a current of one ampere is moved by voltage of one volt.





# Power

- Also as before, the watt is often expressed in other forms to show exceptionally large or very small levels of power:
  - 1 milliwatt (mW) equals 0.001 watts
  - 1 microwatt ( $\mu$ W) equals 0.000001 watts
  - 1 kilowatt (kW) equals 1,000 watts
  - 1 megawatt (MW) equals 1,000,000 watts




# Power

- The watt is abbreviated  $W$  and is measured by a device called a *wattmeter*.
- Also as before, the equation for power can be rearranged mathematically as follows:
  - $P = I \times E$
  - $I = P / E$
  - $E = P / I$
- As before, we have a memory aid for Watt's Law that is very familiar by now.


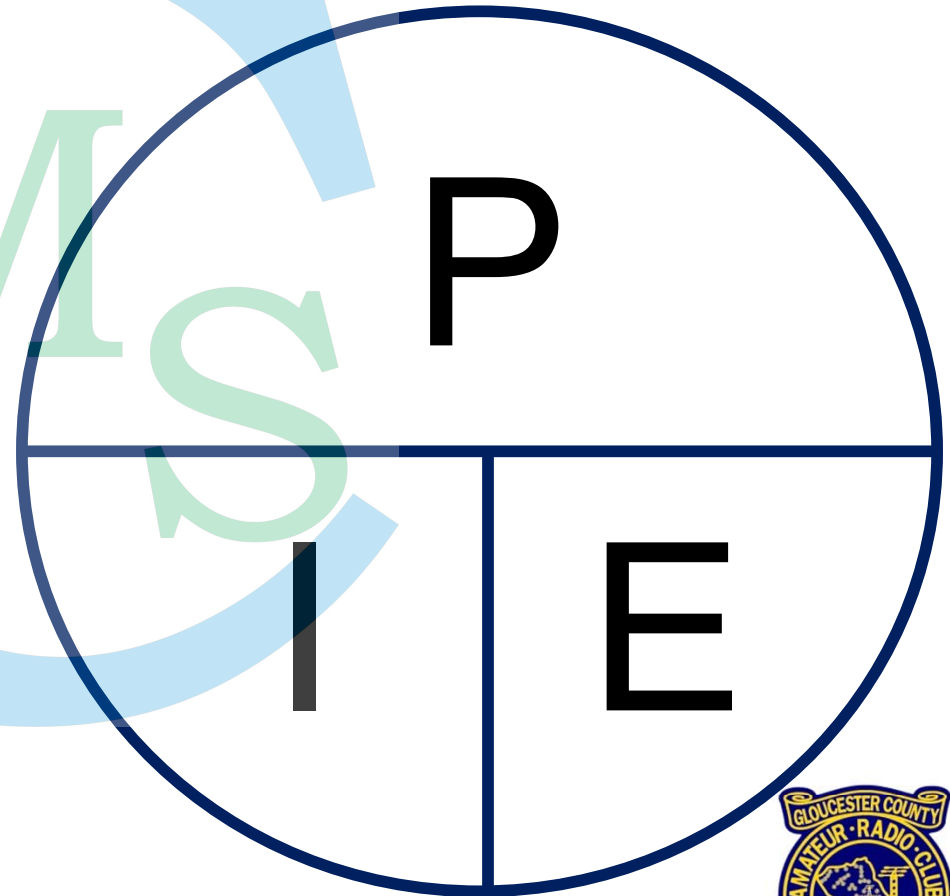
# Watt's Law Wheel

- As with the Ohm's Law wheel, the Watt's Law wheel will give us the equation for any of the equation's parts by covering the part for which we need to solve.




# Power

- Sometimes, we will have to solve for power having been given the resistance instead of either the current or the voltage.
- Some additional useful rearrangements of the equations are:
  - $P = I^2 \times R$  ( $P = I \times E$ , and  $E = I \times R$ , so  $P = I \times I \times R$ )
  - $P = E^2 / R$  ( $P = I \times E$ , and  $I = E / R$ , so  $P = E \times (E/R)$ )
- Other forms of Watt's Law equations exist


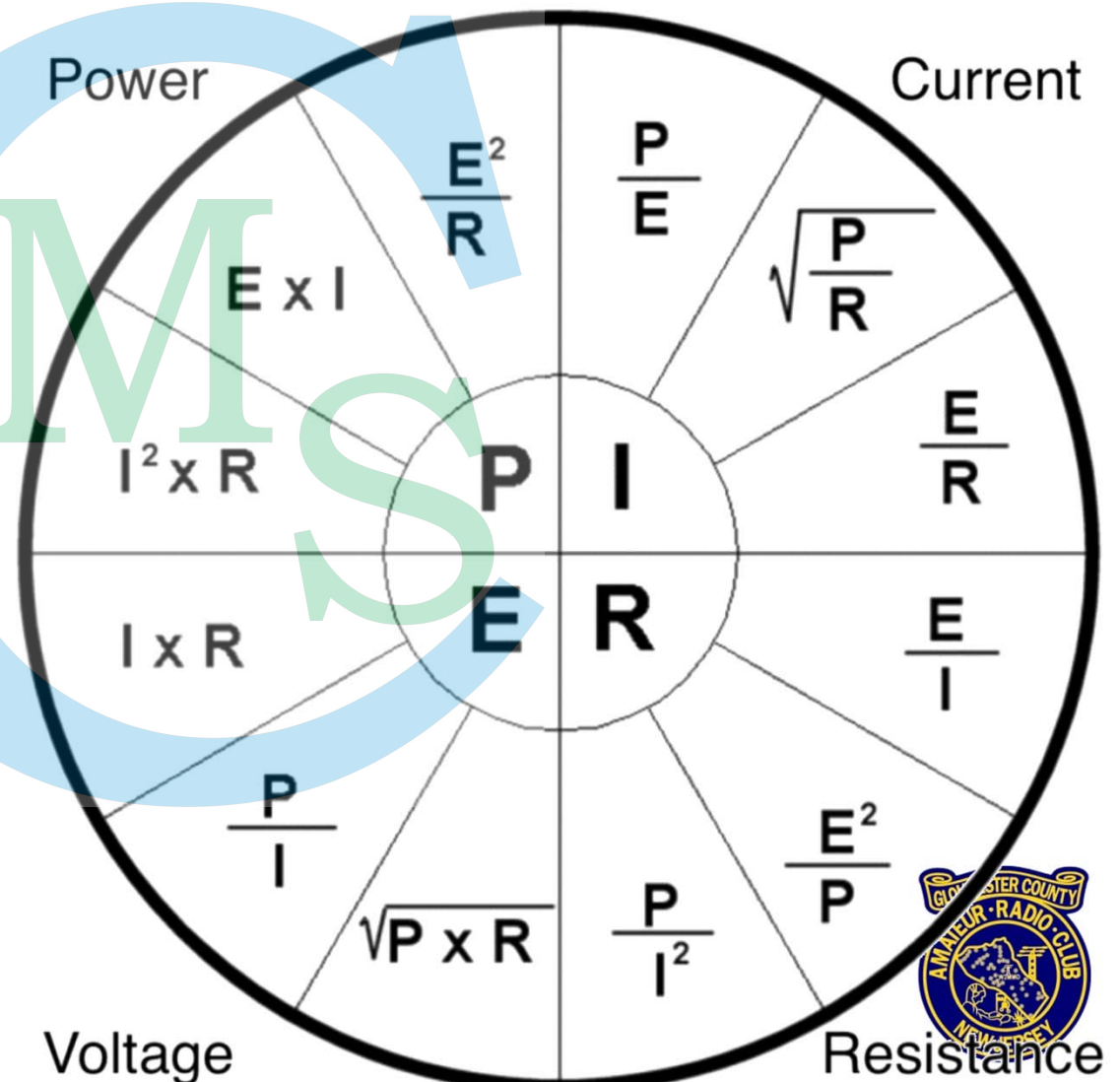
# Ohm's & Watt's Laws Wheel

- This combined wheel shows all of the possible forms of the Ohm's Law and Watt's Law equations, broken apart in quadrants by the factor for which we need to solve.



# Watt's Law Example 1

- How much power in kilowatts is consumed in a circuit in which 21 amperes flows under a voltage of 100 volts?
  - $P = I \times E$
  - $P = 21A \times 100V$
  - $P = 2100W$
  - $P = 2.1kW$



# Watt's Law Example 2

- How much current is flowing in a 250V circuit in which 7.5MW is consumed?
  - $I = P / E$
  - $I = 7.5\text{MW} / 250\text{V}$
  - $I = 7,500,000\text{W} / 250\text{V}$
  - $I = 30,000\text{A}$



# Watt's Law Example 3

- What is the voltage of a circuit in which 48 watts are consumed and a current of 8 amperes is flowing?
- $V = P / I$
- $V = 48W / 8A$
- $V = 6V$





# Watt's Law Example 4

- What is the milliwatt power consumption of a 15V circuit with a resistance of 1.8kΩ?
  - $P = E^2 / R$
  - $P = 15V^2 / 1.8k\Omega$
  - $P = (15 \times 15) / 1800$
  - $P = 225 / 1800$
  - $P = 0.125W$
  - $P = 125mW$



# Watt's Law Example 5

- How many kilowatts are consumed in a circuit having  $470\Omega$  resistance and a current flow of  $375\text{mA}$ ?
  - $P = I^2 \times R$
  - $P = 375\text{mA}^2 \times 470\Omega$
  - $P = 0.375 \times 0.375 \times 470$
  - $P = 66.09375\text{W}$
  - $P = 0.0661\text{kW}$



# AC Variations of Watt's Law

- Up to this point, all of the examples that we have seen involved DC circuits.
- In order to understand these concepts when AC is involved, we must first understand the DC equivalent of an AC voltage.
- As DC flows through a resistance, a given amount of measurable heat is produced.
- We are interested in that amount of heat



# AC Variations of Watt's Law

- While DC is constant and continuous, AC varies continually between some positive peak and some negative peak.
- In an AC sine wave, the average voltage of this wave is zero, as the wave spends as much time above zero as it does below zero, and in the same proportions (pattern).
- Thus, we need a different way to measure AC voltages.



# AC Variations of Watt's Law

- The solution is the AC voltmeter, which measures a property of AC known as its *Root Mean Square*, or *RMS* voltage.
- This is the AC voltage that will produce the same heating effect as the equivalent DC voltage in a resistance.
- RMS voltage is equal to 70.7% of the peak voltage of an AC sine wave.



# AC Variations of Watt's Law

- The full AC sine wave, as stated earlier, swings both positive and negative across the zero line, and is thus called a *peak-to-peak voltage*, or  $V_{P-P}$ .
- RMS voltage is calculated using only one half of the full peak-to-peak sine wave, or the *peak voltage* ( $V_P$ ).
- Thus, the formula for RMS voltage becomes

$$V_{RMS} = V_P \times 0.707$$



# AC Variations of Watt's Law

- In certain disciplines, such as in amateur radio, we are interested in the power represented by an AC signal waveform, possibly as seen on an oscilloscope.
- In radio, we call this waveform the signal's envelope, and we are interested in the *peak envelope power*, or *PEP*.
- PEP is calculated by the formula

$$PEP = V_{RMS}^2 / R$$



# AC Variations of Watt's Law

- In that formula,  $PEP = V_{RMS}^2 / R$ , the R represents the load resistance, which is normally the characteristic impedance of the radio's antenna system, usually shown as  $Z_L$ .
- In order to calculate the PEP, two factors must be known...
  - The voltage; and
  - The load impedance (resistance).





# AC Variations of Watt's Law

- The voltage may be given in one of three forms, two of which will require some manipulation in order to solve the equation:
  - $V_{P-P}$  or peak-to-peak voltage, which we must first convert to peak voltage ( $V_P$ ) and then to RMS voltage ( $V_{RMS}$ );
  - $V_P$ , which must be converted to  $V_{RMS}$ ; or
  - $V_{RMS}$ , which is ready to use in the equation.



# PEP Example 1

- Calculate the PEP of a waveform having a peak-to-peak voltage of 140 volts and a load impedance of 50Ω.
  - $PEP = V_{RMS}^2 / L_Z$  or  $V_{RMS}^2 / L_Z$
  - $PEP = ((140 / 2) \times 0.707)^2 / 50$
  - $PEP = (70 \times 0.707)^2 / 50$
  - $PEP = 49.49^2 / 50$
  - $PEP = 2,449.2601 / 50$
  - $PEP = 48.985202W$



# PEP Example 2

- What is the PEP of a waveform with a peak voltage of 120V and a load impedance of 75Ω?
  - $PEP = (120 \times 0.707)^2 / 75$
  - $PEP = 84.84^2 / 75$
  - $PEP = 7,197.8256 / 75$
  - $PEP = 95.971008W$



# PEP Example 3

- Find the PEP of a waveform having an RMS voltage of 70.7V and a load impedance of 50Ω.
  - $PEP = 70.7^2 / 50$
  - $PEP = 4998.49 / 50$
  - $PEP = 99.9698W$



# Summary

- While there are many applications for this information, it all remains simple arithmetic.
- The Ohm's Law and Watt's Law equations are easily drawn from the wheels if they are not remembered.
- The RMS voltage equation is most easily remembered by thinking of Boeing's first jet airliner, the 707...  $V_{RMS} = V_P \times 0.707$
- The PEP equation, while not really a part of Ohm's Law and Watts's Law, is a useful application of some of this information.



# Questions?

