 


## FLUXO DE DADOS “DATAPATH”

**1. Introdução:** É um conjunto de unidades funcionais destinadas à solução de problemas. O fluxo de dados contém unidades de multiplexagem, de armazenamento, de operações lógicas e aritméticas e opera sob gerência e supervisão de uma unidade de controle a qual gera sinais de controle através das microoperações sequenciais.

1.1 **DATAPATH** – A estrutura a seguir mostra o fluxo de dados e a unidade de controle.



## 2. PROCESSO DE PROJETO CIRCUITOS DIGITAIS

O processo de projeto de circuitos digitais pode ser descrito em duas fases sendo captura e conversão para circuito. Por exemplo:

Tipo de circuito	Captura	Conversão
<b>Combinatório</b>	Comportamento do circuito por: Equação booleana ou tabela da verdade	Converte o comportamento Para circuito.
<b>Seqüencial</b>	Comportamento do circuito por: equação de estados e saída (FSM)	Converte o comportamento Para circuito.
<b>RTL</b>	Comportamento do processador por: FSM de alto nível RTL	Converte o comportamento Para circuito.

## 3. MÉTODO DE PROJETO DO RTL.

O método de projeto RTL será realizado, conforme acima em quatro passos como descritos a seguir na tabela a seguir.

**Passo 1:** Processo de captura o qual descreve o comportamento do circuito através de um algoritmo com operações a serem realizadas dentro de uma seqüência desejada;

**Passo 2:** Definição do fluxo de dados;


**Passo 3:** Projeto do controlador ou unidade de controle;

**Passo 4:** Conversão do algoritmo em instruções da FSM de alto nível e definindo as palavras de controle a serem geradas pela unidade de controle ao fluxo de dados e os sinais recebidos pela unidade de controle do fluxo de dados.


**Obs.:** Um quinto passo é necessário para definir a frequência do relógio e o tipo de transição das unidades funcionais, subida ou descida.

**5. Unidades funcionais** – As unidades funcionais do fluxo de dados são:

 
5.a Multiplexador – Unidade 2 x 1 controlada pela variável de controle S.



5.b – Unidade lógica e aritmética.

 


5.c – Deslocador.

 

5.d – Buffer de saída.


BUFFER DE SAÍDA - 08 BITS

 

6. Unidade de controle - Responsável pela geração e controle sequencial síncrono das operações realizadas no fluxo de dados. É projetada como uma máquina de estados finitos a partir de um problema. Gera os sinais de controle e recebe "status" do fluxo de dados.

**Exemplo:** Transferência entre registradores de dados executar na seqüência as instruções:

 
1. Mem\_Bus → R<sub>1</sub>
2. R<sub>3</sub> → R<sub>2</sub>
3. Mem\_Bus → R<sub>3</sub>




Pede-se:

- a) Representação esquemática do sistema digital completo.
- b) Projeto da UC
- c) Quadro de instruções.

 a) Representação esquemática do sistema digital completo.



 b) Diagrama de estado de descrição da F.S.M. da U.C.



c) Quadro de instruções

item	instrução	S	in_R1	in_R2	in_R3	out_R1	out_R2	out_R3	PC's
1	R1 ← Mem_Bus	1	1	0	0	0	0	0	PC <sub>0</sub>
2	R2 ← R3	0	0	1	0	0	0	1	PC <sub>1</sub>
3	R3 ← Mem_Bus	1	0	0	1	0	0	0	PC <sub>2</sub>

d) Implementação da F.S.M.

Atual	Futuro	-
Q <sub>1</sub> Q <sub>0</sub>	Q <sub>1</sub> Q <sub>0</sub>	PC's
S0 - 00	01	PC <sub>0</sub>
S1 - 01	10	PC <sub>1</sub>
S2 - 10	00	PC <sub>2</sub>
S3 - 11	-	-

Equações booleanas entradas/saídas.

$$D_1 = Q_1'Q_0$$

$$D_0 = Q_0'Q_1'$$

$$PC_0 = (60)_H$$

$$PC_1 = (11)_H$$

$$PC_2 = (48)_H$$

$$S = S_0 + S_2;$$

$$in\_R_1 = S_0;$$

$$in\_R_2 = S_1;$$


$$in\_R_3 = S_2;$$

$$out\_R_1 = 0;$$


$$out\_R_2 = 0;$$

$$out\_R_3 = S_1$$

e) Circuito final da U.C.

 

f) Formas de ondas da U.C.

 

7. Parte final:

---



---



---



---

## VHDL – FLUXO DE DADOS

```
-- Quartus II VHDL
-- Basico latch
-- Registradores temporarios
library ieee;
use ieee.std_logic_1164.all;

entity reg_3
    is port
        (
            in_R1      : in bit;
            in_R2      : in bit;
            in_R3      : in bit;
            D           : in std_logic_vector (7 downto 0);
            Q1         : out std_logic_vector (7 downto 0);
            Q2         : out std_logic_vector (7 downto 0);
            Q3         : out std_logic_vector (7 downto 0));
end reg_3;

architecture Behavioral of reg_3 is

    signal dado1,dado2,dado3: std_logic_vector (7 downto 0);

begin

    process (in_R1,in_R2,in_R3)
        Variable valor: Integer range 0 to 255;
        begin

            IF in_R1 = '1' then dado1 <= D;
            ELSE dado1 <= dado1;
            END IF;
            IF in_R2 = '1' then dado2 <= D;
            ELSE dado2 <= dado2;
            END IF;
            IF in_R3 = '1' then dado3 <= D;
            ELSE dado3 <= dado3;
            END IF;

        End Process;
        Q1 <= dado1;
        Q2 <= dado2;
        Q3 <= dado3;
    End Behavioral;

-- 2-to-1 MUX
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY mux2 IS PORT (
    S0           : IN std_logic; -- select line
    D0,D1       : IN std_logic_vector(7 downto 0); -- data bus input
    Y: OUT std_logic_vector(7 downto 0)); -- data bus output
END mux2;
```

```
ARCHITECTURE Behavioral OF mux2 IS
```

```
  BEGIN
    PROCESS(S0,D1,D0)
      BEGIN
        IF (S0='0')THEN
          Y <= D0;
        END IF;
        IF (S0 ='1') THEN
          Y <= D1;
        END IF;
      END PROCESS;
    END Behavioral;
```

```
-- Tri-state buffer
```

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
ENTITY buffer1 IS PORT (
  OE: IN std_logic;
  D: IN std_logic_vector(7 DOWNTO 0);
  saida: OUT std_logic_vector(7 DOWNTO 0));
END buffer1;
```

```
ARCHITECTURE Behavioral OF buffer1 IS
```

```
  BEGIN
    PROCESS (OE, D) -- get error message if no d
      BEGIN
        IF (OE = '1') THEN
          saida <= D;
        ELSE
          saida <= (OTHERS => 'Z'); -- to get 8 Z values
        END IF;
      END PROCESS;
    END Behavioral;
```

```
-- Tri-state buffer
```

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
ENTITY buffer2 IS PORT (
  OE: IN std_logic;
  D: IN std_logic_vector(7 DOWNTO 0);
  saida: OUT std_logic_vector(7 DOWNTO 0));
END buffer2;
```

```
ARCHITECTURE Behavioral OF buffer2 IS
```

```
  BEGIN
    PROCESS (OE, D) -- get error message if no d
      BEGIN
        IF (OE = '1') THEN
          saida <= D;
        ELSE
          saida <= (OTHERS => 'Z'); -- to get 8 Z values
        END IF;
      END PROCESS;
    END Behavioral;
```

-- Tri-state buffer

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY buffer3 IS PORT (
    OE: IN std_logic;
    D: IN std_logic_vector(7 DOWNTO 0);
    saida: OUT std_logic_vector(7 DOWNTO 0));
END buffer3;

ARCHITECTURE Behavioral OF buffer3 IS
    BEGIN
        PROCESS (OE, D) -- get error message if no d
            BEGIN
                IF (OE = '1') THEN
                    saida <= D;
                ELSE
                    saida <= (OTHERS => 'Z'); -- to get 8 Z values
                END IF;
            END PROCESS;
    END Behavioral;
```

-- BUS CANAL

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY Bus_canal IS PORT (
    out_R1: in std_logic;
    out_R2: in std_logic;
    out_R3: in std_logic;
    A: in std_logic_vector(7 downto 0);
    B: in std_logic_vector(7 downto 0);
    C: in std_logic_vector(7 downto 0);
    Y: out std_logic_vector(7 DOWNTO 0));
END Bus_canal;

ARCHITECTURE Behavioral OF Bus_canal IS
    BEGIN
        PROCESS(out_R1,out_R2,out_R3)
            BEGIN
                IF out_R1 = '1' Then Y <= A;
                ELSIF out_R2 = '1' Then Y <=B;
                ELSIF out_R3 = '1' Then Y <=C;
                ELSE
                    Y <= (OTHERS =>'Z');
                END IF;
            END PROCESS;
    END Behavioral;
```

-- Tri-state buffer

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY apresenta IS PORT (
    OE: IN std_logic;
    D: IN std_logic_vector(7 DOWNTO 0);
    output: OUT std_logic_vector(7 DOWNTO 0));
END apresenta;
```

ARCHITECTURE Behavioral OF apresenta IS

BEGIN

    PROCESS (OE, D) -- get error message if no d

        BEGIN

            IF (OE = '1') THEN

                output <= D;

            ELSE

                output <= (OTHERS => 'Z'); -- to get 8 Z values

            END IF;

    END PROCESS;

END Behavioral;

LIBRARY ieee;

USE ieee.std\_logic\_1164.all;

ENTITY rtl\_aula15 IS PORT (

    input\_mem: IN std\_logic\_vector(7 DOWNTO 0);

    IE0: IN std\_logic;

    in\_R1: in bit;

    in\_R2: in bit;

    in\_R3: in bit;

    out\_R1: in std\_logic;

    out\_R2: in std\_logic;

    out\_R3: in std\_logic;

    OE: in std\_logic;

    output: out std\_logic\_vector(7 downto 0));

END rtl\_aula15;

ARCHITECTURE Structural OF rtl\_aula15 IS

    COMPONENT reg\_3 PORT(

        in\_R1, in\_R2, in\_R3: in bit;

        D: in std\_logic\_vector(7 DOWNTO 0);

        Q1: out std\_logic\_vector(7 DOWNTO 0);

        Q2: out std\_logic\_vector(7 DOWNTO 0);

        Q3: out std\_logic\_vector(7 DOWNTO 0));

    END COMPONENT;

    COMPONENT mux2 PORT (

        S0: IN std\_logic; -- select lines

        D0, D1: IN std\_logic\_vector(7 DOWNTO 0); -- data bus input

        Y: OUT std\_logic\_vector(7 DOWNTO 0)); -- data bus output

    END COMPONENT;

    COMPONENT buffer1 PORT (

        OE: IN std\_logic;

        D: IN std\_logic\_vector(7 downto 0);

        Saida: OUT std\_logic\_vector(7 downto 0));

    END COMPONENT;

    COMPONENT buffer2 PORT (

        OE: IN std\_logic;

        D: IN std\_logic\_vector(7 downto 0);

        Saida: OUT std\_logic\_vector(7 downto 0));

    END COMPONENT;

```
COMPONENT buffer3 PORT (
OE: IN std_logic;
D: IN std_logic_vector(7 downto 0);
Saida: OUT std_logic_vector(7 downto 0));
END COMPONENT;
```

```
COMPONENT Bus_canal PORT(
out_R1: in std_logic;
out_R2: in std_logic;
out_R3: in std_logic;
A: in std_logic_vector(7 downto 0);
B: in std_logic_vector(7 downto 0);
C: in std_logic_vector(7 downto 0);
Y: out std_logic_vector(7 downto 0));
END COMPONENT;
```

```
COMPONENT apresenta PORT (
OE: IN std_logic;
D: IN std_logic_vector(7 downto 0);
output: OUT std_logic_vector(7 downto 0));
END COMPONENT;
```

```
SIGNAL muxout : std_logic_vector(7 DOWNTO 0 );
SIGNAL tristateout1, tristateout2, tristateout3: std_logic_vector(7 DOWNTO 0 );
SIGNAL R1_out, R2_out, R3_out: std_logic_vector(7 downto 0);
SIGNAL orout: std_logic_vector(7 downto 0);
BEGIN
```

-- doing structural modeling here

```
U0: reg_3 PORT MAP(in_R1, in_R2, in_R3, muxout, R1_out, R2_out, R3_out);
U1: mux2 PORT MAP(IE0, input_mem, orout, muxout );
U2: buffer1 PORT MAP(out_R1, R1_out, tristateout1);
U3: buffer2 PORT MAP(out_R2, R2_out, tristateout2);
U4: buffer3 PORT MAP(out_R3, R3_out, tristateout3);
U5: Bus_canal PORT MAP(out_R1, out_R2, out_R3, tristateout1, tristateout2, tristateout3, orout);
U6: apresenta PORT MAP(OE, muxout, output);
END Structural;
```

VHDL – Unidade de controle

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
ENTITY uc_aula15 IS
PORT(
clk : IN BIT;
reset : IN BIT;
q : OUT BIT_VECTOR(1 DOWNTO 0);
B : OUT std_logic_vector(6 downto 0));
END uc_aula15;
```

```
ARCHITECTURE exemplo OF uc_aula15 IS
TYPE maq_estado IS (carga, transfer, move);
SIGNAL state: maq_estado;
BEGIN
PROCESS (clk)
```

```

BEGIN
    IF reset = '1'
        Then state <= carga;

    ELSIF clk'EVENT AND clk = '1' THEN
        CASE state IS
            WHEN carga =>
                state <= transfer;
            WHEN transfer =>
                state <= move;
            WHEN move =>
                state <= carga;
        END CASE;
    END IF;

    CASE state IS
        WHEN carga => B <= "1100000";
        WHEN transfer => B <= "0010001";
        WHEN move => B <= "1001000";
    END CASE;

    END PROCESS;

    WITH state SELECT
    q <="00" WHEN carga,
        "01" WHEN transfer,
        "10" WHEN move;

    END exemplo;

```

VHDL – Associação UC + DATAPATH

```

LIBRARY IEEE;
USE IEEE.std_logic_1164.all;
USE IEEE.std_logic_arith.all;

```

```

ENTITY cpu_aula15 IS PORT (
    clk_cpu: in std_logic;
    reset_cpu: IN std_logic;
    input_cpu: in std_logic_vector(7 downto 0);
    output_cpu: out std_logic_vector(7 downto 0));
END cpu_aula15;

```

ARCHITECTURE structure OF cpu\_aula15 IS

```

COMPONENT uc_aula15 PORT (
    clk : in std_logic;
    reset : in std_logic;

```

```

    IE0 : out std_logic;
    in_R1 : out std_logic;
    in_R2 : out std_logic;
    in_R3 : out std_logic;
    out_R1 : out std_logic;
    out_R2 : out std_logic;
    out_R3 : out std_logic;
    OE : out std_logic);

```

```

END COMPONENT;

```

```
COMPONENT rtl_aula15 PORT (
```

```
input_mem: in std_logic_vector(7 DOWNT0 0 );
```

```
IE0      : in std_logic;
```

```
in_R1 : in std_logic;
```

```
in_R2 : in std_logic;
```

```
in_R3 : in std_logic;
```

```
out_R1: in std_logic;
```

```
out_R2: in std_logic;
```

```
out_R3: in std_logic;
```

```
OE      : in std_logic;
```

```
output: out std_logic_vector(7 downto 0));
```

```
END COMPONENT;
```

```
--SIGNAL C_input_mem : std_logic_vector(7 DOWNT0 0);
```

```
SIGNAL output: std_logic_vector(7 downto 0);
```

```
SIGNAL C_IE0,C_out_R1,C_out_R2,C_out_R3,C_OE: std_logic;
```

```
SIGNAL C_in_R1,C_in_R2,C_in_R3: std_logic;
```

```
BEGIN
```

```
U0: uc_aula15 PORT MAP(clk_cpu,reset_cpu,C_IE0,C_in_R1,C_in_R2,C_in_R3,C_out_R1,C_out_R2,C_out_R3,C_OE);
```

```
U1: rtl_aula15 PORT MAP(input_cpu,C_IE0,C_in_R1,C_in_R2,C_in_R3,C_out_R1,C_out_R2,C_out_R3,C_OE,output_cpu);
```

```
END structure;
```