



**NPTEL Online Certification Course**  
**<Design of Power Electronics converter>**  
**<Assignment Number 5>: Detailed Solution**  
**Indian Institute of Technology Guwahati**



Note the following important instructions for entering answer:

- Enter values exactly as given in the datasheet.
- Enter answers upto two decimal places. For example: 3.00
- Apply rounding off. For example: enter 5.375 as 5.38 and 5.374 as 5.37
- Solve all problems dependent on answers of previous steps, using values obtained after rounding off upto two decimal places in previous steps.
- Do not enter the unit.

A buck converter is designed using MOSFETs - IRF540NPBF. Following can be noted for the converter:

Input voltage: 40 V

Output voltage: 30 V

Switching frequency( $f_s$ ): 100 kHz Ambient temperature: 60 ° C

Average inductor current,  $I_L$ : 8 A

Assume switch current  $I_{sw} = I_L$

From the datasheet of the MOSFET, note the following:

1. The value of ON state resistance,  $R_{D-on} \dots (m\Omega)$

**Ans: 44**

2. Typical turn ON time of MOSFET ... (ns)

**Ans:  $t_{d(on)} + t_r = (11 + 35) = 46$**

3. Typical turn OFF time of MOSFET ... (ns)

**Ans:  $t_{d(off)} + t_f = (39 + 35) = 74$**

4. Maximum junction temperature ... (° C)

**Ans: 175**

5. Junction to case resistance,  $R_{\theta jc} \dots (^\circ C/W)$

**Ans: 1.15**

6. Case to sink resistance,  $R_{\theta cs} \dots (^{\circ} C/W)$

**Ans: 0.50**

Calculate the following:

7. Conduction loss ... (W)

**Solution:**

From the given values of all parameters ( $V_{in} = 40V$ ,  $V_{out} = 30V$ ,  $I_L = 8A$ ,  $R_{D-on} = 44m\Omega$ ),  $D = V_{out}/V_{in} = 0.75$ .

$$\text{MOSFET conduction loss} = I_L^2 \times R_{D-on} \times D = 2.11 \text{ W}$$

**Ans: 2.11**

8. Switching loss ... (W)

**Solution:**

$$I_{sw} = I_L = 8A, f_s = 100kHz$$

$$\text{Switching loss} = V_{in} \times I_{sw} \times (t_{on} + t_{off}) \times f_s / 2 = 1.92 \text{ W}$$

**Ans: 1.92**

9. Total power loss ... (W)

**Solution:**

$$\text{Total power loss} = \text{conduction loss} + \text{switching loss} = (2.11 + 1.92) = 4.03 \text{ W}$$

**Ans: 4.03**

10. Sink to ambient resistance,  $R_{\theta sa} \dots (^{\circ} C/W)$

**Solution:**

$$T_j = (R_{\theta jc} + R_{\theta cs} + R_{\theta sa}) \times P_{diss} + T_a$$

$$\text{From here, } R_{\theta sa} = 26.89 ^{\circ} C/W$$

**Ans: 26.89**

11. Select the most appropriate heat sink for the design if natural cooling is performed:

(a) Manufacturer part no: **ICK SMD A 10 SA** ( $75 ^{\circ} C/W$ )

(b) Manufacturer part no: **217-36CTE6** ( $55 ^{\circ} C/W$ )

(c) Manufacturer part no: **ICK 14/16 L** ( $46 ^{\circ} C/W$ ) (d) Manufacturer part no: **FK 243 MI 247 O**

( $18.7 ^{\circ} C/W$ )

**Solution:**

As calculated  $R_{\theta_{sa}} = 26.89^\circ \text{C/W}$ , the  $R_{\theta_{sa}}$  of the heat sink has to be less than  $26.89^\circ \text{C/W}$

**Ans: d**

12. Let the heat sink **217-36CTE6** is used with forced air cooling. A fan of 200 LFM is used. At 200 LFM,  $R_{\theta_{sa}}$  of the heat sink is  $16^\circ \text{C/W}$ . Calculate the rise in temperature. ... ( $^\circ \text{C}$ )

**Solution:**

The rise in temperature =  $T_j = (R_{\theta_{jc}} + R_{\theta_{cs}} + R_{\theta_{sa}}) \times P_{diss} + T_a = 131.13^\circ \text{C}$

**Ans: 131.13**

Indian Institute of Technology Guwahati