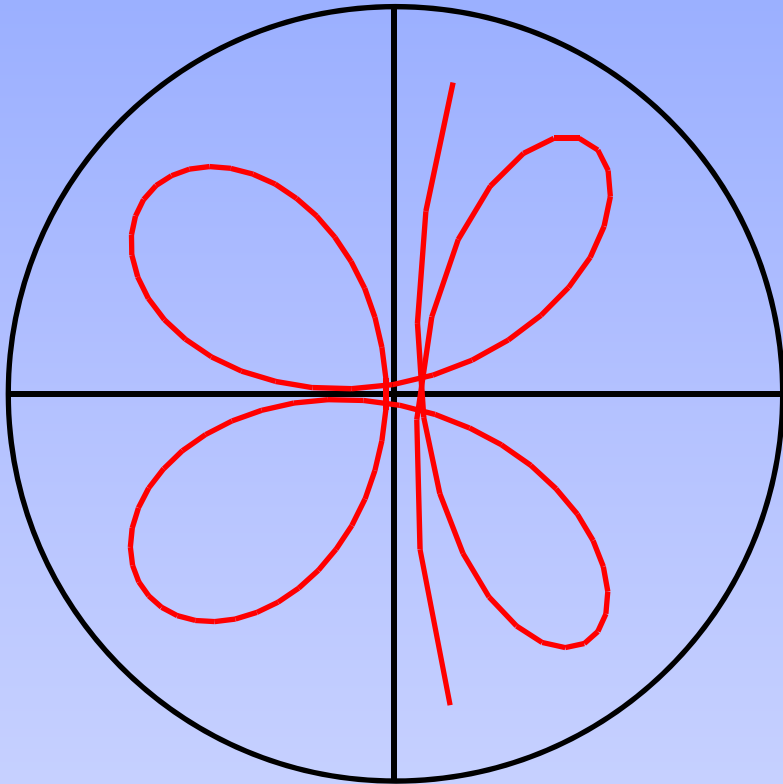


Narrowband Compline Filter Design with ANSYS HFSS




Daniel G. Swanson, Jr.

DGS Associates, LLC
Boulder, CO

dan@dgsboulder.com
www.dgsboulder.com


Introduction

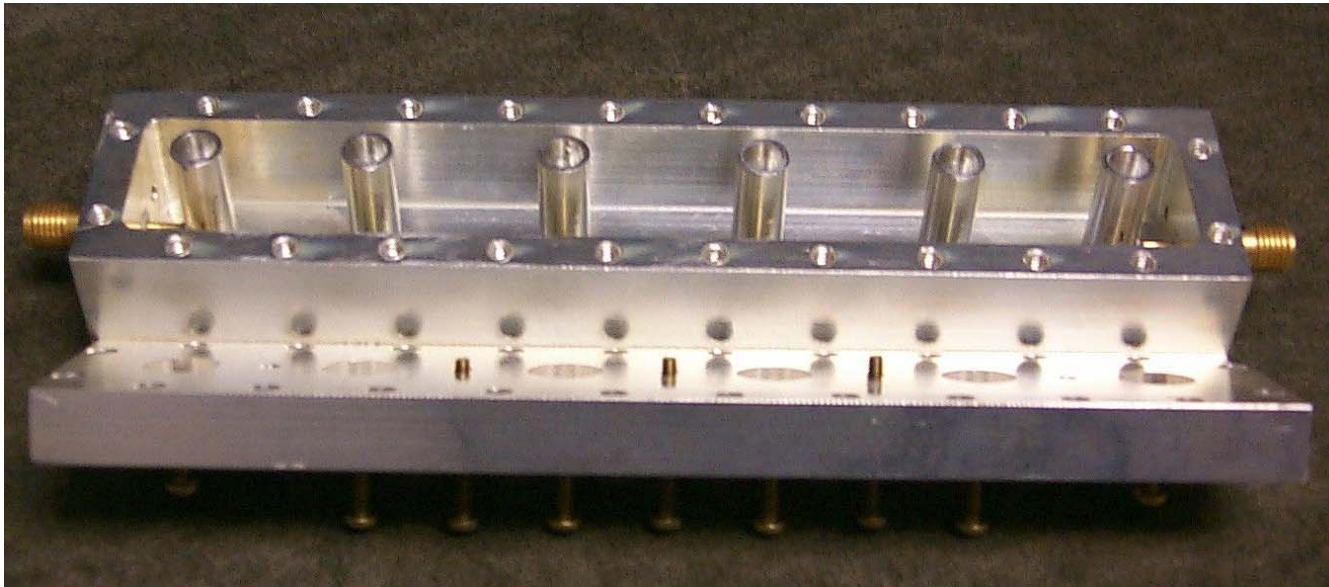N = 6 Inline, Cover Loaded, Comblin Filter



- Single comblin filters and comblin multiplexers can be found in many wireless systems.
- Today we will introduce a simple design flow for narrowband comblin filters using ANSYS HFSS.
- This material is suitable for the non-specialist who wants a better understanding of narrowband filter design.

Comblines Filter Examples

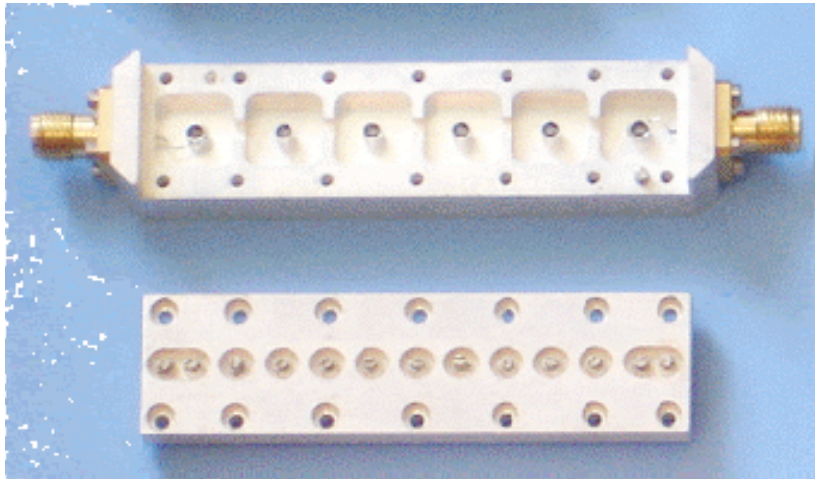


www.orionmicrowave.com

Comblines Triplexer




www.swfilterdesign.com

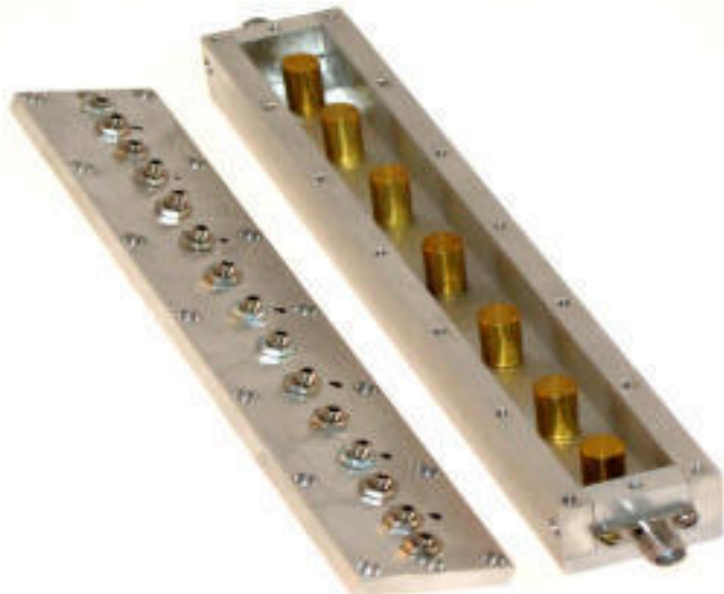

www.allenavionics.com

Compline Resonator Loading

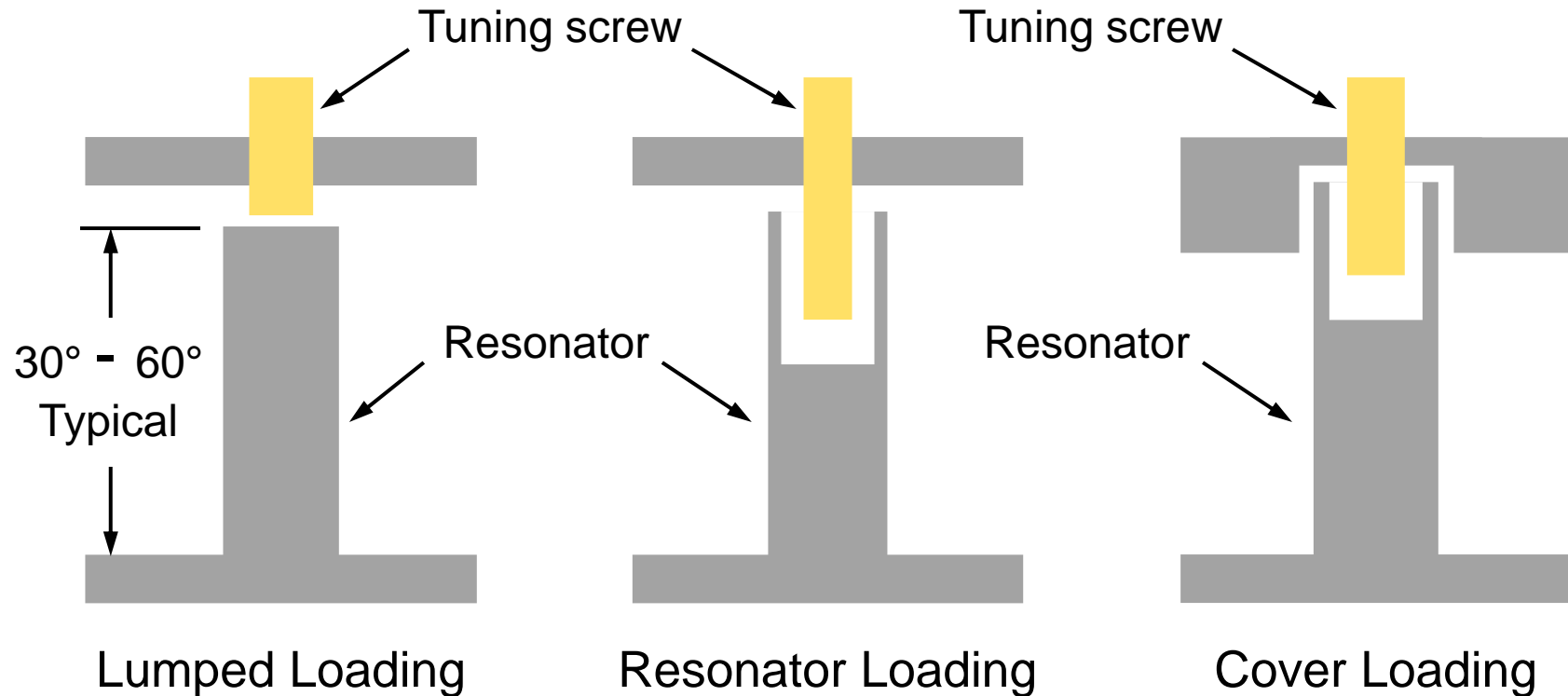

- We have resonators that are less than 90° long that we resonate with capacitance off the end.
- Resonator loading is perhaps the most flexible.
- Lumped loading is used at higher frequencies.
- Cover loading is typically used at lower frequencies.


Input / Output Coupling Options



Tapped Resonator



Inductive Loop

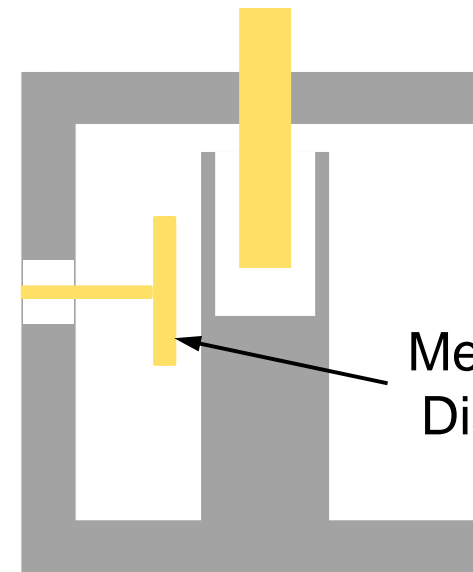

Metal
Disk

Capacitive Probe

- Tapping into the resonator works over a broad range of bandwidths and is quite common.
- Coupling with an inductive loop near the base of the resonator is another option.
- Using a capacitive probe is a third option.

Comblne Filter Design Flow

- Estimate order of filter and stopband rejection
- Build a model of the proposed resonator:
 - Compute available unloaded Q
 - Estimate insertion loss
- Build K_{ij} design curve
- Build Q_{ex} design curve
- Build a model of complete filter and apply port tuning
- Use port tuning corrections to refine filter dimensions
- Do final simulation of filter with loss:
 - Verify insertion loss in passband
 - Verify rejection in stopbands


Wimax Filter Example

| | |
|--------------------|-----------------------------------|
| Center Frequency: | $f_0 = 3440$ MHz |
| Equal Ripple BW: | BW = 70 MHz (add 10 MHz for temp) |
| Rejection: | >30 dB @ $f_0 \pm 80$ MHz |
| Insertion Loss: | <1 dB at band edges |
| Return Loss: | RL > 20 dB (should add margin) |
| Temperature Range: | -30 to +70 deg C |
| Power Handling: | < 20 dBm |

Morten Hagensen, "Narrowband Microwave Bandpass Filter Design by Coupling Matrix Synthesis," Guided Wave Technology, April 26, 2009.


www.gwtsoft.com/Misc/Hagensen3.pdf

Wimax Filter Example

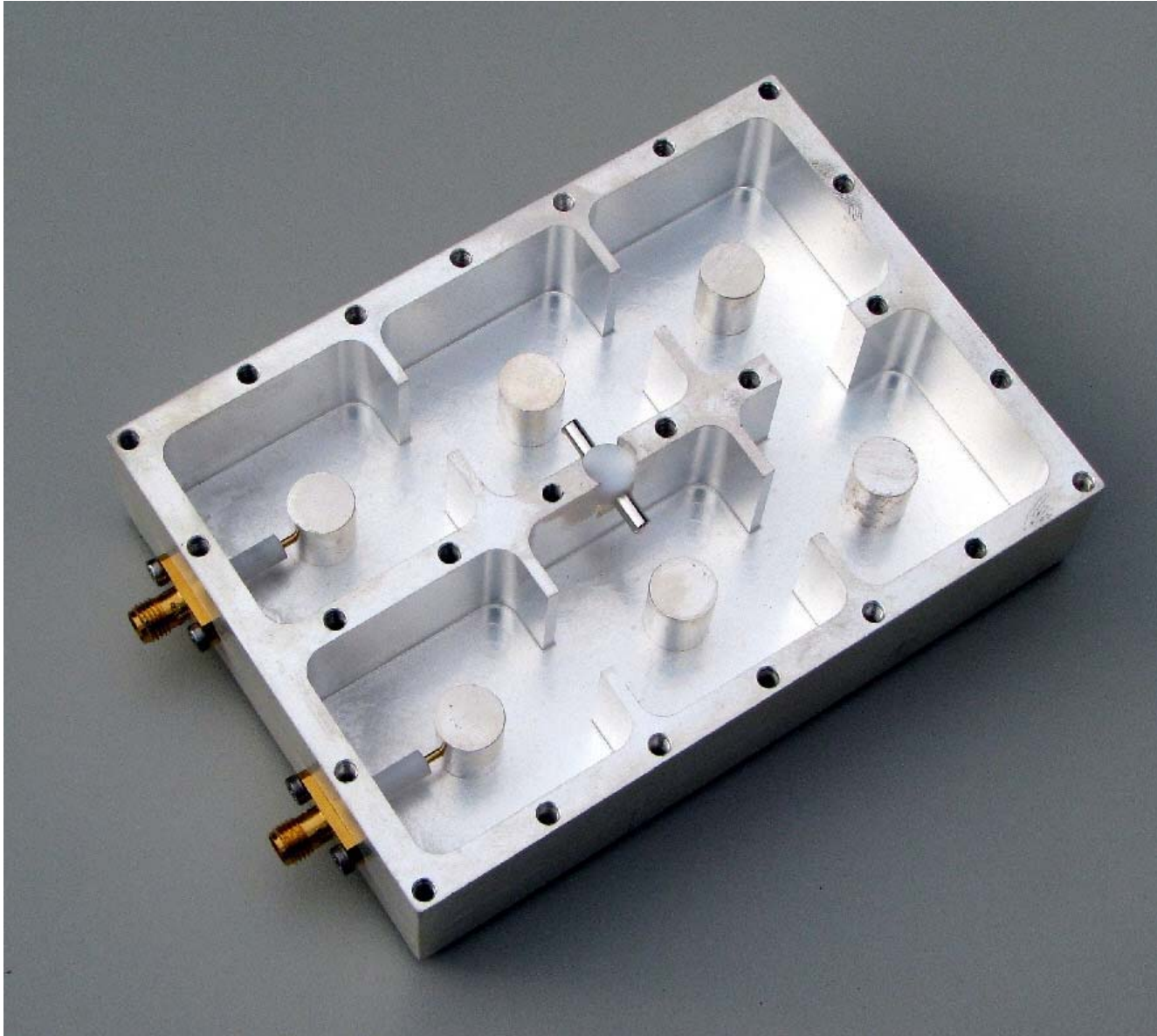

www.gwtsoft.com/Misc/Hagensen3.pdf

Comblines Filter Asymmetry or “Skewing”

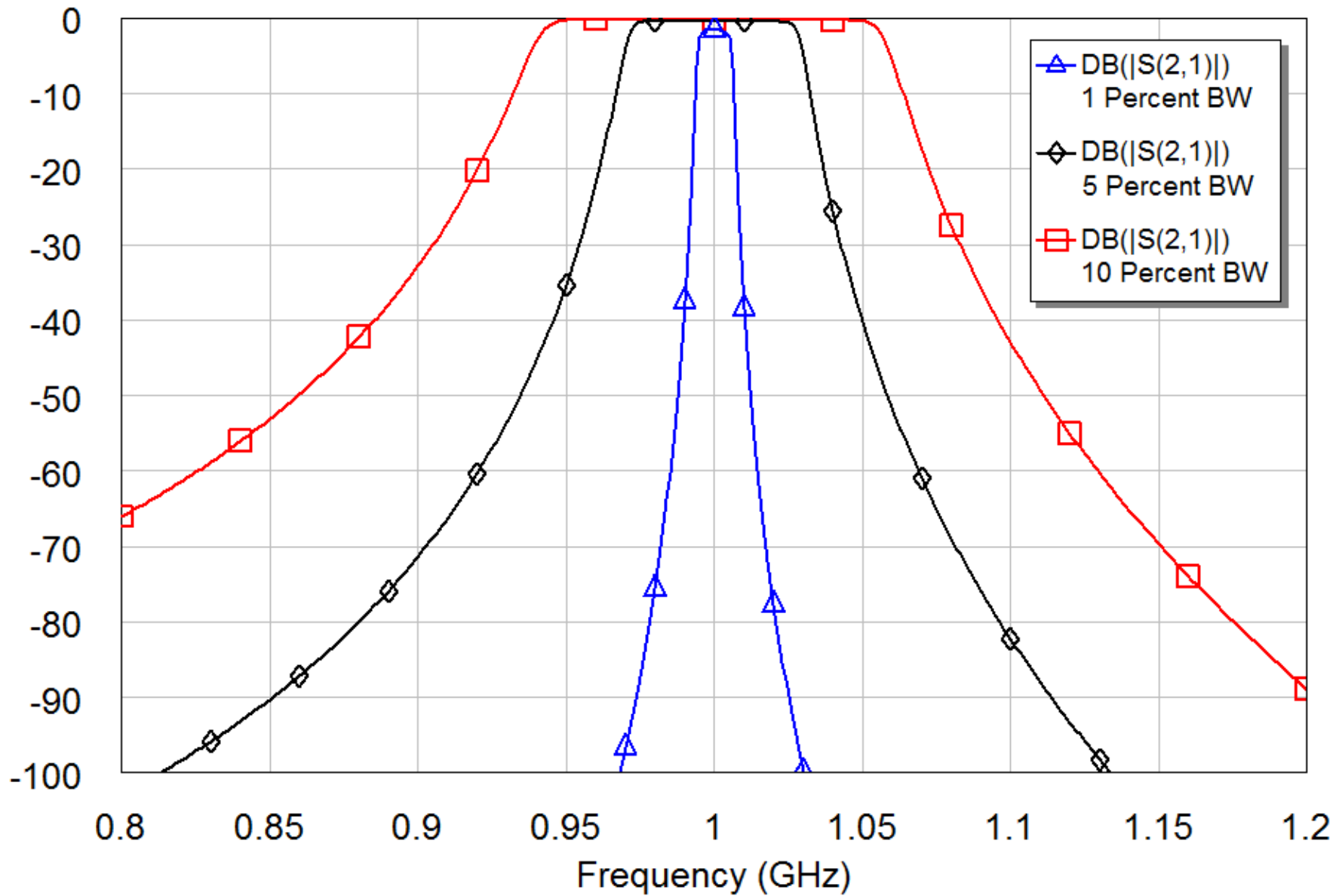

Estimating Filter Order

$$N > \frac{Rejection \text{ (dB)} + RtnLoss \text{ (dB)} + 6}{20 \log_{10}(S + \sqrt{S^2 - 1})}$$


Rejection = Stopband Insertion Loss

RtnLoss = Passband Return Loss


$$S = \frac{\text{Reject Bandwidth}}{\text{Filter Bandwidth}}$$

- Any simple formula that estimates filter order, N assumes the filter is symmetrical.
- Our 2% bandwidth filter is almost symmetrical and this estimate is probably good enough.
- For broader band combline filters, we may want to generate a circuit theory model to get a better estimate of stopband performance.

Estimating Filter Order

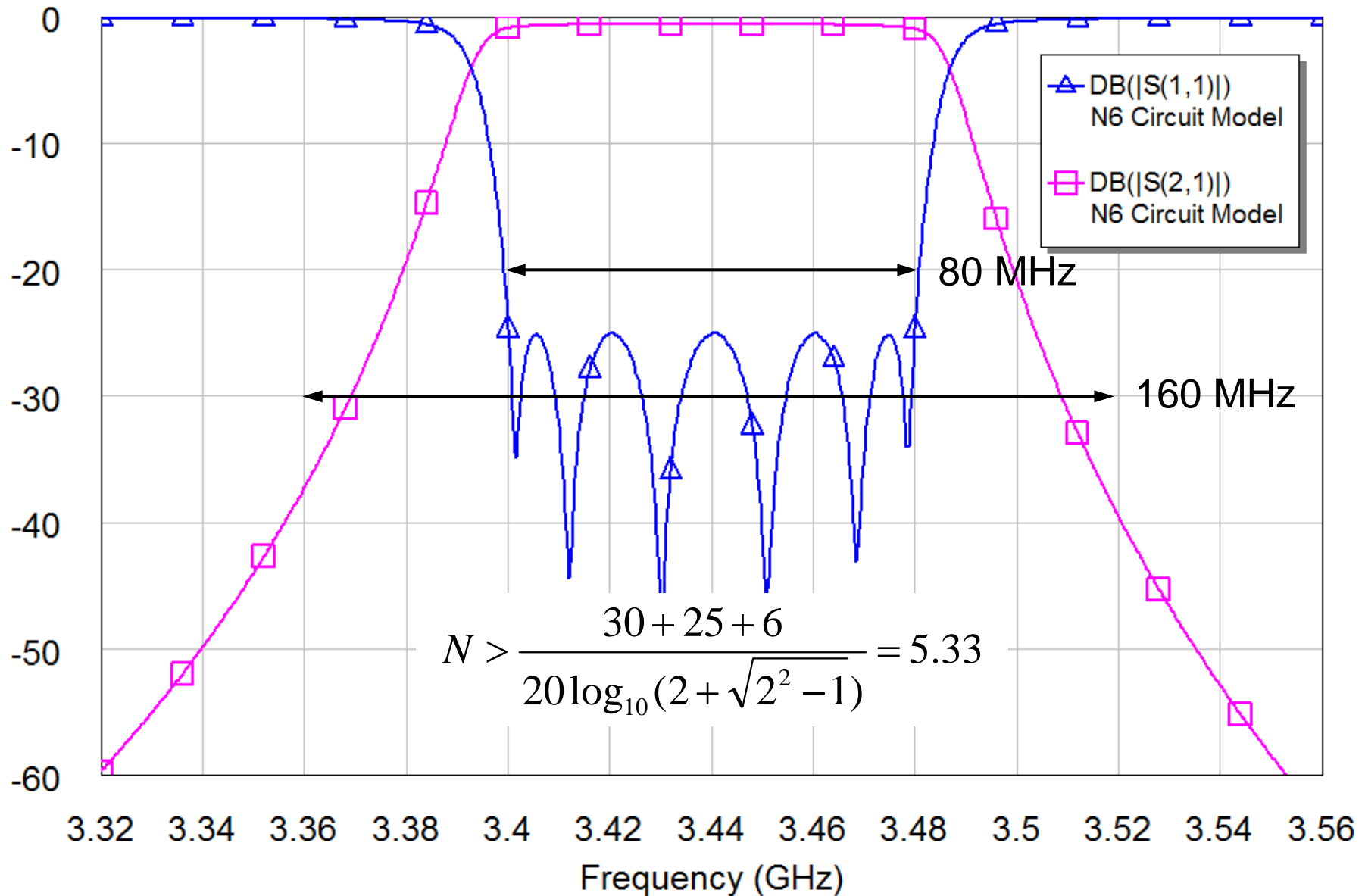

Qc of Infinitely Long Coaxial Line

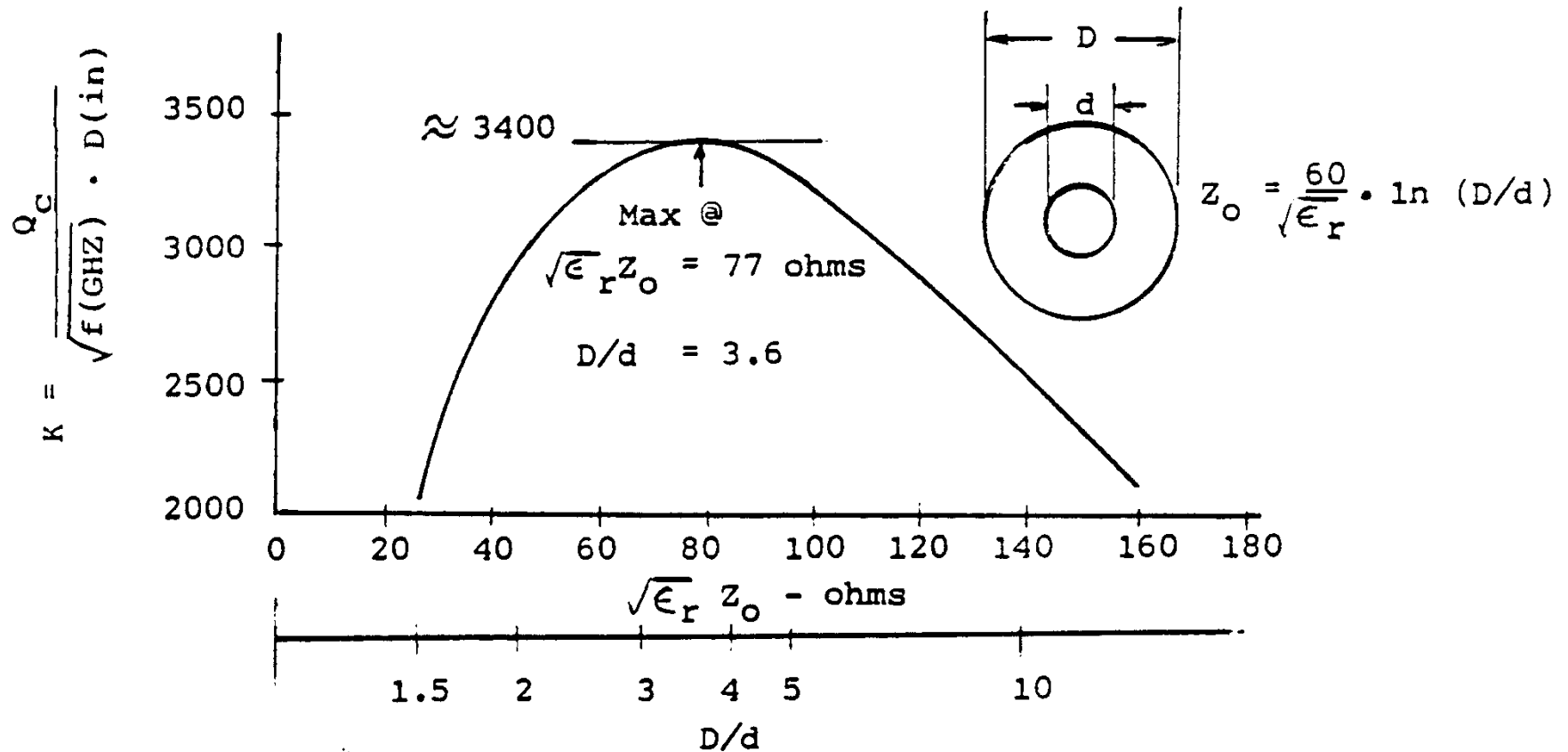


For a given dominant dimension D , maximum K and hence maximum realizable Q_c is achieved when $D/d = 3.6$, or $\sqrt{\epsilon_r} Z_0$ is about 77 ohms.

$$Q = K \sqrt{f} D \quad \text{Collect } K \text{ data from measured filters [1]}$$



Resonator Design: Zo

Wave port defined on top surface


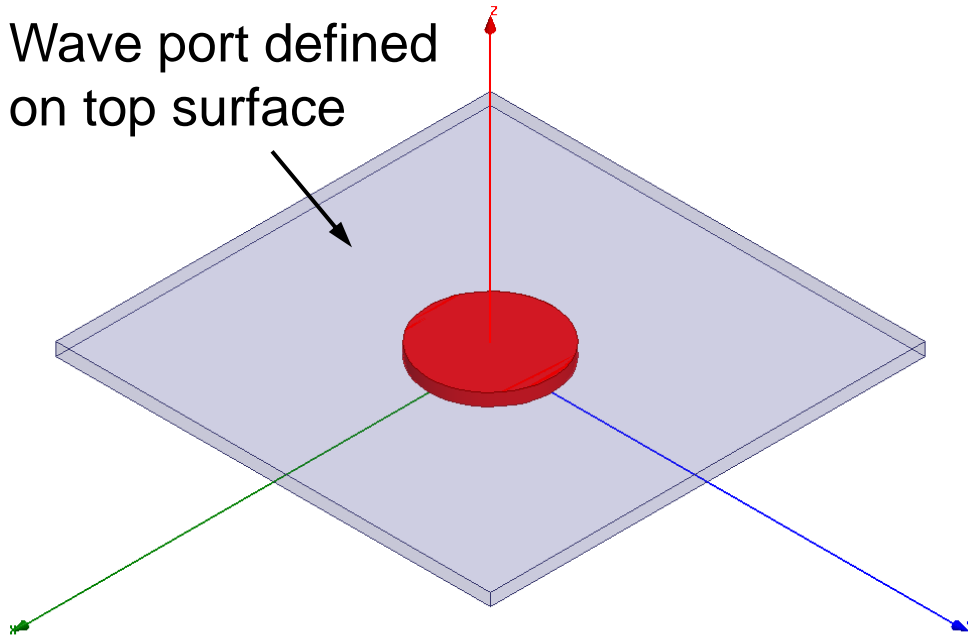


Outer: 35 x 35 mm
Inner: 10 mm dia
Height: Don't care

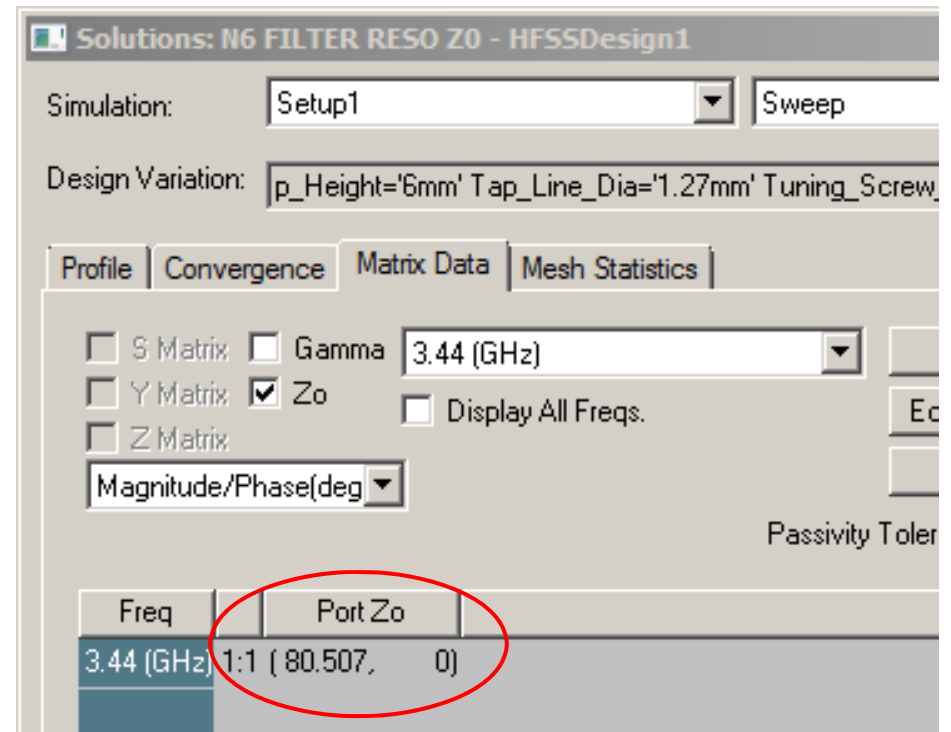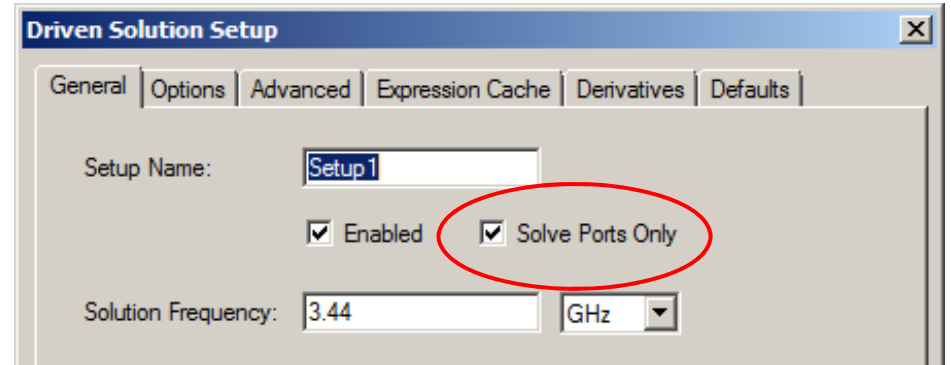- Use HFSS as a 2D cross-section solver
- 80.5 ohms is close enough to ideal Zo.



Resonator Design: Freq and Qu

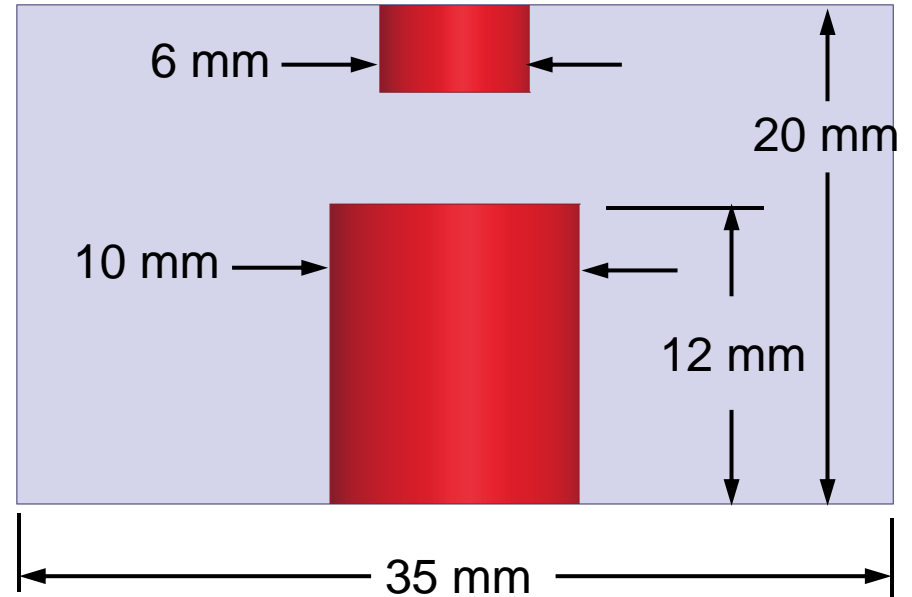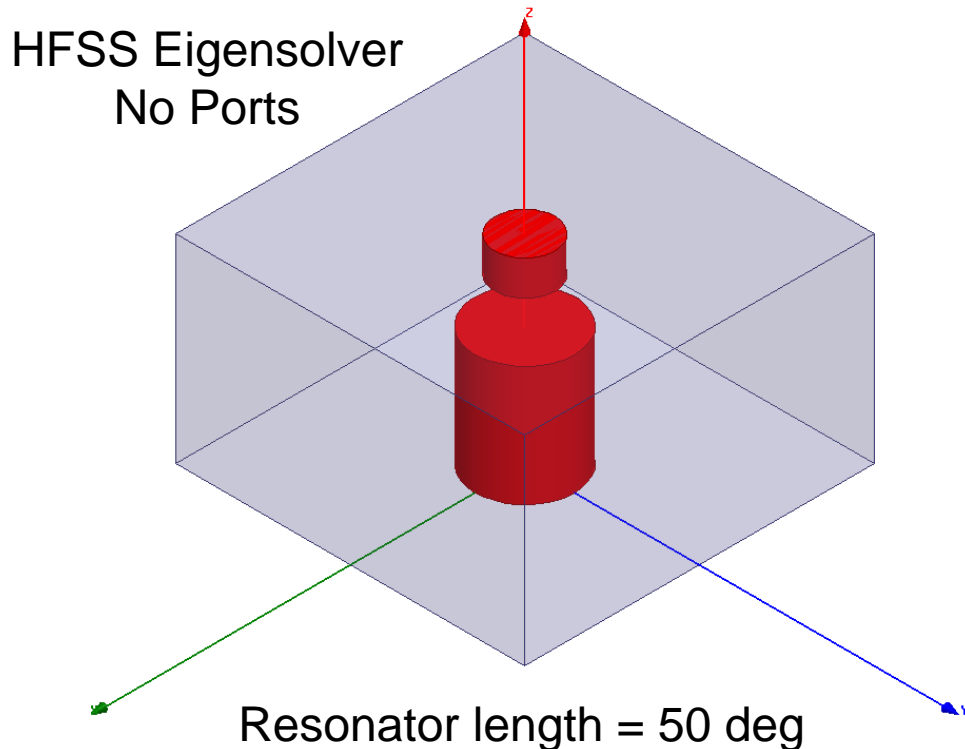

Solutions: N6 FILTER RESONATOR - HFSSDesign1

Simulation: Setup1

Design Variation: p_Height='6mm' Tap_Line_Dia='1.27mm'

Profile | Convergence | Eigenmode Data | Mesh Statistics

Solved Modes Export

| Eigenmode | Frequency (GHz) | Q |
|-----------|------------------------|---------|
| Mode 1 | 3.45873 +j 0.000293273 | 5896.77 |

- Surface of box, resonator and screw assumed to be silver plated.
- Use 80% of ideal conductivity as a starting point.
- Use measured data from filters to adjust conductivity in the future.

Chebyshev Lowpass Prototype

Chebyshev Lowpass Prototype: 0.044 dB ripple, 20 dB return loss, 1.22 VSWR

| N | g_0 | g_1 | g_2 | g_3 | g_4 | g_5 | g_6 | g_7 | g_8 | g_9 | g_{10} | $\sum g_1 - g_N$ |
|-----|--------|--------|--------|--------|--------|--------|--------|--------|--------|--------|----------|------------------|
| 2 | 1.0000 | 0.6682 | 0.5462 | 1.2222 | | | | | | | | 1.2144 |
| 3 | 1.0000 | 0.8534 | 1.1039 | 0.8534 | 1.0000 | | | | | | | 2.8144 |
| 4 | 1.0000 | 0.9332 | 1.2923 | 1.5795 | 0.7636 | 1.2222 | | | | | | 4.5727 |
| 5 | 1.0000 | 0.9732 | 1.3723 | 1.8032 | 1.3723 | 0.9732 | 1.0000 | | | | | 6.4989 |
| 6 | 1.0000 | 0.9958 | 1.4131 | 1.8950 | 1.5505 | 1.7272 | 0.8147 | 1.2222 | | | | 8.4011 |
| 7 | 1.0000 | 1.0097 | 1.4368 | 1.9414 | 1.6216 | 1.9414 | 1.4368 | 1.0097 | 1.0000 | | | 10.4028 |
| 8 | 1.0000 | 1.0189 | 1.4518 | 1.9682 | 1.6570 | 2.0252 | 1.6104 | 1.7744 | 0.8336 | 1.2222 | | 12.3447 |
| 9 | 1.0000 | 1.0252 | 1.4618 | 1.9852 | 1.6772 | 2.0662 | 1.6772 | 1.9852 | 1.4618 | 1.0252 | 1.0000 | 14.3710 |

- N is the lowpass or bandpass filter order.
- The g_i 's are frequency and impedance scaled values for a lowpass filter with a cutoff frequency of $\omega = 1$ radian and a return loss of 20 dB.
- Any given passband ripple / return loss level requires a unique table.
- Other tables are available in the literature or the g_i 's can be computed.

Midband Insertion Loss

Chebyshev Lowpass Prototype: 0.044 dB ripple, 20 dB return loss, 1.22 VSWR

| N | g_0 | g_1 | g_2 | g_3 | g_4 | g_5 | g_6 | g_7 | g_8 | g_9 | g_{10} | $\sum g_1 - g_N$ |
|-----|--------|--------|--------|--------|--------|--------|--------|--------|--------|--------|----------|------------------|
| 2 | 1.0000 | 0.6682 | 0.5462 | 1.2222 | | | | | | | | 1.2144 |
| 3 | 1.0000 | 0.8534 | 1.1039 | 0.8534 | 1.0000 | | | | | | | 2.8144 |
| 4 | 1.0000 | 0.9332 | 1.2923 | 1.5795 | 0.7636 | 1.2222 | | | | | | 4.5727 |
| 5 | 1.0000 | 0.9732 | 1.3723 | 1.8032 | 1.3723 | 0.9732 | 1.0000 | | | | | 6.4989 |
| 6 | 1.0000 | 0.9958 | 1.4131 | 1.8950 | 1.5505 | 1.7272 | 0.8147 | 1.2222 | | | | 8.4011 |
| 7 | 1.0000 | 1.0097 | 1.4368 | 1.9414 | 1.6216 | 1.9414 | 1.4368 | 1.0097 | 1.0000 | | | 10.4028 |
| 8 | 1.0000 | 1.0189 | 1.4518 | 1.9682 | 1.6570 | 2.0252 | 1.6104 | 1.7744 | 0.8336 | 1.2222 | | 12.3447 |
| 9 | 1.0000 | 1.0252 | 1.4618 | 1.9852 | 1.6772 | 2.0662 | 1.6772 | 1.9852 | 1.4618 | 1.0252 | 1.0000 | 14.3710 |

$$Loss(f_0) = \frac{4.343 \cdot \sum_{i=1}^N g_i \cdot f_0}{\Delta f \cdot Q_u} = \frac{4.343 \cdot 8.4011 \cdot 3.44}{0.08 \cdot 5900} = 0.27 \text{ dB}$$

- Q_u is a little optimistic, at the high end of what is possible.
- Loss will be higher at the band edges.

Dishal's Method

- As early as 1951, Milton Dishal [2] recognized that any narrow band, lumped element or distributed bandpass filter could be described by three fundamental variables:
 - the synchronous tuning frequency, f_0
 - the couplings between adjacent resonators, $K_{r,r+1}$
 - the singly loaded or external Q, Q_{ex}
- The K_{ij} set the bandwidth of the filter and the Q_{ex} sets the return loss level.
- For any narrowband filter (<10% bandwidth) we can compute the required K_{ij} and Q_{ex} from the Chebyshev lowpass prototype.
- The K and Q concept is universal and can be applied to any lumped element or distributed filter topology or technology [4,5].

Definition of Kij and Qex

$$Q_{ex} = \frac{f_0 \cdot g_0 \cdot g_1}{f_2 - f_1} = \frac{g_0 \cdot g_1}{BW}$$

$$K_{ij} = \frac{(f_2 - f_1)}{f_0 \sqrt{g_i \cdot g_j}} = \frac{BW}{\sqrt{g_i \cdot g_j}}$$

$$f_0 = \frac{f_1 + f_2}{2} \quad BW = \frac{f_2 - f_1}{f_0}$$

f_1 = bandpass filter lower equal ripple frequency

f_2 = bandpass filter upper equal ripple frequency

f_0 = bandpass filter center frequency

BW = percentage bandwidth

g_i = prototype element value for element i

Note: Equations assume Q_u is infinite.

Our Filter: $N = 6$, $BW = 2.3\%$

Chebyshev Lowpass Prototype: 0.044 dB ripple, 20 dB return loss, 1.22 VSWR

| N | g_0 | g_1 | g_2 | g_3 | g_4 | g_5 | g_6 | g_7 | g_8 | g_9 | g_{10} | $\Sigma g_1 - g_N$ |
|-----|--------|--------|--------|--------|--------|--------|--------|--------|--------|--------|----------|--------------------|
| 2 | 1.0000 | 0.6682 | 0.5462 | 1.2222 | | | | | | | | 1.2144 |
| 3 | 1.0000 | 0.8534 | 1.1039 | 0.8534 | 1.0000 | | | | | | | 2.8144 |
| 4 | 1.0000 | 0.9332 | 1.2923 | 1.5795 | 0.7636 | 1.2222 | | | | | | 4.5727 |
| 5 | 1.0000 | 0.9732 | 1.3723 | 1.8032 | 1.3723 | 0.9732 | 1.0000 | | | | | 6.4989 |
| 6 | 1.0000 | 0.9958 | 1.4131 | 1.8950 | 1.5505 | 1.7272 | 0.8147 | 1.2222 | | | | 8.4011 |
| 7 | 1.0000 | 1.0097 | 1.4368 | 1.9414 | 1.6216 | 1.9414 | 1.4368 | 1.0097 | 1.0000 | | | 10.4028 |
| 8 | 1.0000 | 1.0189 | 1.4518 | 1.9682 | 1.6570 | 2.0252 | 1.6104 | 1.7744 | 0.8336 | 1.2222 | | 12.3447 |
| 9 | 1.0000 | 1.0252 | 1.4618 | 1.9852 | 1.6772 | 2.0662 | 1.6772 | 1.9852 | 1.4618 | 1.0252 | 1.0000 | 14.3710 |

$$K_{1,2} = \frac{BW}{\sqrt{g_1 \cdot g_2}} = \frac{0.023}{\sqrt{0.9958 \cdot 1.4131}} = 0.0194$$

$$K_{2,3} = \frac{BW}{\sqrt{g_2 \cdot g_3}} = \frac{0.023}{\sqrt{1.4131 \cdot 1.8950}} = 0.0141$$

$$K_{3,4} = \frac{BW}{\sqrt{g_3 \cdot g_4}} = \frac{0.023}{\sqrt{1.8950 \cdot 1.5505}} = 0.0134$$


$$Q_{ex} = \frac{g_0 \cdot g_1}{BW} = \frac{1.0 \cdot 0.9958}{0.023} = 43.3$$

Computing Iris Widths and Tap Height


- Our resonator geometry is now fixed.
- We have enough Q_u to meet the insertion loss goal.
- We have goals for the K_{ij} 's and Q_{ex}
- Now we need to compute the iris widths and the tap height.

Basic Two Resonator HFSS Project

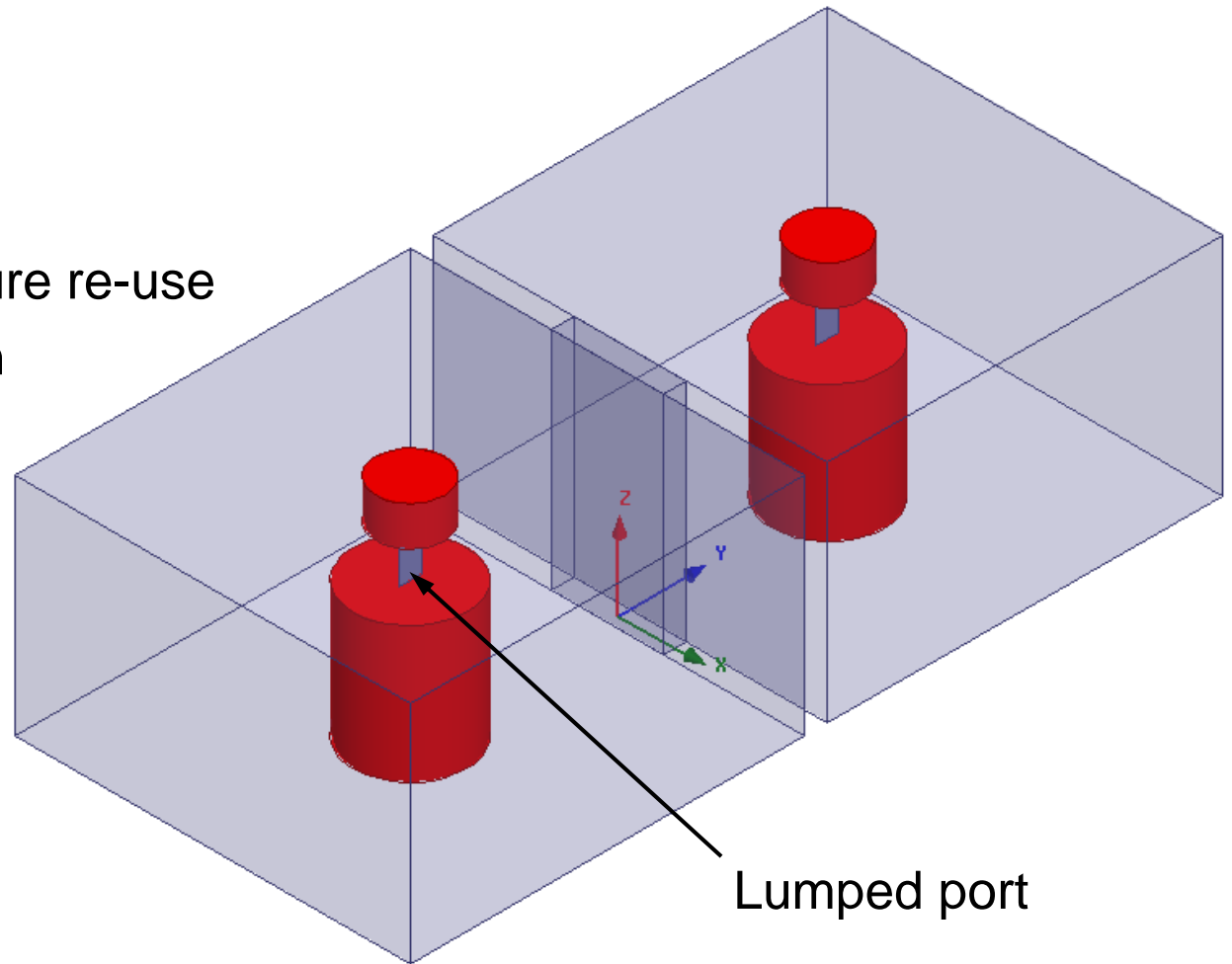- Distance between resonators is fixed
 - Iris width controls coupling
 - Some details ignored, like corner radii
- Lossless model
 - Faster
 - No corrections to K_{ij}
- Make it parametric for future re-use
- Lumped ports for tuning in our circuit simulator
 - FEM mesh is not perfectly symmetrical
 - Faster than making geometry changes in the EM model



Extracting Coupling Coefficients

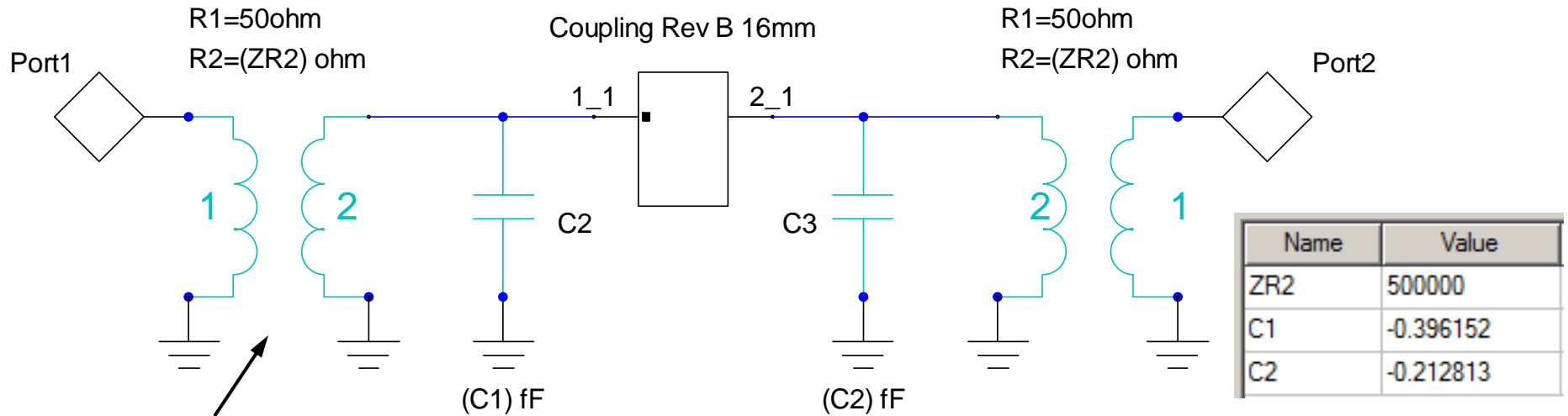


Loosely couple
with transformers.

We want to force
synchronous tuning.


At resonance:

$$\text{mag}(im(Y(1,1))) = 0$$

$$\text{mag}(im(Y(2,2))) = 0$$

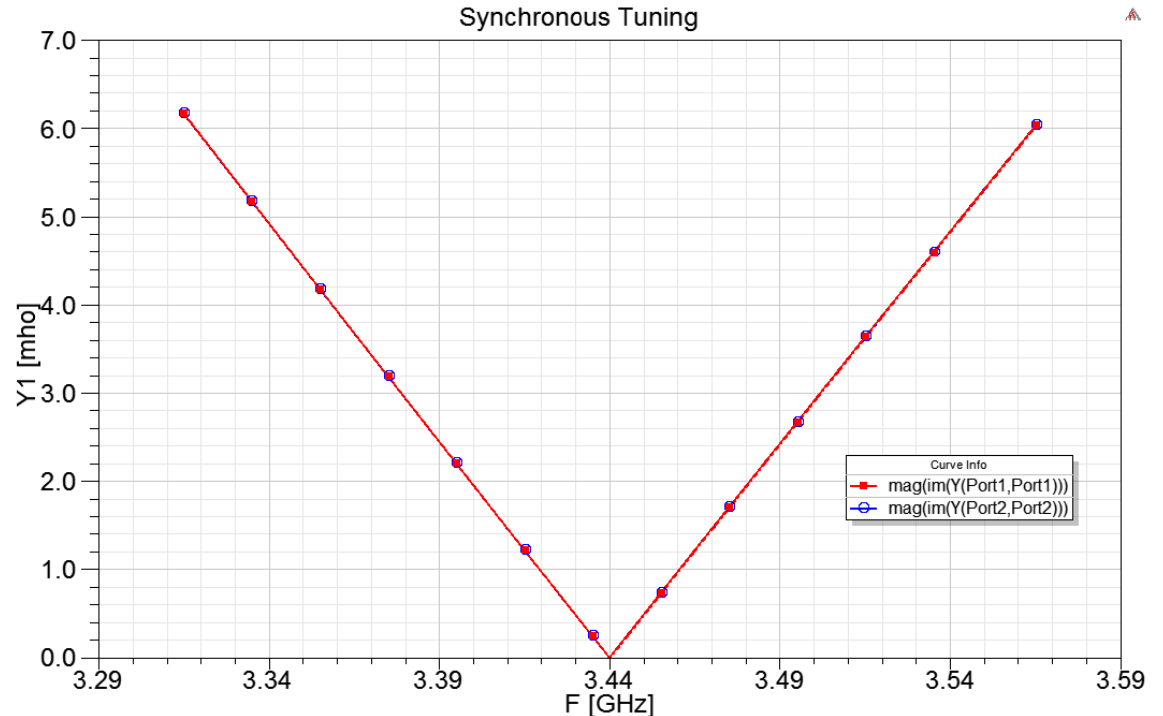


Extracting Coupling Coefficients

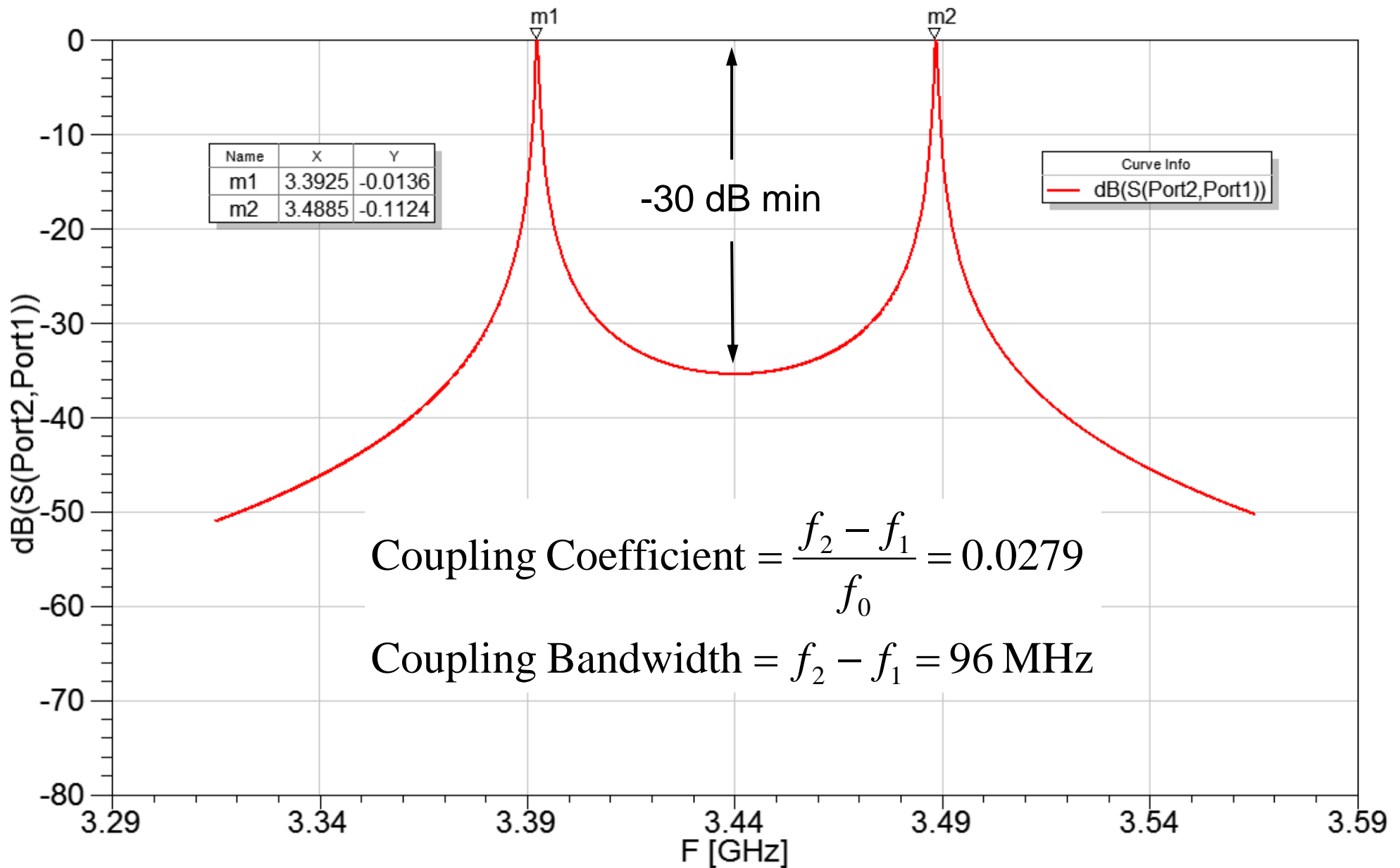


Dummy Elements Around The Iris

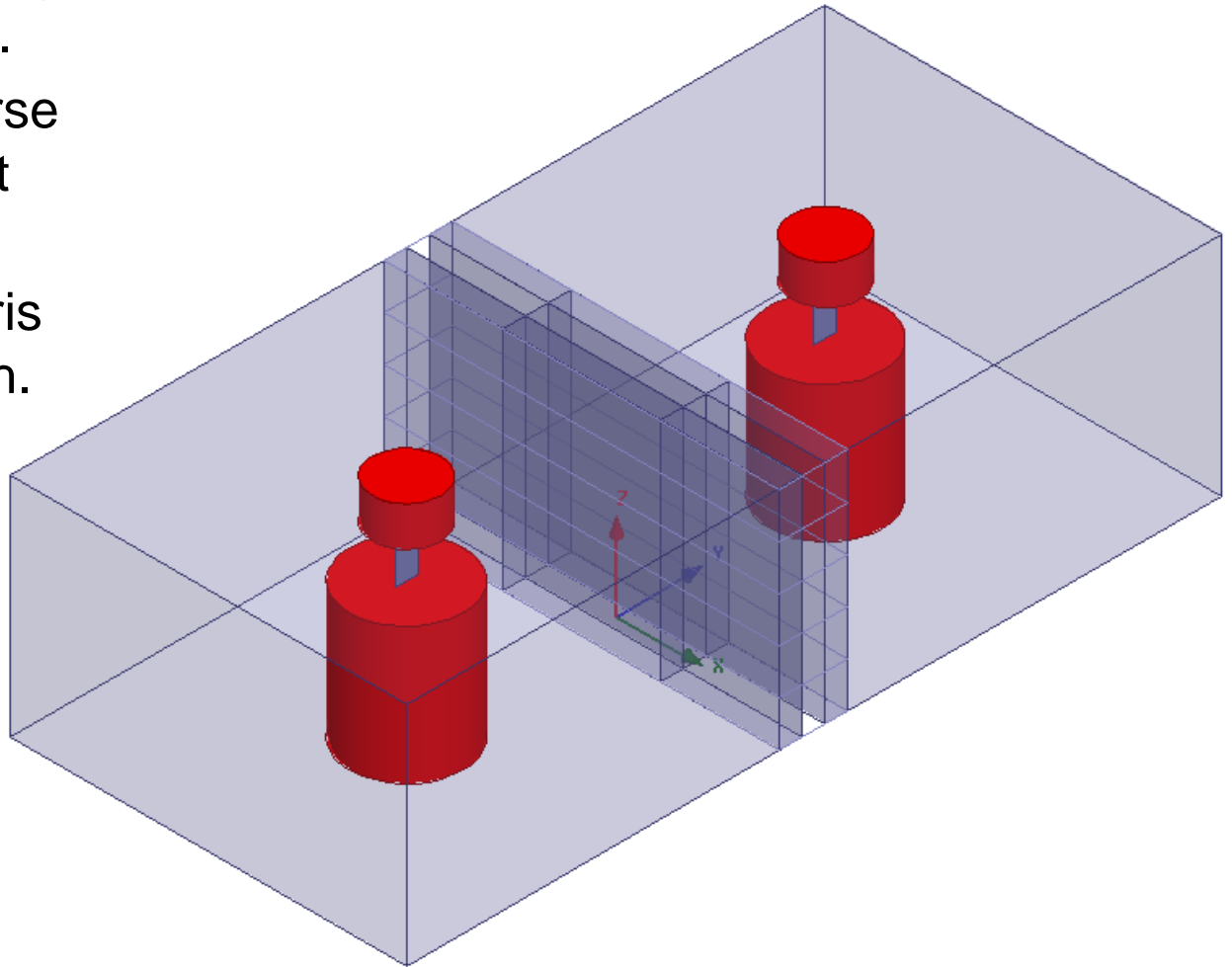- There are many evanescent modes in the iris region.
- The FEM mesher uses energy balance to refine the mesh.
- The mesh may be too coarse in the iris region for highest accuracy.
- Add physical detail in the iris region to force a finer mesh.
- Only important if you are comparing this simulation to measured hardware.




Coupling With and Without Dummies

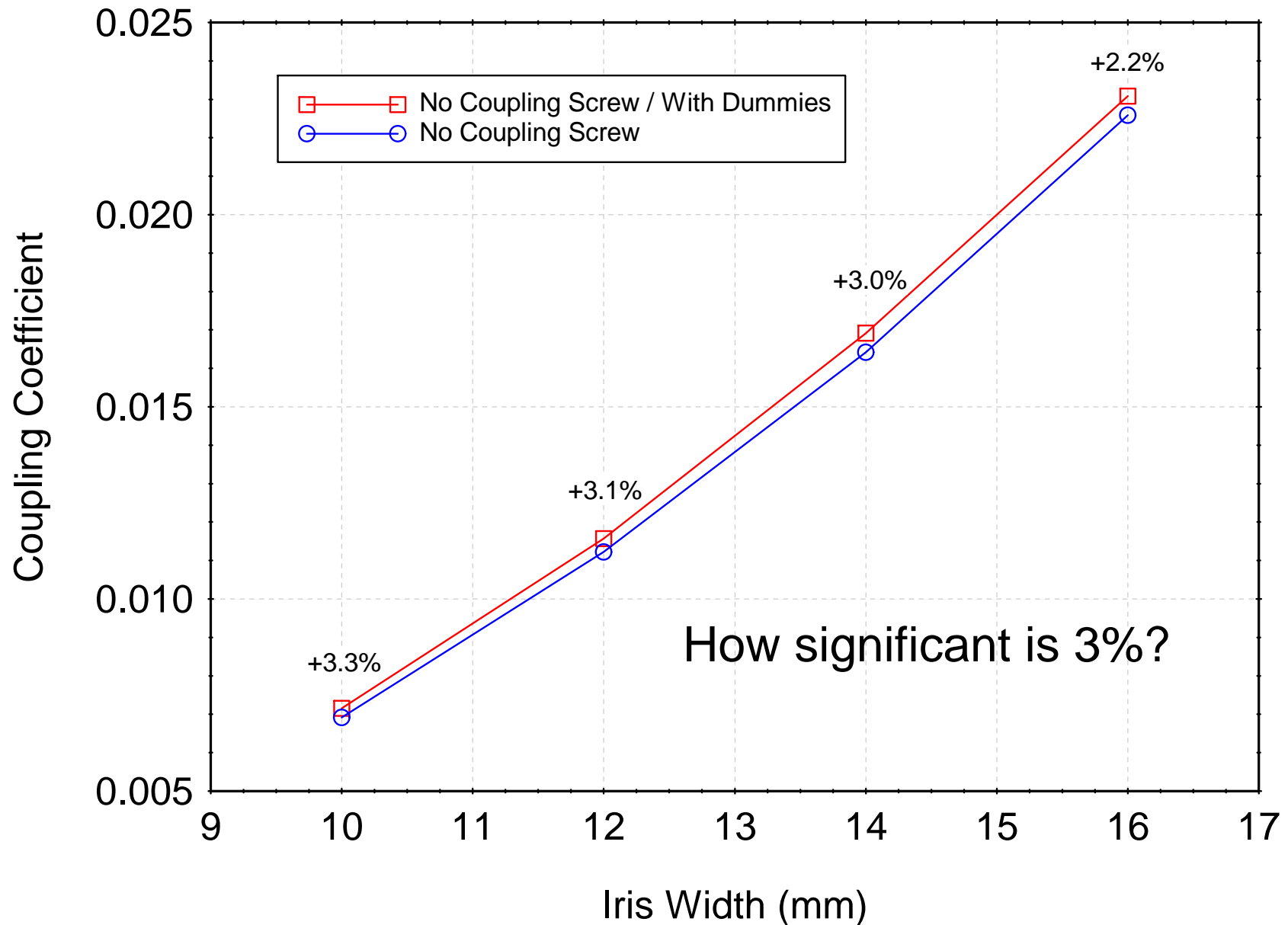


Add Coupling Screw

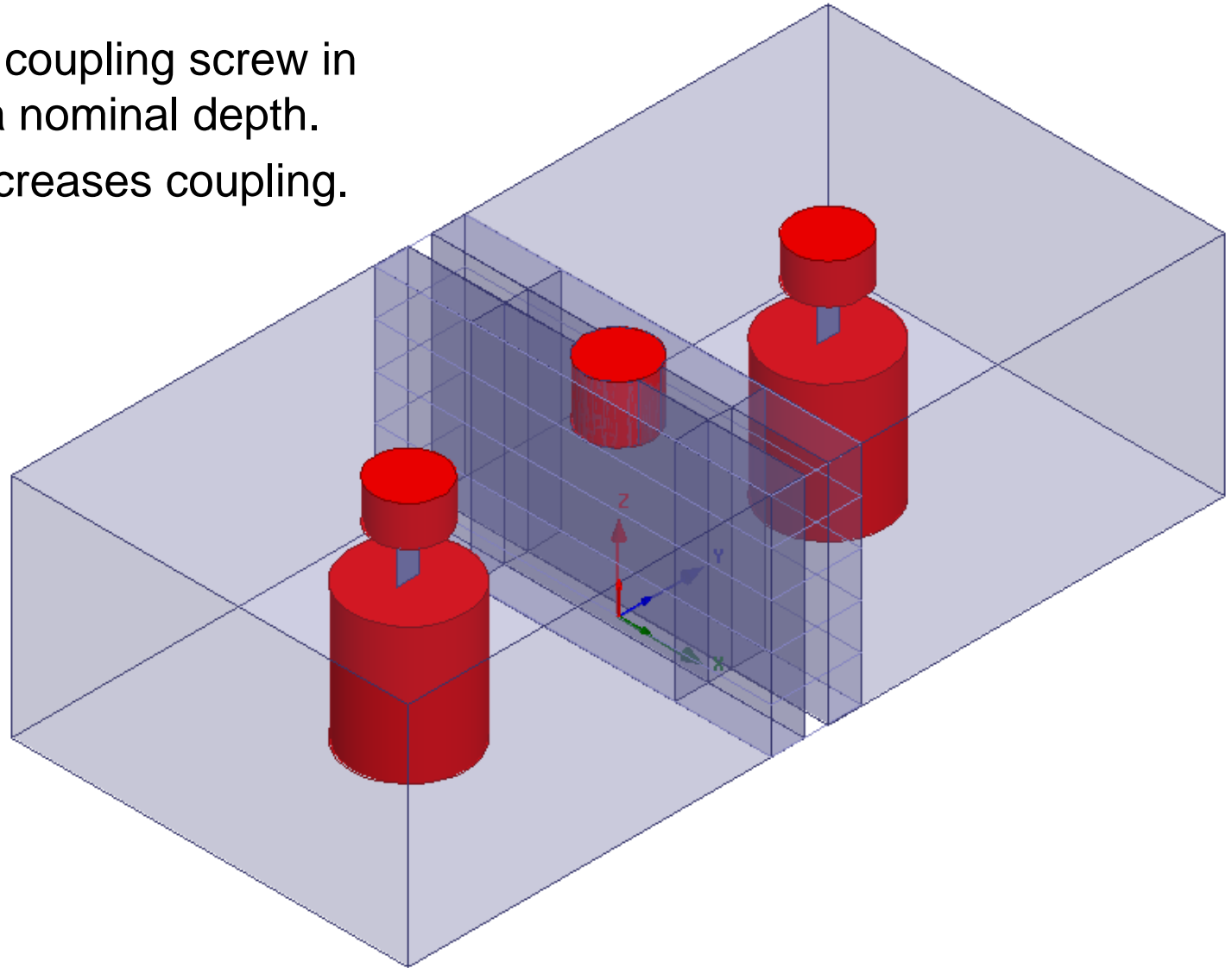
- We can include a coupling screw in our model set to a nominal depth.
- A longer screw increases coupling.



Coupling vs Screw Length & Iris Width

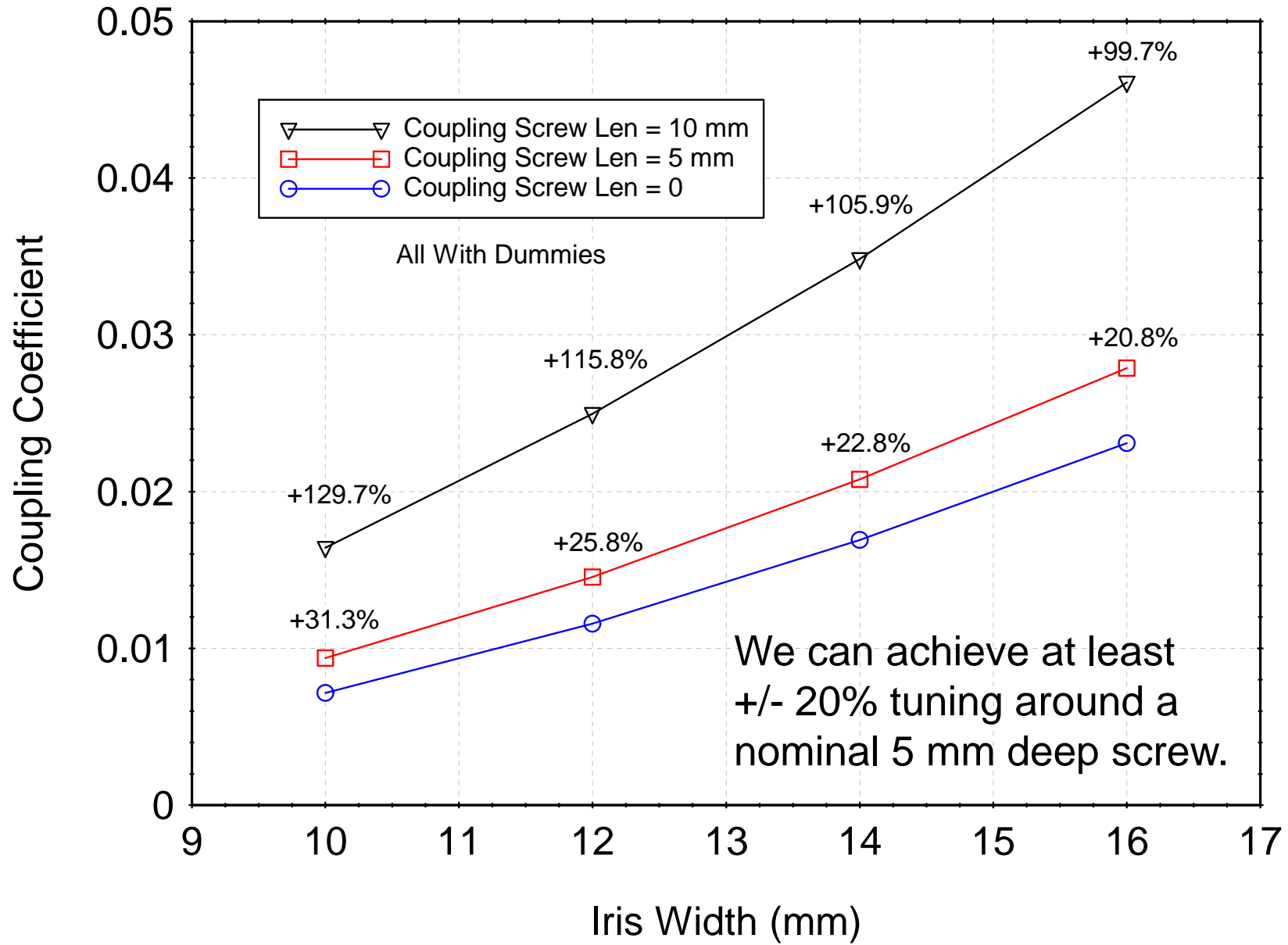

Coupling Curve For 2 mm Thick Wall

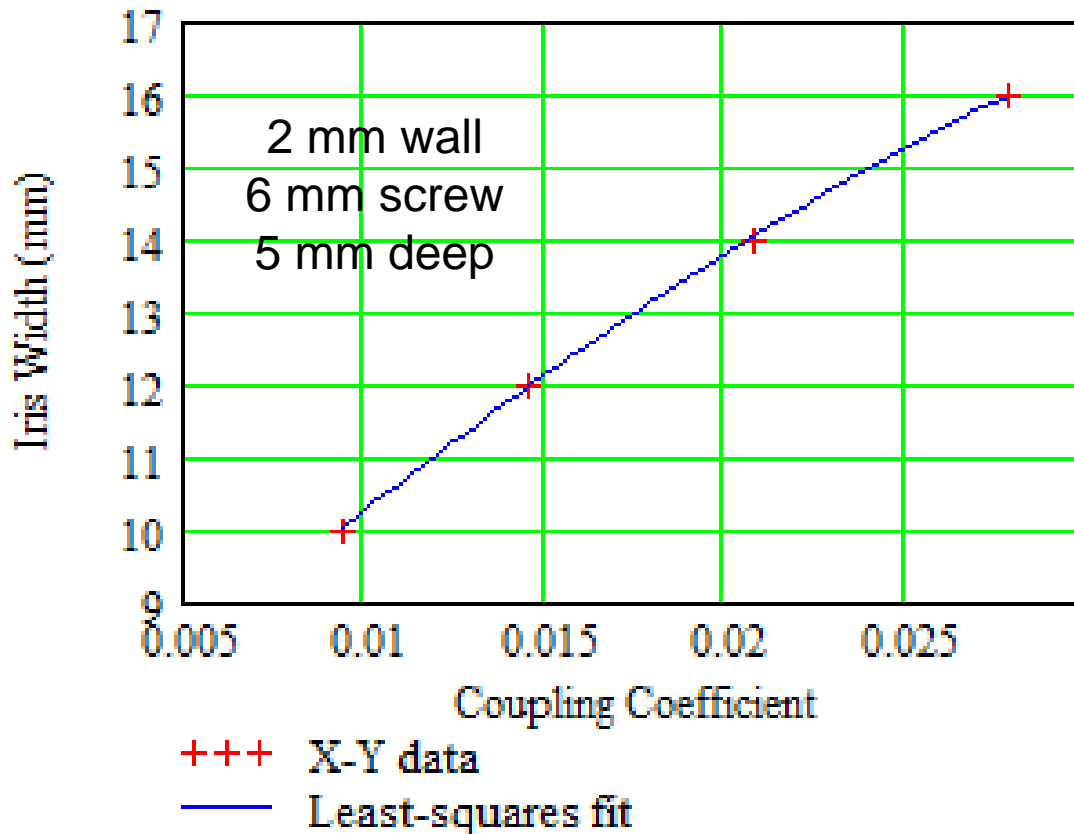


$$S = \begin{pmatrix} 5.902 \\ 476.295 \\ -4.103 \times 10^3 \end{pmatrix} \quad \begin{matrix} 2^{\text{nd}} \text{ order} \\ \text{polynomial} \\ \text{coefficients} \end{matrix}$$

$$K := .01493$$


$$\text{Iris_Width}(x) := F(x) \cdot S$$

$$\text{Iris_Width}(K) = 12.099$$
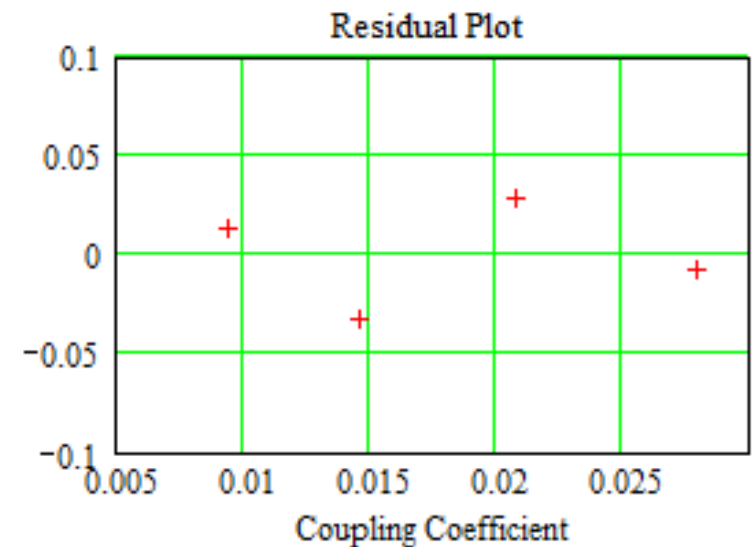
$$\text{Iris Width} = 5.9 + 476.3 \cdot K - 4103 \cdot K^2$$



Coupling Curve For 5 mm Thick Wall

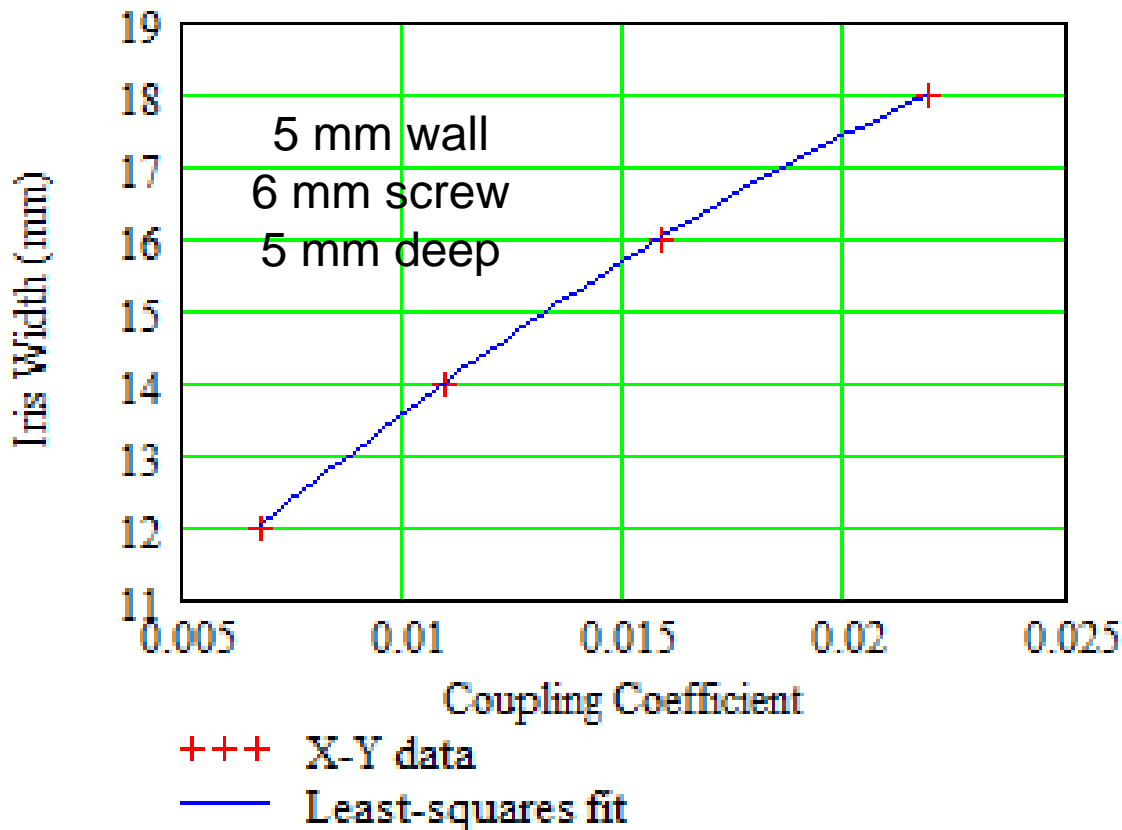


$$S = \begin{pmatrix} 8.261 \\ 604.054 \\ -7.273 \times 10^3 \end{pmatrix} \quad \text{2}^{\text{nd}} \text{ order polynomial coefficients}$$

$$K := .01493$$


$$\text{Iris_Width}(x) := F(x) \cdot S$$

$$\text{Iris_Width}(K) = 15.658$$

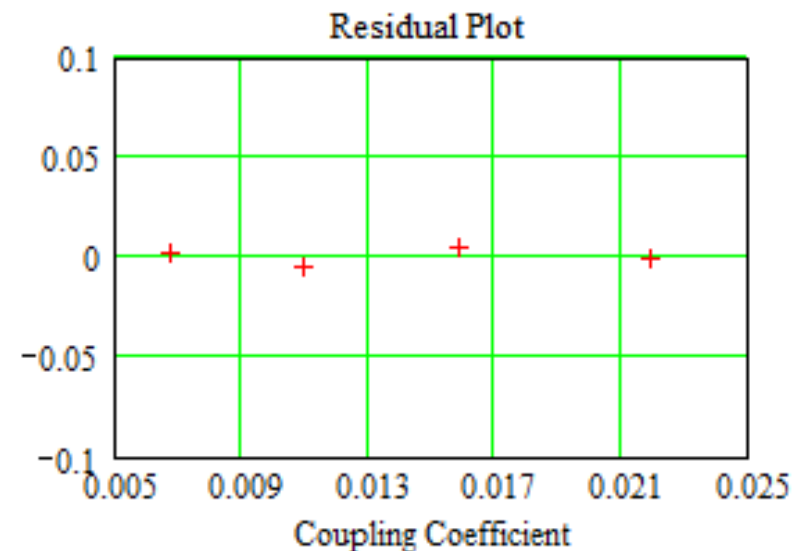
$$\text{Iris Width} = 8.3 + 604.1 \cdot K - 7273 \cdot K^2$$




Coupling Coefficients vs Iris Thickness

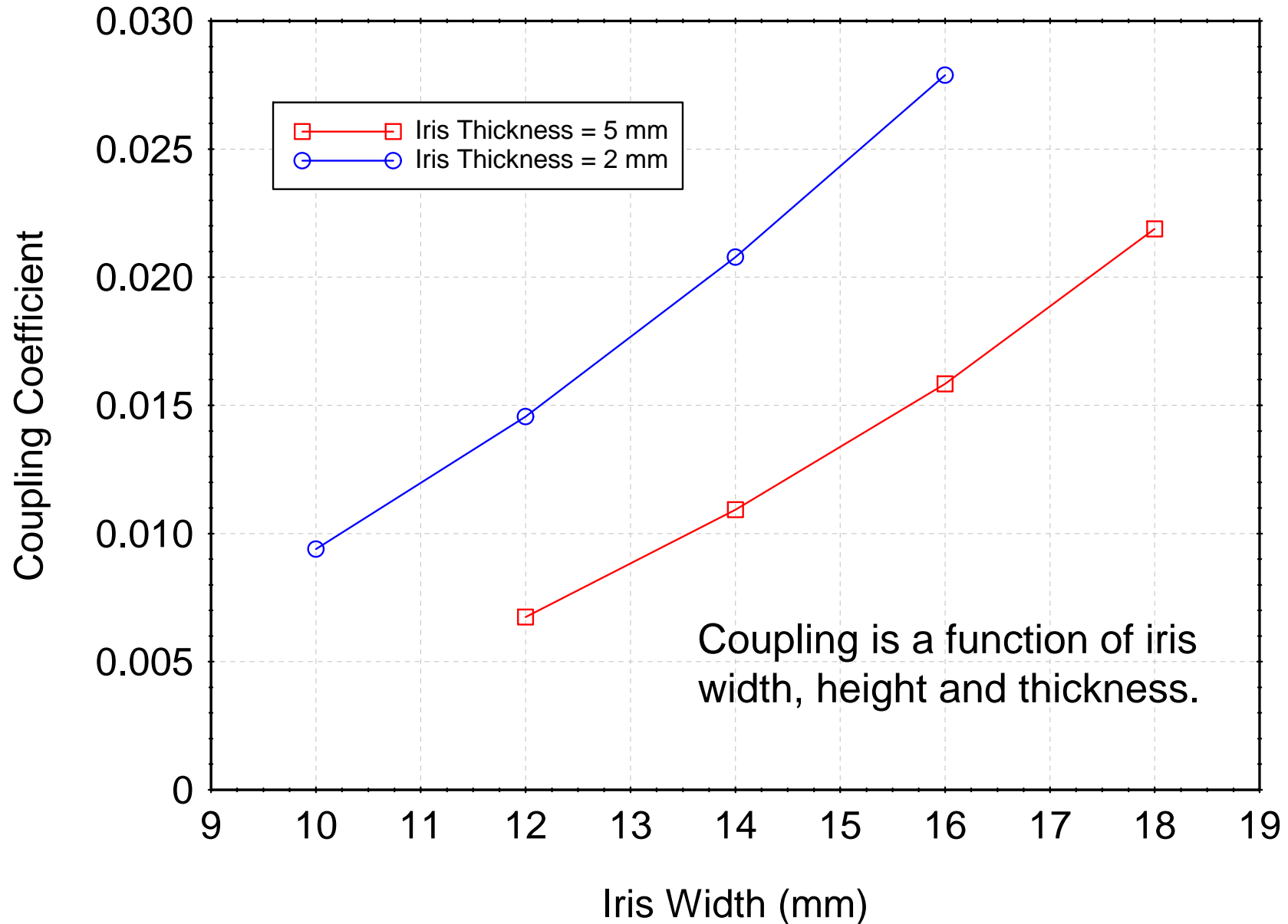

HFSS Project for Qex

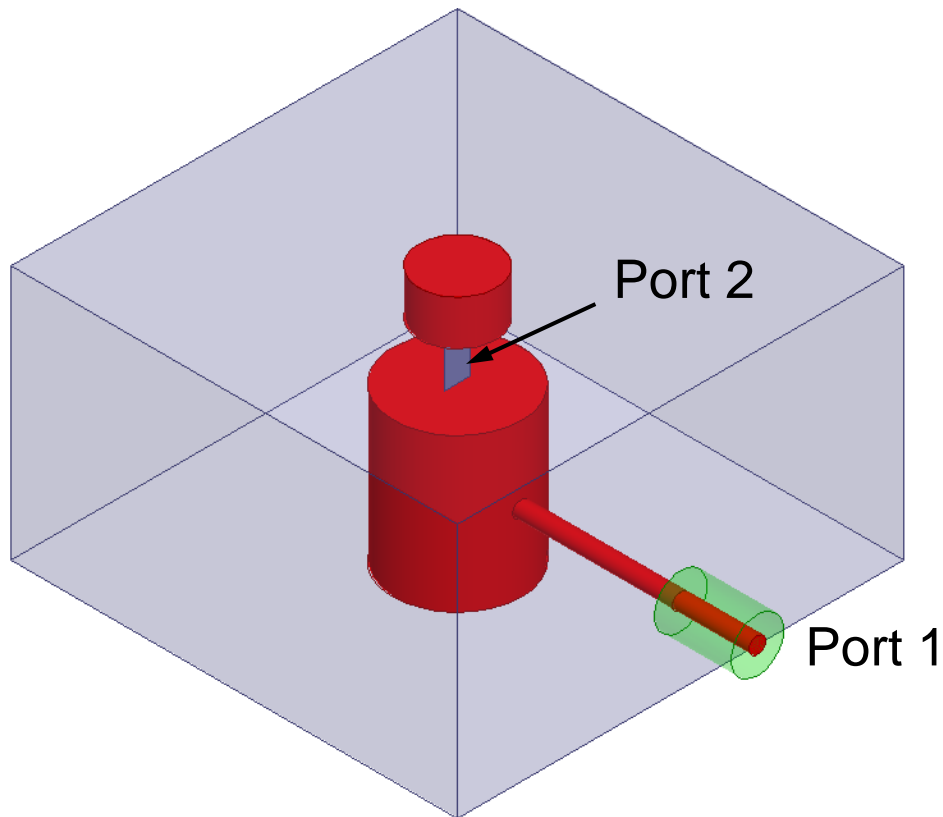


| Name | Value | Unit | Evaluated Value |
|------------------|-------|------|-----------------|
| Cavity_XY | 35 | mm | 35mm |
| Cavity_Z | 20 | mm | 20mm |
| Reso_Dia | 10 | mm | 10mm |
| Reso_Len | 12 | mm | 12mm |
| Tuning_Screw_Dia | 6 | mm | 6mm |
| Tuning_Screw_Len | 3.5 | mm | 3.5mm |
| Tap_Height | 6 | mm | 6mm |
| Tap_Line_Dia | 1.27 | mm | 1.27mm |

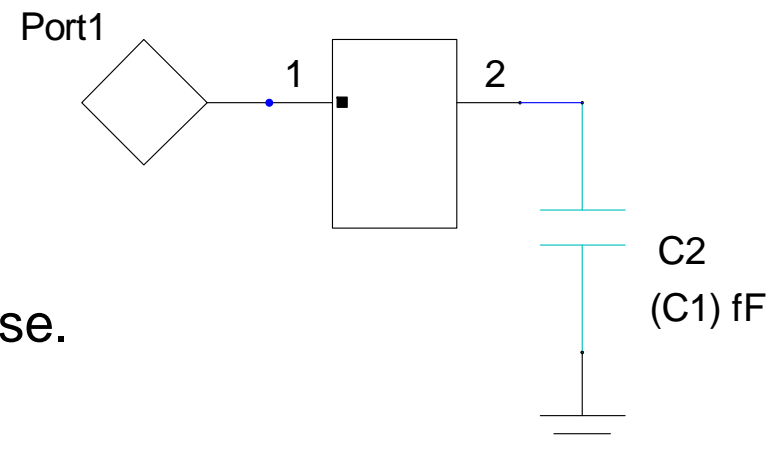


- Make the model parametric for future re-use.
- Tune to center frequency at Port 2.
- Measure reflected group delay at Port 1.
- Tap height sets the return loss level of our filter.

Port Tuned Reflected Delay

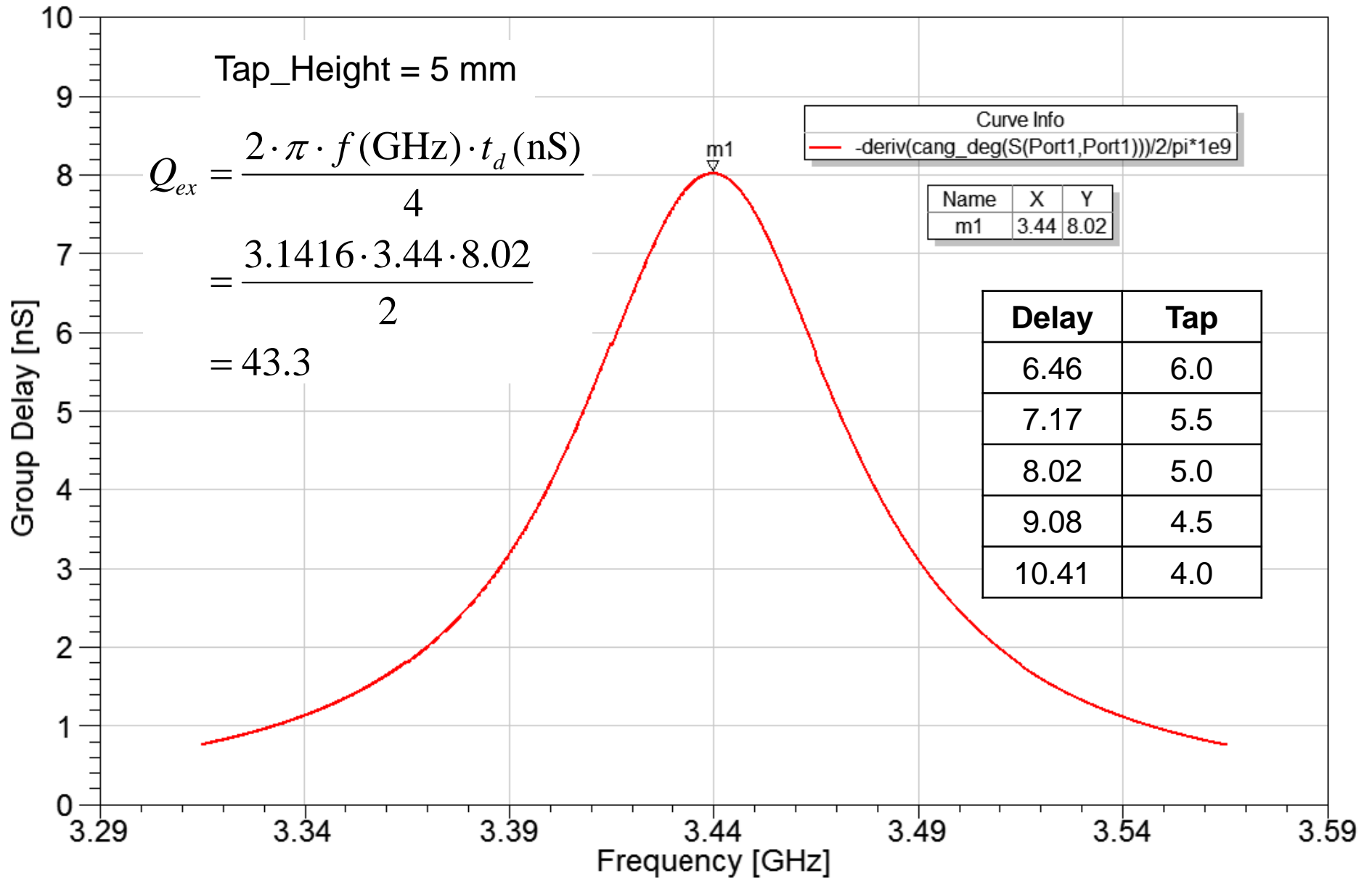

Qex Data Curve Fit in MathCAD

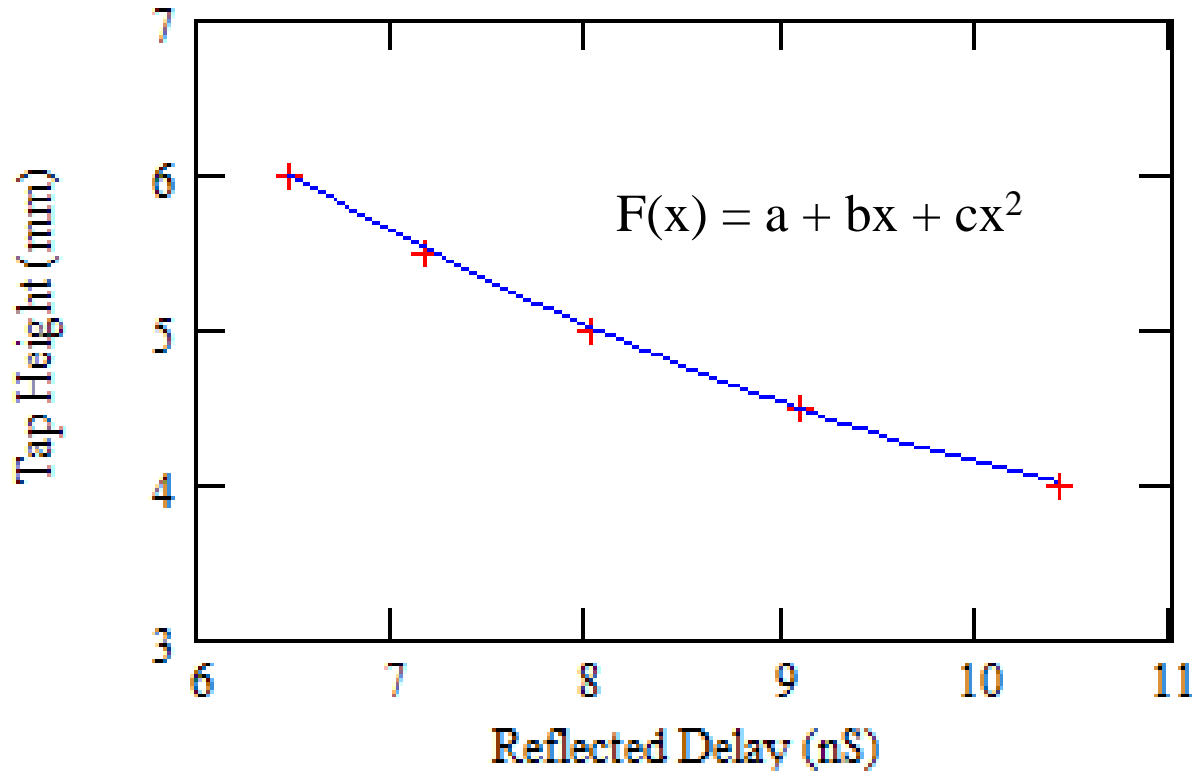

+++ X-Y data
 — Least-squares fit


$$\text{Tap Height} = 12.865 - 1.412 \cdot \text{Delay} + 0.054 \cdot \text{Delay}^2$$

$$S = \begin{pmatrix} 12.865 \\ -1.412 \\ 0.054 \end{pmatrix}$$

$$td := 7.96$$


$$\text{Tap_Height}(x) := F(x) \cdot S$$

$$\text{Tap_Height}(td) = 5.039$$

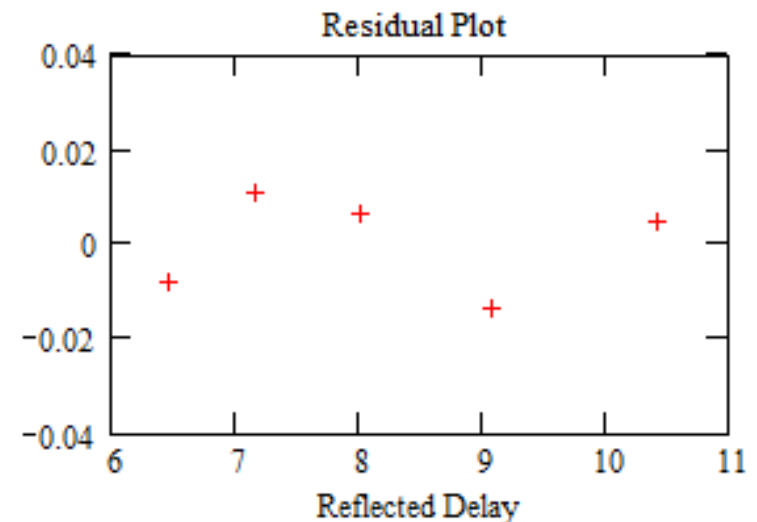


HFSS Model of Complete Filter

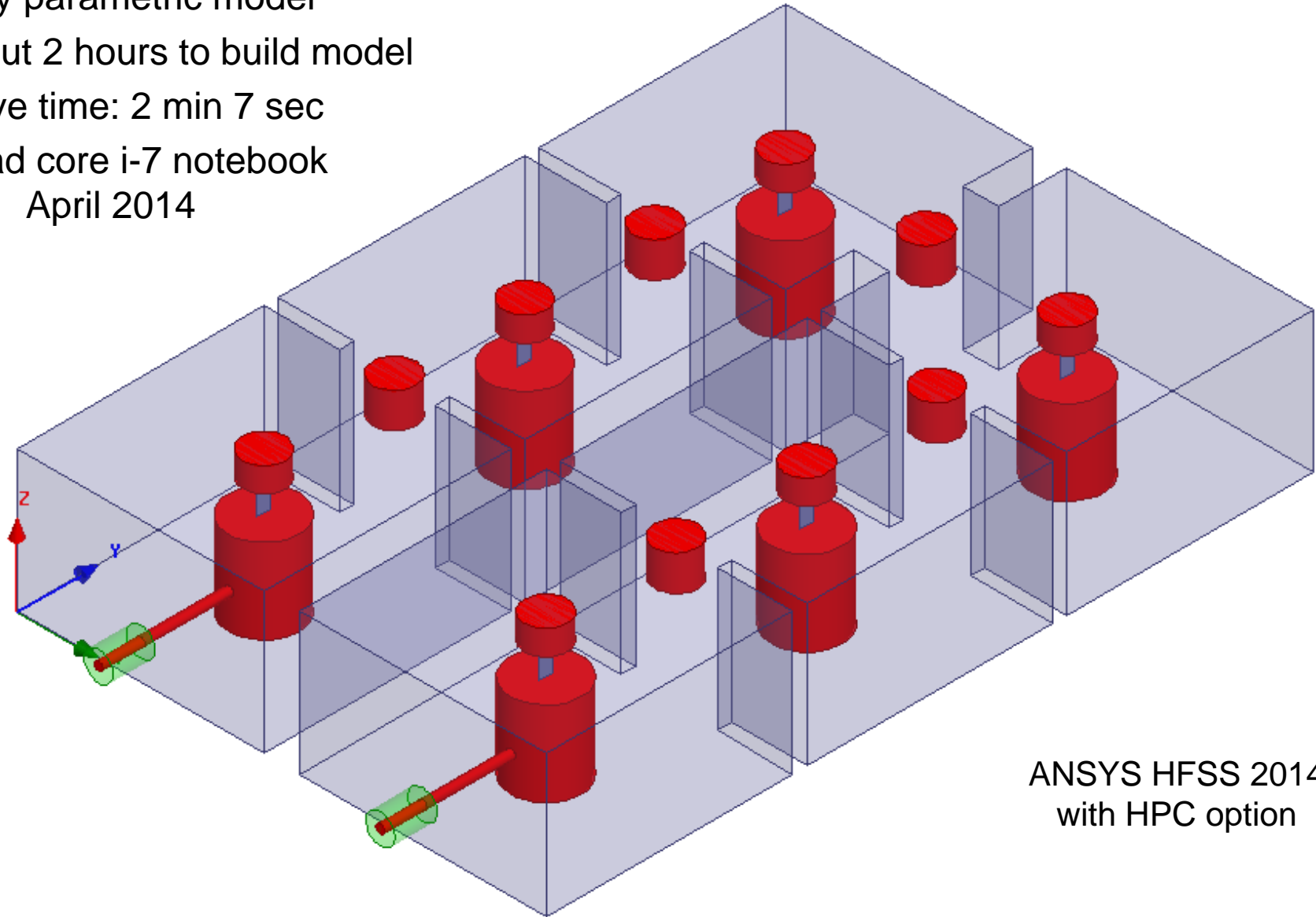- Fully parametric model
 - About 2 hours to build model
 - Solve time: 2 min 7 sec
 - Quad core i-7 notebook
- April 2014




ANSYS HFSS 2014
with HPC option

Initial Simulation – No Tuning

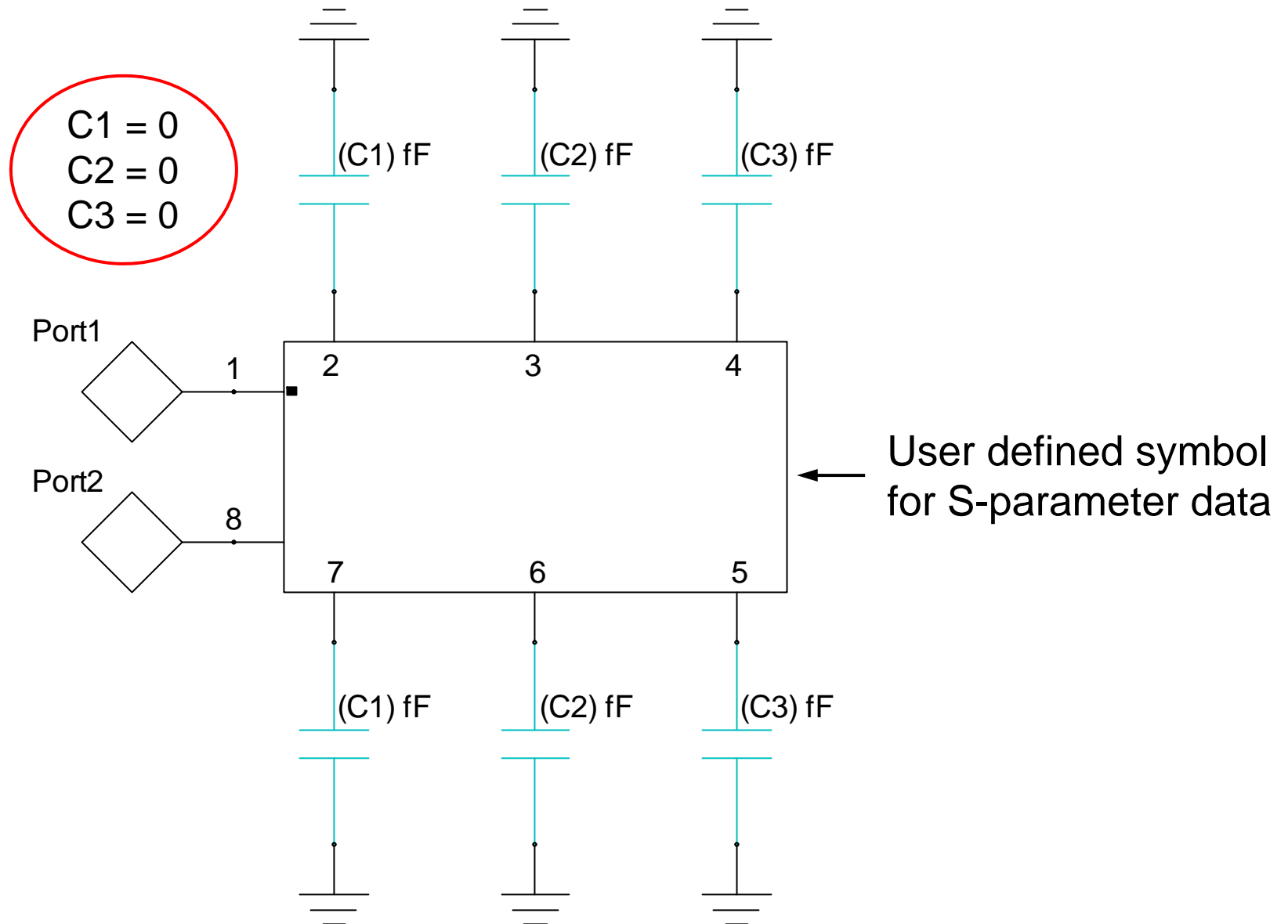


Initial Simulation – No Tuning

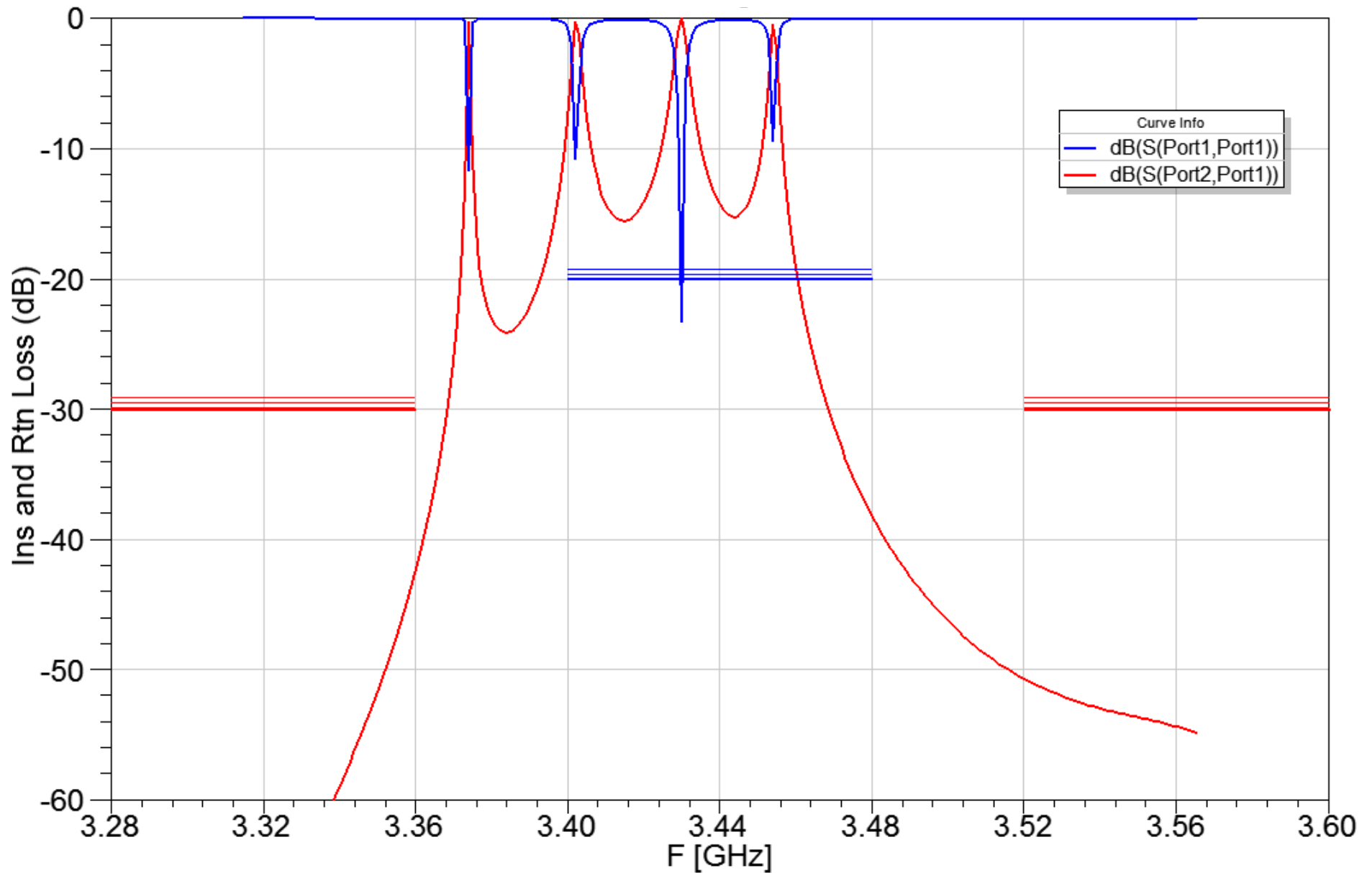


Symmetrical Tune of Resonators

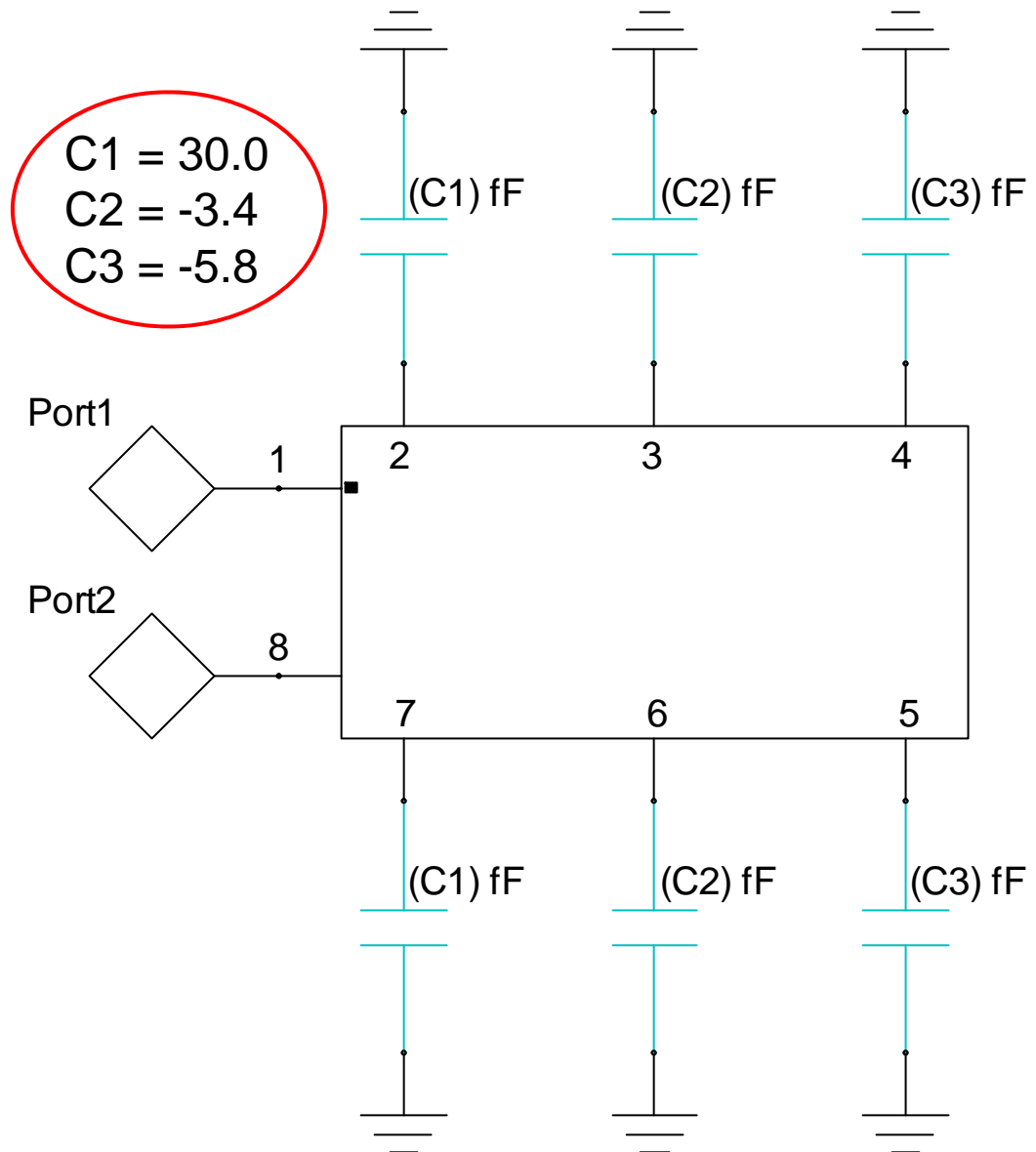
- Only tune the resonators, not the couplings.
- Use symmetry to reduce the number of variables.
- We can tune this manually, don't need an optimizer.



Symmetrical Tune of Resonators

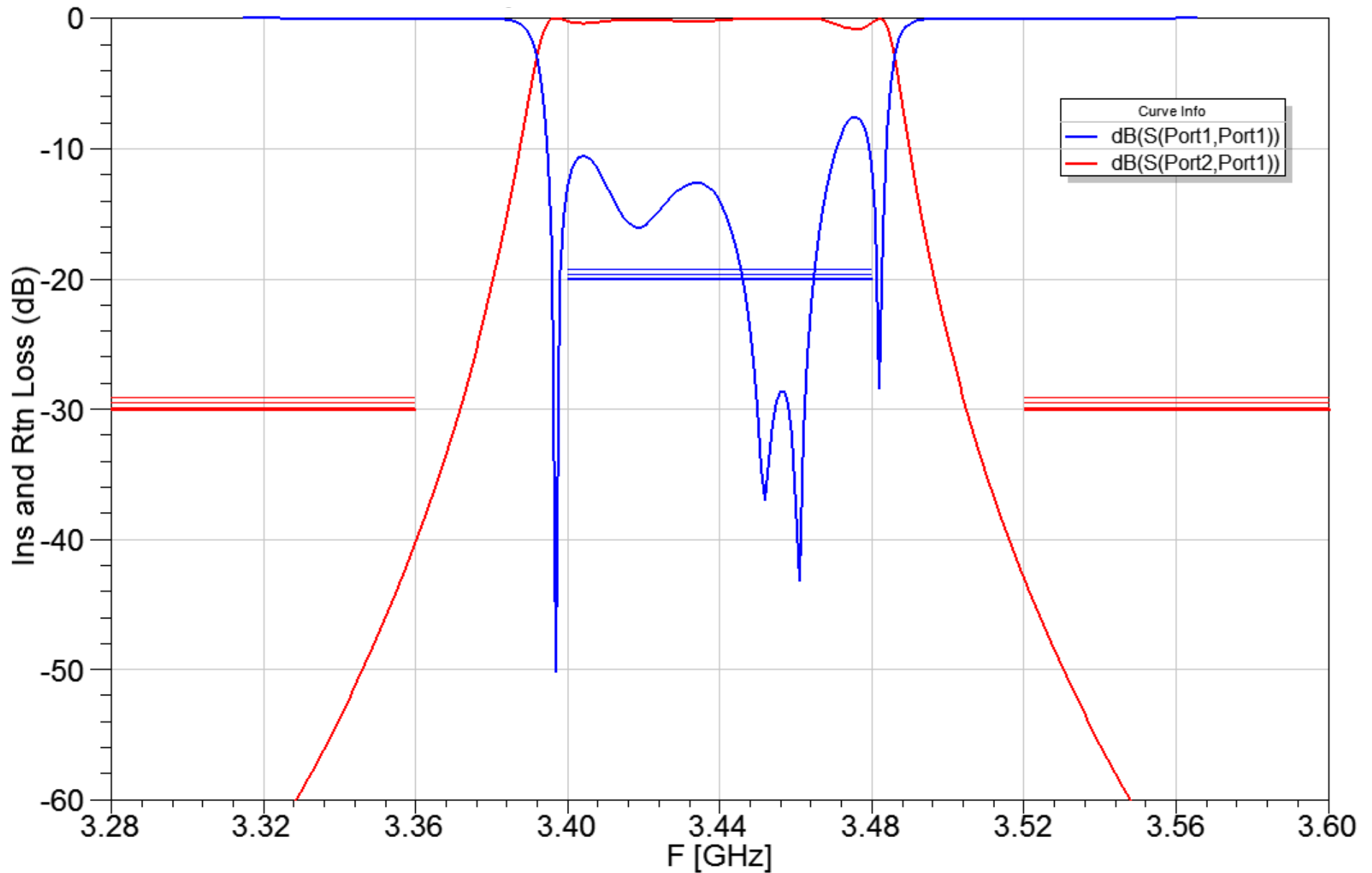


Full Port Tune with EQR_OPT

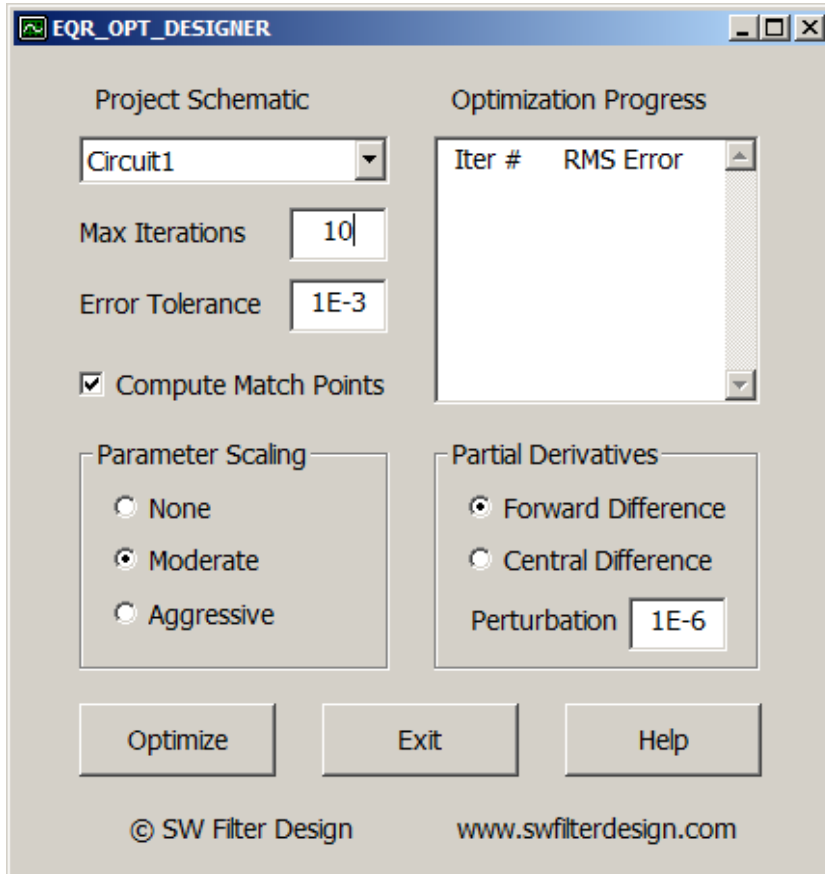


Note: Units are fF and pH

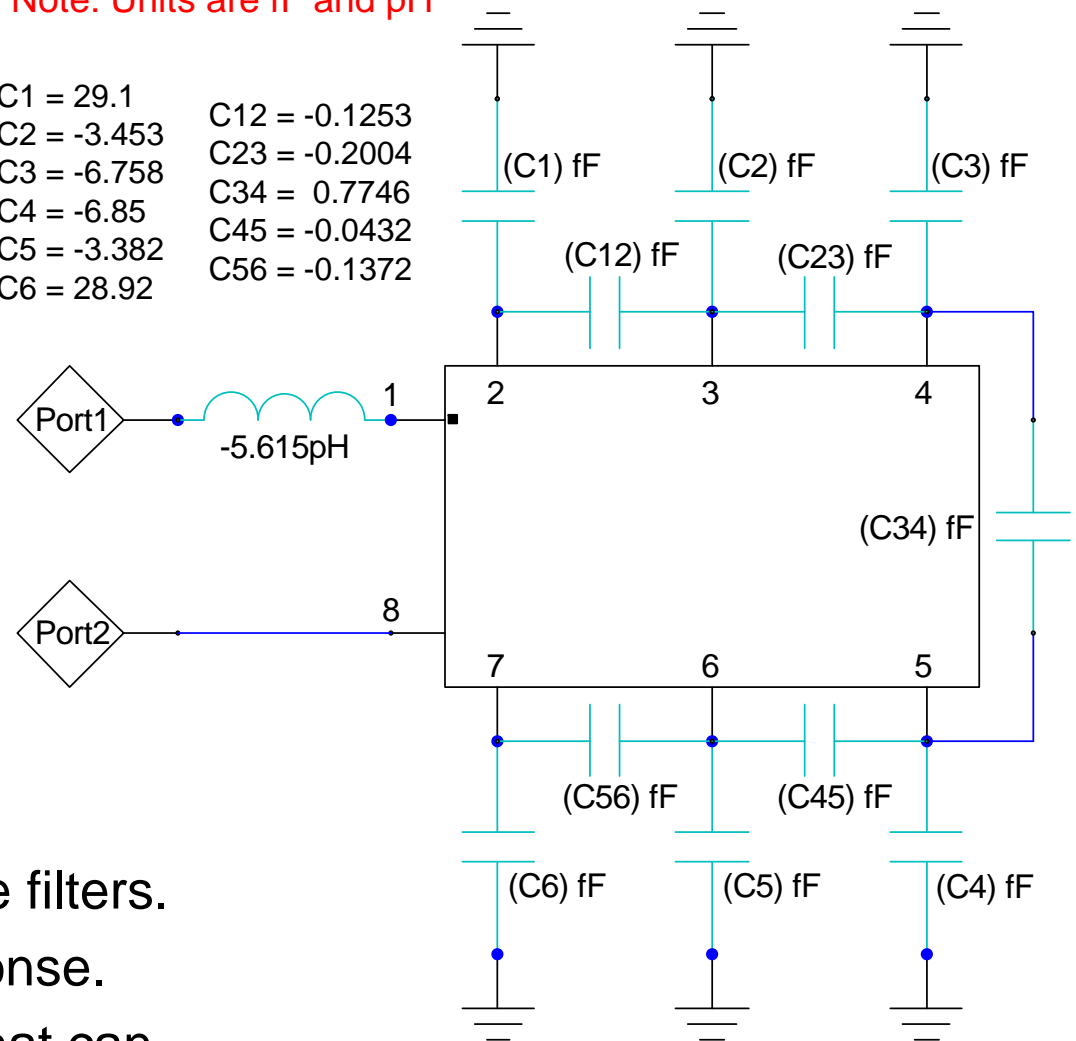C1 = 29.1
 C2 = -3.453
 C3 = -6.758
 C4 = -6.85
 C5 = -3.382
 C6 = 28.92
 C12 = -0.1253
 C23 = -0.2004
 C34 = 0.7746
 C45 = -0.0432
 C56 = -0.1372



- Dedicated optimizer for microwave filters.
- It finds an exact equal ripple response.
- It works on any Chebyshev filter that can be defined in your circuit simulator.

Full Port Tune of HFSS Model

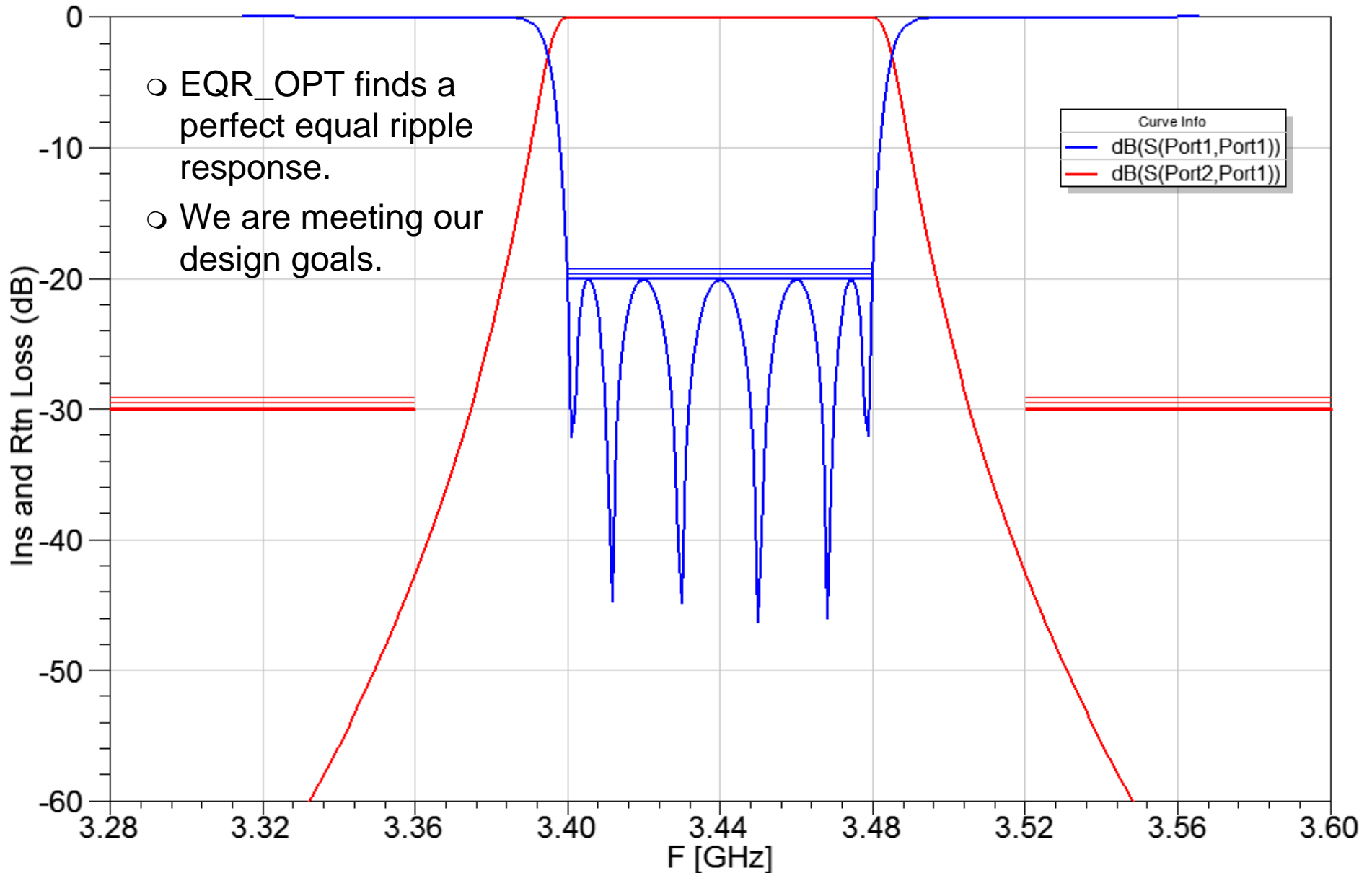


Moving The Tuning Screws

- The largest errors are the first and last resonator tunings.
- This is a well known characteristic of tapped resonators.
- We can move the tuning screws in the HFSS model to get a feel for the amount of correction needed.

Note: Units are fF and pH

→ C1 = 29.1
C2 = -3.453
C3 = -6.758
C4 = -6.85
C5 = -3.382
C6 = 28.92

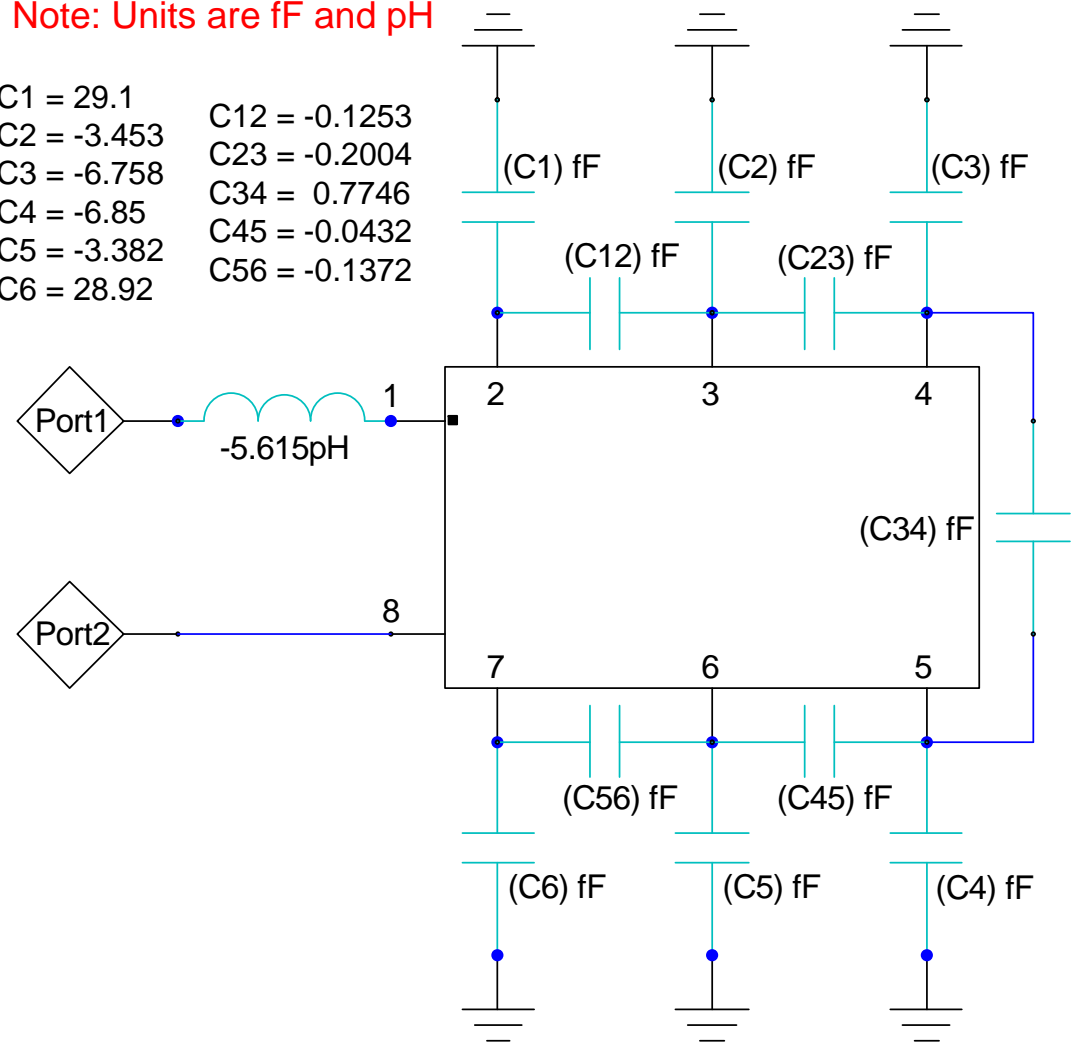→ C12 = -0.1253
C23 = -0.2004
C34 = 0.7746
C45 = -0.0432
C56 = -0.1372




Tuning Results


| Variable | Initial Screw Depths (mm) | Initial Tunings (fF) | Final Screw Depths (mm) | Final Tunings (fF) |
|----------|---------------------------|----------------------|-------------------------|--------------------|
| C1 | 3.5 | 29.100 | 4.33 | 1.168 |
| C2 | 3.5 | -3.453 | 3.35 | 0.224 |
| C3 | 3.5 | -6.850 | 3.27 | 0.148 |
| C4 | 3.5 | -6.850 | 3.27 | -0.132 |
| C5 | 3.5 | -3.382 | 3.35 | 0.223 |
| C6 | 3.5 | 28.920 | 4.33 | 0.659 |
| C12 | 5.0 | -0.125 | 5.2 | 0.031 |
| C23 | 5.0 | -0.020 | 5.0 | -0.028 |
| C34 | 5.0 | 0.775 | 2.8 | 0.043 |
| C45 | 5.0 | -0.043 | 5.0 | -0.036 |
| C56 | 5.0 | -0.137 | 5.2 | 0.019 |

- We see strong symmetry in the initial tunings.
- We see some numerical noise in the final tunings.

HFSS Simulation With Loss

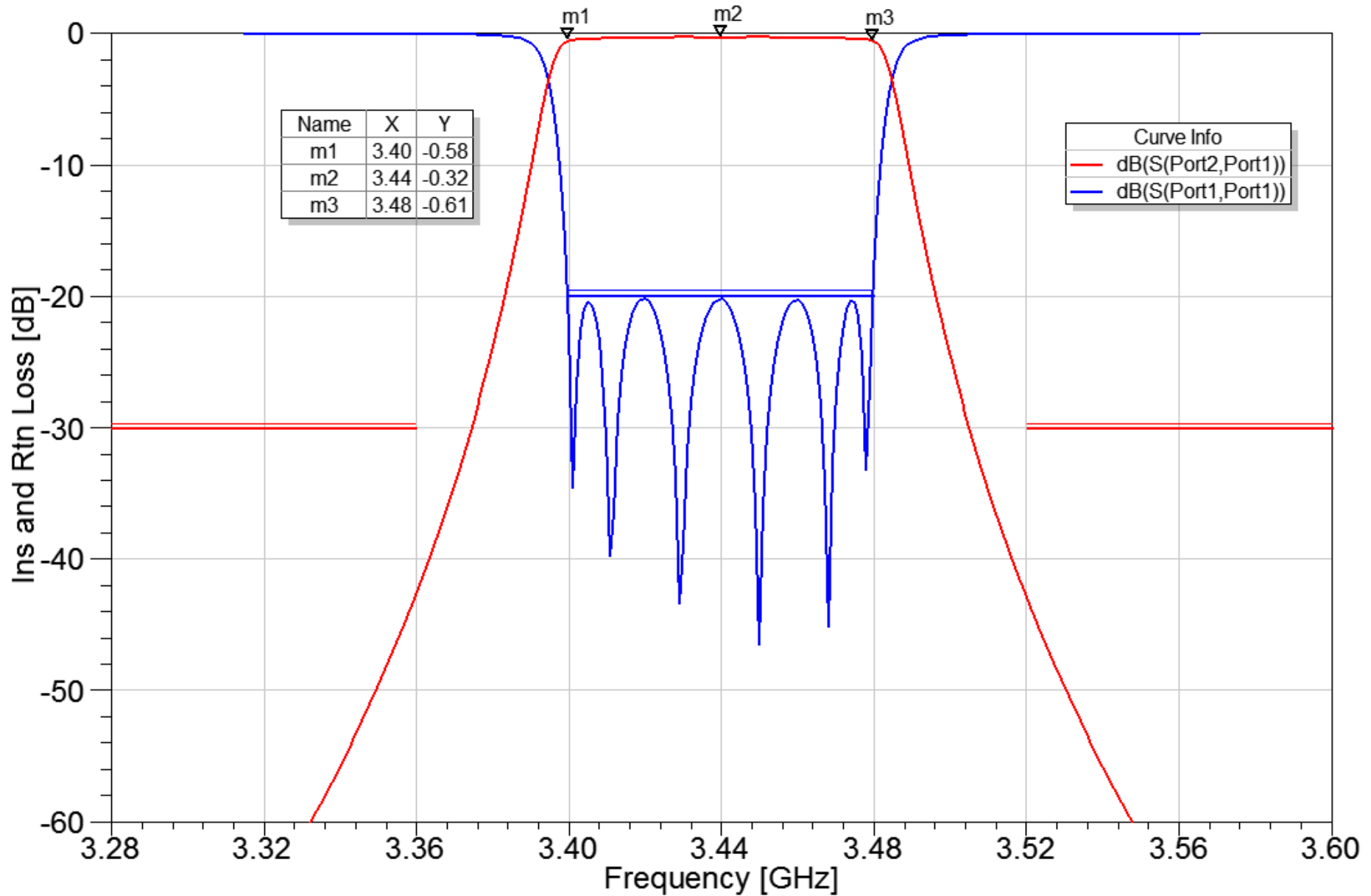

Computing Average Qu

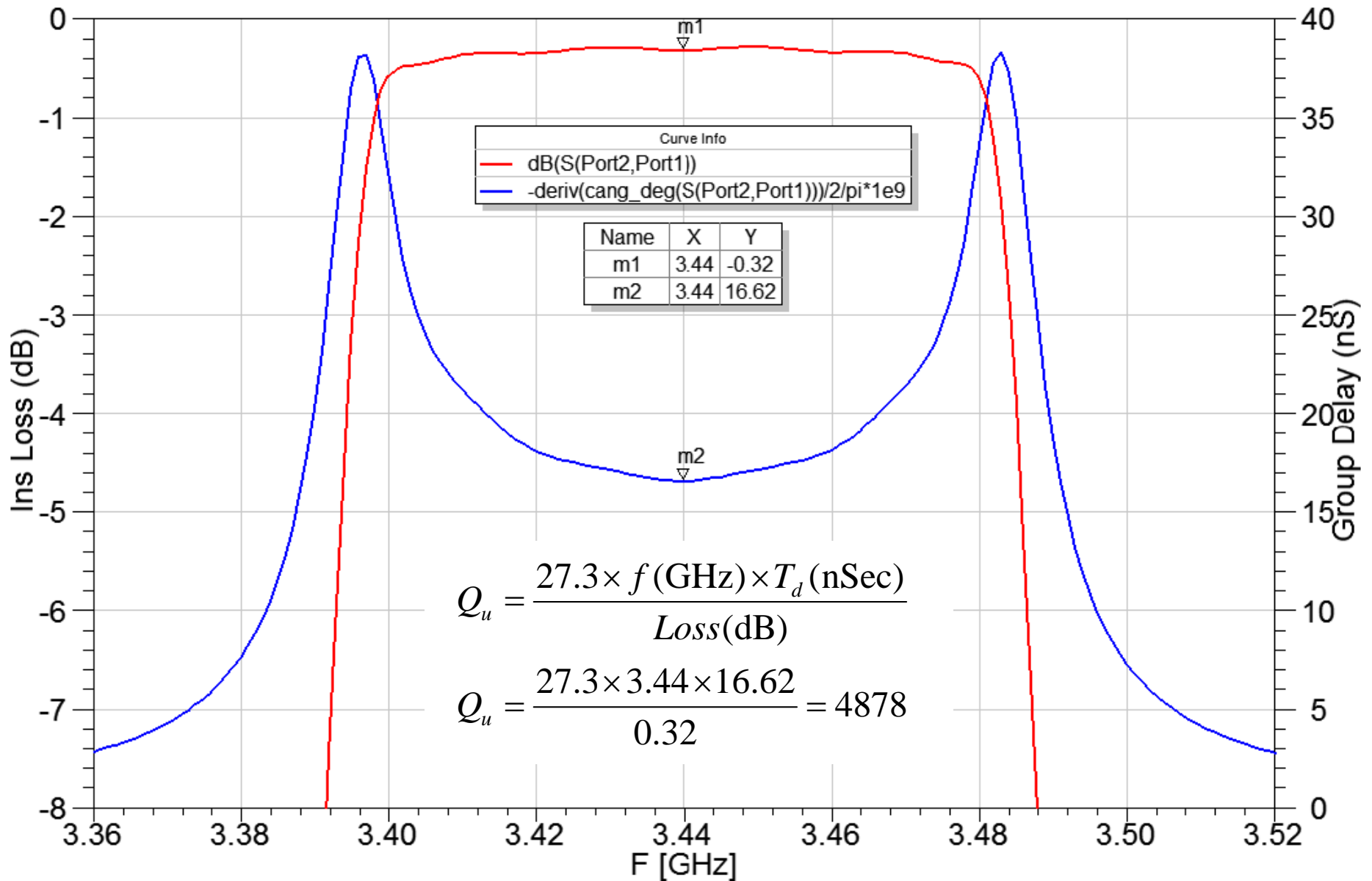

Summary

- Dishal's K and Q method leads us to a simple design flow for narrowband filters.
- We can modernize the method by using HFSS to build the K_{ij} and Q_{ex} design curves that we need.
- We can then build a complete model of our filter in HFSS, port tune it and get a very good prediction of performance.
- These virtual prototypes in HFSS avoid the time and expense of multiple hardware prototypes.
- Experience has shown that we can rely on the HFSS filter model.

References

- [1] R. Levy, R. Snyder and G. Matthaei, “Design of Microwave Filters,” *IEEE Trans. Microwave Theory Tech.*, vol. MTT-50, pp. 783-793, March 2002.
- [2] M. Dishal, “Alignment and adjustment of synchronously tuned multiple resonate circuit filters,” *Proc IRE*, vol. 30, pp. 1448-1455, Nov. 1951.
- [3] M. Dishal, “A simple design procedure for small percentage bandwidth round-rod interdigital filters,” *IEEE Trans. Microwave Theory Tech.*, vol. MTT-13, pp. 696-698, Sept. 1965.
- [4] J. Wong, “Microstrip tapped-line filter design,” *IEEE Trans. Microwave Theory Tech.*, vol. MTT-27, pp. 44-50, Jan. 1979.
- [5] D. G. Swanson, Jr., “Narrow-Band Microwave Filter Design,” *IEEE Microwave Magazine*, vol. 8, no. 5, pp. 105-114, Oct. 2007.
- [6] D. G. Swanson, Jr., “Corrections to “Narrow-Band Microwave Filter Design,” *IEEE Microwave Magazine*, vol. 9, no. 1, p. 116, Feb. 2008.