

# **ANALOG ELECTRONIC CIRCUITS**

**D. K. KAUSHIK**

**DHANPAT RAI PUBLISHING COMPANY**

# Contents

<i>Chapter</i>	<i>Page No.</i>
Preface .....	iii
<b>Chapter 1– Transducers .....</b>	<b>1–31</b>
1.1 Classification of transducers .....	1
1.2 Selection criteria for transducer .....	3
1.3 Resistance strain gauge .....	3
1.4 Types of strain gauges.....	6
1.5 Potentiometric transducer .....	10
1.6 Resistance thermometer .....	12
1.7 Thermistor .....	13
1.8 Thermocouples .....	14
1.9 Photoelectric transducers .....	14
1.9.1 Vacuum photo tube .....	15
1.9.2 Gas filled phototubes .....	16
1.9.3 Photomultiplier tubes.....	16
1.9.4 Photo conductive cell .....	17
1.9.5 Photo voltaic cell .....	18
1.9.6 Photo junctions .....	19
1.10 Capacitive transducers .....	20
1.11 Inductive transducers .....	21
1.11.1 Change in self inductance with number of turns .....	22
1.11.2 Change in self inductance with change in permeability .....	22
1.11.3 Variable reluctance type transducers .....	22
1.11.4 Linear variable differential transducer (LVDT) .....	24
1.12 Piezoelectric transducer .....	27
1.13 Microphones .....	28
1.13.1 Carbon microphone .....	28

vi		
1.13.2	Moving coil microphone .....	29
1.13.3	Crystal microphone .....	29
1.13.4	Capacitor microphone .....	30
1.14	Loudspeaker .....	30
<b>Chapter 2–IC Fabrication</b>	.....	<b>32–61</b>
2.1	Integrated circuit technology .....	32
2.2	Advantages of integrated circuits (ICs) .....	33
2.2.1	Limitations of the integrated circuits .....	34
2.3	Basic monolithic integrated circuits .....	34
2.3.1	Wafer Preparation .....	35
2.3.2	Epitaxial Growth .....	36
2.3.3	Masking and etching .....	38
2.3.4	Diffusion of impurities .....	41
2.3.5	Metallization .....	41
2.4	The planar technology .....	43
2.5	Monolithic integrated circuits technology .....	43
2.5.1	p-n junction isolation .....	44
2.5.2	Dielectric isolation .....	45
2.5.3	V-groove isolation .....	45
2.6	Formation of monolithic integrated circuit components .....	46
2.6.1	n-p-n transistors .....	46
2.6.2	Diodes .....	47
2.6.3	Resistors .....	49
2.6.4	Capacitors .....	51
2.6.5	p-n-p transistors .....	52
2.7	Monolithic junction field effect transistors .....	53
2.8	MOS field effect transistors .....	54
2.9	IC Crossovers .....	55
2.10	Complete integrated circuit formation .....	56
<b>Chapter 3– Feedback Amplifiers</b>	.....	<b>62–78</b>
3.1	Classification of amplifiers .....	62
3.1.1	Voltage amplifiers .....	62
3.1.2	Current amplifiers .....	63
3.1.3	Transconductance amplifiers .....	64
3.1.4	Transresistance amplifiers .....	64
3.2	Classification of feedback .....	65
3.3	Feedback topologies .....	65

3.4	Effect of feedback on transfer gain .....	66
3.4.1	Transfer gain for voltage series feedback topology .....	66
3.4.2	Transfer gain for voltage shunt feedback topology .....	67
3.4.3	Transfer gain for current series feedback topology .....	68
3.4.4	Transfer gain for current shunt feedback topology .....	68
3.5	Effect of feedback on input resistance .....	69
3.5.1	Input resistance for voltage series feedback topology .....	69
3.5.2	Input resistance for current series feedback topology .....	70
3.5.3	Input resistance for voltage shunt feedback topology .....	71
3.5.4	Input resistance for current shunt feedback topology .....	71
3.6	Effect of feedback on output resistance .....	72
3.7	Practical feedback circuits .....	74
<b>Chapter 4– Operational Amplifiers .....</b>		<b>79–115</b>
4.1	The basic operational amplifier .....	79
4.2	The inverting amplifier .....	80
4.2.1	Practical inverting amplifier .....	81
4.3	The non-inverting amplifier .....	85
4.3.1	Input resistance of voltage series feedback amplifier .....	87
4.3.2	Output resistance of voltage series feedback amplifier .....	88
4.3.3	Frequency response of voltage series feedback amplifier .....	90
4.3.4	Stability in voltage series feedback amplifier .....	92
4.3.5	Distortion in voltage series feedback amplifier .....	94
4.4	Difference amplifier .....	94
4.5	Common mode rejection ratio .....	98
4.6	Emitter coupled differential amplifier .....	100
4.6.1	Emitter coupled differential amplifier using constant current bias .....	103
4.6.2	Use of current mirror as constant current source .....	105
4.7	IC 741 operational amplifier .....	106
<b>Chapter 5– Applications of Operational Amplifiers .....</b>		<b>116–157</b>
5.1	Error voltages and currents in operational amplifiers .....	116
5.1.1	Input bias current .....	116
5.1.2	Input offset current .....	119
5.1.3	Input offset voltage .....	120
5.1.4	Thermal drift .....	125
5.2	Applications of operational amplifiers .....	126
5.2.1	Sign changer .....	126
5.2.2	Phase shifter .....	126

viii		
5.3	Summing amplifier .....	127
5.3.1	Non-inverting summing amplifier .....	128
5.4	Current-to-Voltage converter .....	130
5.5	Voltage -to - current converter .....	131
5.6	D.C. voltage follower .....	131
5.7	A.C. coupled amplifier .....	132
5.7.1	A.C. voltage follower .....	133
5.8	Bridge amplifier .....	133
5.9	Integrator .....	135
5.9.1	Practical integrator .....	137
5.10	Differentiator .....	139
5.11	Logarithmic amplifier .....	141
5.12	Antilogarithmic amplifier .....	143
5.13	Logarithmic multiplier .....	144

## Chapter 6- Regulated Power Supply ..... 158-192

6.1	Voltage regulator .....	158
6.1.1	Percentage regulation .....	159
6.1.2	Classification of voltage regulators .....	160
6.2	Series voltage regulator .....	160
6.2.1	Simple series regulator circuit .....	161
6.2.2	Improved series regulator circuit .....	162
6.2.3	Feedback type of voltage regulator .....	163
6.3	Shunt voltage regulator .....	168
6.3.1	Zener diode shunt regulator .....	168
6.3.2	Basic transistor shunt regulator .....	170
6.3.3	Improved shunt regulator .....	170
6.4	Regulators using operational amplifiers .....	173
6.4.1	Series voltage regulator using operational amplifier .....	173
6.4.2	Modified zener biasing .....	175
6.4.3	Short circuit protection .....	177
6.5	Shunt voltage regulator using op-amp .....	178
6.6	Adjustable voltage regulator ICs .....	178
6.6.1	IC 723 voltage regulator .....	179
6.6.2	Three terminal adjustable voltage regulator ICs .....	180
6.6.3	Three terminal fixed voltage regulator ICs .....	181
6.7	Switch mode power supply (SMPS) .....	186

<b>Chapter 7– Sinusoidal Oscillators .....</b>	<b>193–238</b>
7.1 Principle of operation .....	193
7.2 Negative resistance .....	196
7.3 Classification of oscillators .....	197
7.4 R C phase shift oscillator .....	197
7.4.1 Transistor phase shift oscillator .....	199
7.4.2 Operational amplifier phase shift oscillator .....	202
7.5 The wien bridge oscillator .....	208
7.6 L-C oscillator .....	213
7.7 Tuned drain FET oscillator .....	215
7.7 Tuned collector oscillator .....	218
7.8 General form of resonant circuit oscillators .....	220
7.9 Transistor Hartley oscillator .....	223
7.10 Transistor Colpitt's oscillator .....	226
7.11 Crystal oscillator .....	229
<b>Chapter 8– Multivibrators .....</b>	<b>239–275</b>
8.1 Bistable multivibrator .....	239
8.2 Triggering methods of bistable multivibrator .....	242
8.2.1 Asymmetrical triggering .....	243
8.2.2 Symmetrical triggering .....	245
8.3 Monostable multivibrator .....	248
8.3.1 Collector coupled monostable multivibrator .....	251
8.3.2 Emitter coupled monostable multivibrator .....	252
8.4 Astable multivibrator .....	252
8.5 Comparator .....	255
8.6 Schmitt trigger .....	257
8.7 Astable multivibrator using an operational amplifier .....	259
8.8 Monostable multivibrator using an operational amplifier .....	262
8.9 Triangular waveform generator .....	264
8.10 Timer IC 555 .....	267
8.10.1 Monostable operation .....	268
8.10.2 Astable operation .....	270
8.10.3 Saw tooth generator .....	272
8.10.4 Voltage controlled oscillator .....	273
<b>Chapter 9– Active Filters .....</b>	<b>276–297</b>
9.1 Active filters .....	276
9.2 First order low pass filter .....	277
9.3 Second order low pass filter .....	279

9.4	First order high pass filter .....	282
9.5	Second order high pass filter .....	283
9.6	Higher order filters .....	285
9.7	Band pass filters .....	287
9.7.1	Wide band pass filter .....	287
9.7.2	Narrow band pass filter .....	289
9.8	Band rejection filters .....,	291
9.8.1	Wide band rejection filter .....	291
9.8.2	Narrow band rejection filter .....	292
	<b>Chapter 10– Bridge Circuits .....</b>	<b>298–319</b>
10.1	Wheatstone bridge .....	298
10.1.1	Thevenin's equivalent Wheatstone bridge .....	299
10.1.2	Slightly unbalance Wheatstone bridge .....	300
10.1.3	Sources of errors in Wheatstone bridge .....	301
10.2	Kelvin bridge .....	302
10.2.1	Practical kelvin double bridge .....	304
10.3	A.C. bridges .....	305
10.4	Maxwell bridge .....	306
10.5	Hay bridge .....	307
10.6	Schering bridge .....	309
10.7	Wien bridge .....	310
10.8	Wagner ground connection .....	312
	<b>Chapter 11– Switching Devices and Circuits .....</b>	<b>320–335</b>
11.1	Unijunction transistor .....	320
11.2	Unijunction transistor relaxation oscillator .....	322
11.3	Silicon controlled rectifier .....	323
11.4	Half wave series static switch .....	326
11.5	Phase control circuit .....	326
11.6	SCR half wave rectifier .....	327
11.7	SCR full wave rectifier .....	328
11.8	Silicon controlled switch .....	329
11.8	The triac .....	331
11.10	The diac .....	332
11.11	Dimmer circuit .....	333