

0/20

Roll No.

(12/24)

5156

**B.Sc.B.Ed. (4 Years) (For Batch 2011 &
Onwards)/B.A./B.Sc. (First Semester)
(For Batch 2011 to 2020 Only)**

EXAMINATION

COMPUTER SCIENCE : LOGICAL
ORGANIZATION
OF COMPUTER-I

Paper-II

Time : Three Hours

Maximum Marks : 30

Note : Attempt *Five* questions in all, selecting *one* question from each Unit. Q. No. 1 is compulsory.

1. (a) Universal Gate
- (b) Full Adder

(c) Multiplexer

(d) Number System.

$$1.5 \times 4 = 6$$

Unit I

2. (a) Explain ASCII Code and EBCDIC Code in Detail.

(b) Explain Error Detecting and Correcting Code.

$$3 \times 2 = 6$$

Or

3. (a) What do you mean by Number System ? Explain types of Number System in detail.

2

(b) Convert the following Decimal number in to Hexadecimal Number :

$$1 \times 4 = 4$$

(i) 238

(ii) 7547

(iii) 4246.625

(iv) 1046.25

Unit II

4. (a) Write any five Postulates of Boolean Algebra.

(b) What do you mean by Duality Principle and Distributive Law ? Explain with the help of Example.

$$3 \times 2 = 6$$

Or

5. (a) Simply :

$$f(A, B, C, D) = \Pi(4, 6, 10, 12,$$

13, 15)

Using K Map.

(b) $XY + XYZ + X(Y + XY)$ by Boolean Expression.

$$3 \times 2 = 6$$

Unit III

6. (a) Explain Basic GATES in Detail.
(b) Explain NAND, NOR, XNOR, Universal Gate. $3 \times 2 = 6$

Or

7. (a) Explain Multilevel NAND and NOR Circuits.
(b) Implement the following Boolean Functions :
 $F = (A + B + \bar{C}).(BD + E)$ Using NAND Gate. $3 \times 2 = 6$

Unit IV

8. (a) What is the function of Code Converter ? Explain with diagram.
(b) Write about combination circuits in detail. $3 \times 2 = 6$

Or

9. (a) Explain Multiplexer and Demultiplexers.
(b) Explain Encoder and Decoder in detail. $3 \times 2 = 6$