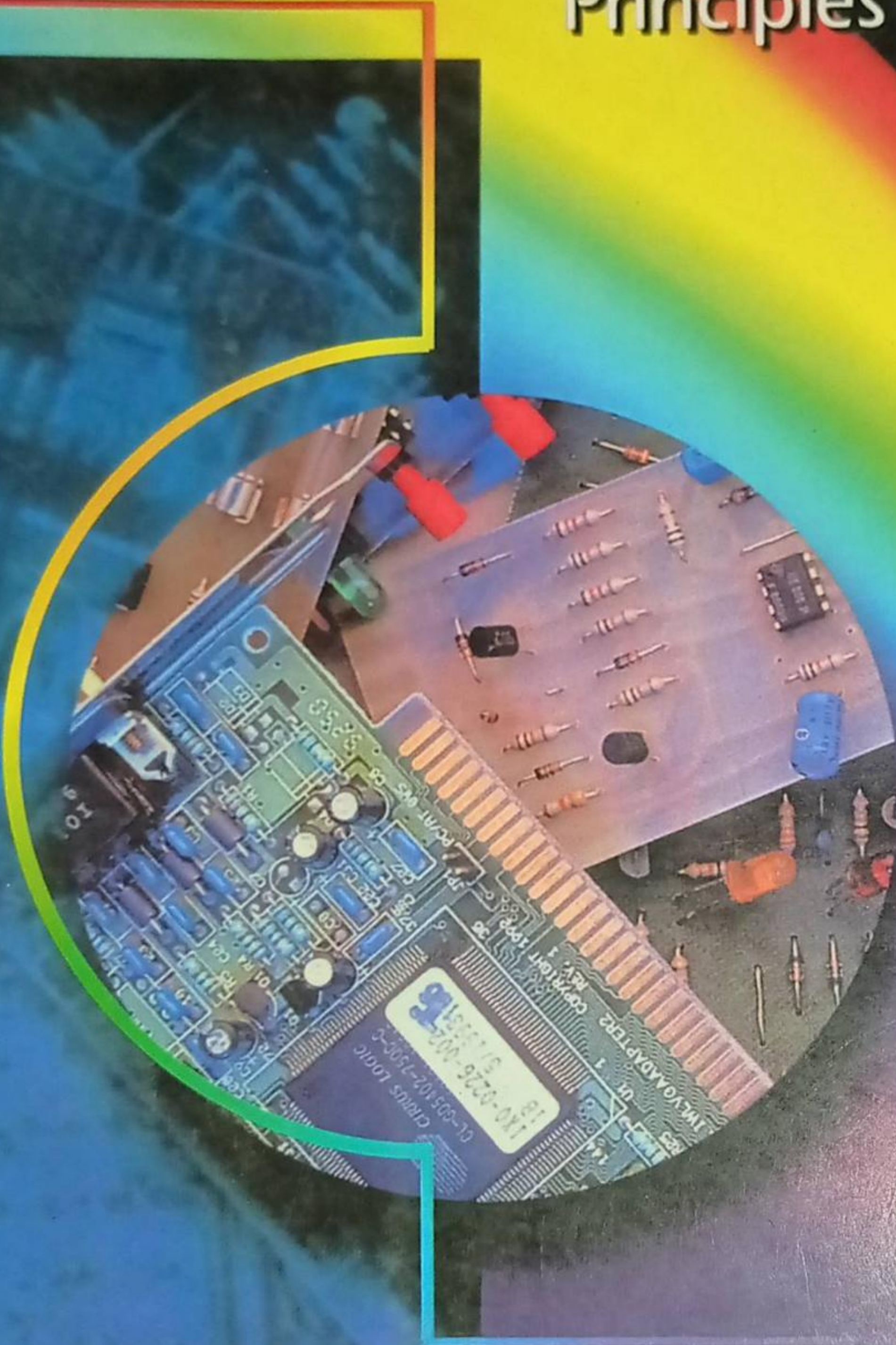


TATA McGRAW-HILL
EDITION

DIGITAL ELECTRONICS

Principles and Applications



Fifth Edition

Tokheim

Basic Skills in Electricity and Electronics

001-552

Contents

Editor's Foreword	v
Preface	vi
Acknowledgments	vii
Safety	viii

Chapter 1 Digital Electronics 1

1-1	What Is Digital Circuit	1
1-2	Where Are Digital Circuits Used?	3
1-3	Why Use Digital Circuits	10
1-4	How Do You Make a Digital Signal?	12
1-5	How Do You Test for a Digital Signal	15

Chapter 2 Numbers We Use in Digital Electronics 21

2-1	Counting in Decimal and Binary	21
2-2	Place Value	22
2-3	Binary to Decimal Conversion	23
2-4	Decimal to Binary Conversion	24
2-5	Electronic Translators	24
2-6	Hexadecimal Numbers	25
2-7	Octal Numbers	27

Chapter 3 Logic Gates 31

3-1	The AND Gate	31
3-2	The OR Gate	33
3-3	The Inverter and Buffer	34
3-4	The NAND Gate	35
3-5	The NOR Gate	36
3-6	The Exclusive OR Gate	37
3-7	The Exclusive NOR Gate	38
3-8	The NAND Gate as a Universal Gate	38
3-9	Gates with More Than Two Inputs	38
3-10	Using Inverters to Convert Gates	41
3-11	Practical TTL Logic Gates	43
3-12	Practical CMOS Logic Gates	47
3-13	Troubleshooting Simple Gate Circuits	49
3-14	IEEE Logic Symbols	51

Chapter 4 Using Logic Gates 57

4-1	Constructing Circuits from Boolean Expressions	57
-----	--	----

4-2	Drawing a Circuit from a Maxterm Boolean Expression	59
4-3	Truth Tables and Boolean Expressions	60
4-4	Sample Problem	62
4-5	Simplifying Boolean Expressions	63
4-6	Karnaugh Maps	64
4-7	Karnaugh Maps with Three Variables	65
4-8	Karnaugh Maps with Four Variables	67
4-9	More Karnaugh Maps	68
4-10	A Five-Variable Karnaugh Map	69
4-11	Using NAND Logic	70
4-12	Solving Logic Problems the Easy Way	71
4-13	More Data Selector Problems	74
4-14	Using DeMorgan's Theorems	77

Chapter 5 IC Specifications and Simple Interfacing 86

5-1	Logic Levels and Noise Margin	86
5-2	Other Digital IC Specifications	90
5-3	MOS and CMOS ICs	94
5-4	Interfacing TTL and CMOS with Switches	96
5-5	Interfacing TTL and CMOS with LEDs	98
5-6	Interfacing TTL and CMOS ICs	101
5-7	Interfacing with Buzzers, Relays, Motors, and Solenoids	105
5-8	Optoisolators	109
5-9	Interfacing with Stepper Motors	111
5-10	Troubleshooting Simple Logic Circuits	116

Chapter 6 Encoding, Decoding, and Seven-Segment Displays 122

6-1	The 8421 BCD Code	122
6-2	The Excess-3 Code	123
6-3	The Gray Code	124
6-4	The ASCII Code	125
6-5	Encoders	125
6-6	Seven-Segment LED Displays	127
6-7	Decoders	130
6-8	BCD-to-Seven-Segment Decoder/Drivers	131
6-9	Liquid-Crystal Displays	134
6-10	Using CMOS to Drive an LCD	138
6-11	Vacuum Fluorescent Displays	139
6-12	Driving a VF Display	142
6-13	Troubleshooting a Decoding Circuit	146

Chapter 7 Flip-Flops 154

7-1	The R-S Flip Flop	154
7-2	The Clocked R-S Flip-Flop	156
7-3	The D Flip-Flop	158
7-4	The J-K Flip-Flop	160
7-5	IC Latches	162
7-6	Triggering Flip-Flops	164
7-7	Schmitt Trigger	166
7-8	IEEE Logic Symbols	167

Chapter 8 Counters 173

8-1	Ripple Counters	173
8-2	Mod-10 Ripple Counters	175
8-3	Synchronous Counters	175
8-4	Down Counters	178
8-5	Self-Stopping Counters	179
8-6	Counters as Frequency Dividers	179
8-7	TTL IC Counters	181
8-8	CMOS IC Counters	183
8-9	Counting Real-World Events	189
8-10	Using a CMOS Counter in an Electric Game	193
8-11	Sequential Logic Troubleshooting Equipment	194
8-12	Troubleshooting a Counter	201

Chapter 9 Shift Registers 208

9-1	Serial Load Shift Registers	209
9-2	Parallel Load Shift Registers	211
9-3	A Universal Shift Register	213
9-4	Using the 74194 IC Shift Register	215
9-5	An 8-Bit CMOS Shift Register	218
9-6	Using Shift Registers—Digital Roulette	220
9-7	Troubleshooting a Simple Shift Register	225

Chapter 10 Arithmetic Circuits 231

10-1	Binary Addition	231
10-2	Half Adders	232
10-3	Full Adders	233
10-4	Three-Bit Adders	235
10-5	Binary Subtraction	236
10-6	Parallel Subtractors	238
10-7	Using Adders for Subtraction	239
10-8	IC Adders	241
10-9	Binary Multiplication	243
10-10	Binary Multipliers	244
10-11	2s Complement Notation, Addition, and Subtraction	247
10-12	2s Complement Adders/Subtractor	253
10-13	Troubleshooting a Full Adder	254

Chapter 11 Memories 259

11-1	Overview of Memory	260
11-2	Random-Access Memory (RAM)	263
11-3	Static RAM ICs	264
11-4	Using a SRAM	267
11-5	Read-Only Memory (ROM)	269
11-6	Using a ROM	272
11-7	Programmable Read-Only Memory (PROM)	274
11-8	Nonvolatile Read/Write Memory	276
11-9	Memory Packaging	281
11-10	Computer Bulk Storage Devices	283

Chapter 12 Digital Systems 294

12-1	Elements of a System	294
12-2	A Digital System of an IC	295
12-3	The Calculator	296
12-4	The Computer	298
12-5	The Microcomputer	300
12-6	Microcomputer Operation	302
12-7	Microcomputer Address Decoding	305
12-8	Data Transmission	308
12-9	Detecting Error in Data Transmissions	312
12-10	Adder/Subtractor System	313
12-11	The Digital Clock	316
12-12	The LSI Digital Clock	319
12-13	A Practical LSI Digital Clock System	322
12-14	The Frequency Counter	327
12-15	An Experimental Frequency Counter	331
12-16	LCD Timer with Alarm	334
12-17	Electronic Games	337
12-18	Programmable Logic Controllers (PLCs)	344
12-19	Microcontrollers	348

Chapter 13 Connecting with Analog Devices 360

13-1	D/A Conversion	361
13-2	Operational Amplifiers	362
13-3	A Basic D/A Converter	363
13-4	Ladder-Type D/A Converters	364
13-5	An A/D Converter	366
13-6	Voltage Comparators	369
13-7	An Elementary Digital Voltmeter	370
13-8	Other A/D Converters	372
13-9	A/D Converter Specifications	376
13-10	An A/D Converter IC	377
13-11	Digital Light Meter	379
13-12	Digital Voltmeter	384
Appendix A		389
Glossary		390
Index		401