

DIGITAL FUNDAMENTALS

3RD EDITION

FLOYD



Contents

1	INTRODUCTION	1
1-1	Logic Levels and Pulse Waveforms	2
1-2	Elements of Digital Logic	5
1-3	Functions of Digital Logic	6
1-4	Digital Integrated Circuits	11
1-5	Microprocessors	14
1-6	Digital Testing and Troubleshooting Instruments	15
2	NUMBER SYSTEMS AND CODES	27
2-1	Decimal Numbers	28
2-2	9's and 10's Complements	29
2-3	Binary Numbers	32
2-4	Binary Arithmetic	36
2-5	1's and 2's Complements	39
2-6	Decimal-to-Binary Conversion	42
2-7	Octal Numbers	45
2-8	Hexadecimal Numbers	48

- 2-9 Binary Coded Decimal (BCD) 54
 2-10 Digital Codes 58

3 LOGIC GATES 75

- 3-1 The Inverter 76
 3-2 The AND Gate 78
 3-3 The OR Gate 82
 3-4 The NAND Gate 86
 3-5 The NOR Gate 90
 3-6 Gate Propagation Delay Time 94
 3-7 Power Dissipation 95
 3-8 Noise Immunity 96
 3-9 Loading Considerations 98
 3-10 Integrated Circuit Logic Families 100
 3-11 Data Sheet Interpretation 108
 3-12 Logic Gate Applications 110
 3-13 Troubleshooting Logic Gates 112

4 BOOLEAN ALGEBRA 125

- 4-1 Boolean Operations 126
 4-2 Logic Expressions 127
 4-3 Rules and Laws of Boolean Algebra 129
 4-4 DeMorgan's Theorems 135
 4-5 Boolean Expressions for Gate Networks 137
 4-6 Simplification of Boolean Expressions 140
 4-7 The Karnaugh Map 142

5 COMBINATIONAL LOGIC 157

- 5-1 Analysis of Combinational Logic Circuits 158
 5-2 Designing Combinational Logic Circuits 166
 5-3 The Universal Property of the NAND Gate 175
 5-4 The Universal Property of the NOR Gate 178

- 5-5 Pulsed Operation 181
- 5-6 Troubleshooting Gate Networks 184

6

FUNCTIONS OF COMBINATIONAL LOGIC 199

- 6-1 Adders 200
- 6-2 Parallel Binary Adders 204
- 6-3 A Method of Speeding Addition 209
- 6-4 Magnitude Comparators 214
- 6-5 Decoders 221
- 6-6 Encoders 236
- 6-7 Code Conversion 242
- 6-8 Multiplexers (Data Selectors) 247
- 6-9 Demultiplexers 258
- 6-10 Parity Generators/Checkers 260
- 6-11 Troubleshooting 268

7

FLIP-FLOPS AND OTHER MULTIVIBRATORS 285

- 7-1 Latches 286
- 7-2 Edge-Triggered Flip-Flops 293
- 7-3 Pulse-Triggered (Master-Slave) Flip-Flops 305
- 7-4 The Data Lock-Out Flip-Flops 314
- 7-5 Operating Characteristics 315
- 7-6 Basic Flip-Flop Applications 319
- 7-7 One-Shots 324
- 7-8 Astable Multivibrators 328
- 7-9 Troubleshooting 331

8

COUNTERS 349

- 8-1 Asynchronous Counters 350
- 8-2 Synchronous Counters 359
- 8-3 Up/Down Synchronous Counters 368
- 8-4 A Procedure for the Design of Sequential Circuits 372

- 8-5 Cascaded Counters 381
- 8-6 Counter Decoding 386
- 8-7 Counter Applications 390
- 8-8 Logic Symbols with Dependency Notation 396

9**SHIFT REGISTERS 411**

- 9-1 Shift Register Functions 412
- 9-2 Serial In-Serial Out Shift Registers 413
- 9-3 Serial In-Parallel Out Shift Registers 419
- 9-4 Parallel In-Serial Out Shift Registers 422
- 9-5 Parallel In-Parallel Out Shift Registers 426
- 9-6 Bidirectional Shift Registers 428
- 9-7 Shift Register Counters 431
- 9-8 Shift Register Applications 436
- 9-9 Troubleshooting 445
- 9-10 Logic Symbols with Dependency Notation 450

10**MEMORIES 463**

- 10-1 Memory Concepts 464
- 10-2 Read-Only Memories (ROMs) 470
- 10-3 Programmable ROMs (PROMs and EPROMs) 482
- 10-4 Read/Write Random Access Memories (RAMs) 486
- 10-5 Memory Expansion 497
- 10-6 Magnetic Bubble Memories (MBMs) 500
- 10-7 Magnetic Surface Storage Devices 505
- 10-8 Special Memories and Applications 510
- 10-9 Troubleshooting 514

11**INTERFACING AND DATA TRANSMISSION 529**

- 11-1 Interfacing Logic Families 530
- 11-2 Interfacing with Buses 536
- 11-3 Interfacing Digital and Analog Systems 541

- 11-4 Modems and Interfaces 562
 11-5 The Schmitt Trigger as an Interface Circuit 569

12 ARITHMETIC PROCESSES WITH AN INTRODUCTION TO MICROPROCESSORS 579

- 12-1 Binary Representation of Signed Numbers 580
 12-2 Signed Binary Arithmetic 582
 12-3 Implementation of Signed Binary Arithmetic 593
 12-4 Addition of Signed BCD Numbers 598
 12-5 Microprocessors 600

A INTEGRATED CIRCUIT TECHNOLOGIES 609

- A-1 Integrated Circuit Inverters 609
 A-2 Integrated Circuit NAND Gates 612
 A-3 Integrated Circuit NOR Gates 614
 A-4 TTL AND Gates and OR Gates 615
 A-5 Open-Collector Gates 616
 A-6 More TTL Circuits 617
 A-7 ECL Circuits 620
 A-8 I²L Circuits 622
 A-9 CMOS Circuits 624
 A-10 PMOS and NMOS 626

B DATA SHEETS 629

C ERROR DETECTION AND CORRECTION 652

- C-1 Error Detection Codes 652
 C-2 Hamming Error Correction Codes 653
 C-3 Detecting and Correcting an Error 657

D**CONVERSIONS 659**

POWERS OF TWO 661**SOLUTIONS TO SELF-TESTS A-1****ANSWERS TO ODD-NUMBERED PROBLEMS B-1****GLOSSARY C-1****INDEX D-1**