

Sanjeev Gupta
Santosh Gupta



ELECTRONIC DEVICES & CIRCUITS



DHANPAT RAI PUBLICATIONS

CONTENTS IN BRIEF

1. Energy Levels and Energy Bands	1.1-1.20
2. Conduction in Semiconductors	2.1-2.28
3. Semiconductor Device Physics	3.1-3.32
4. P-N Junction Diode and Clipping and Clamping Circuits Applications	4.1-4.60
5. Special Semiconductor Devices	5.1-5.64
6. Transistors	6.1-6.40
7. Field Effect Transistors	7.1-7.62
8. Rectifying Circuits and D.C. Power Supplies	8.1-8.62
9. Four-terminal Active network, Different parameters (Z, Y and h) and Network Theorems	9.1-9.46
10. Transistor Biasing and Thermal Stabilization	10.1-10.38
11. Small Signal Amplifiers	11.1-11.48
12. Feedback Amplifiers	12.1-12.36
13. Large Signal or Power Amplifiers	13.1-13.46
14. Sinusoidal Oscillators	14.1-14.37
15. Switching Circuits (Multivibrators)	15.1-15.34
16. Integrated Circuits	16.1-16.22
17. Operational Amplifiers, Applications and Waveform Generators	17.1-17.78
18. Active Filters	18.1-18.24
19. Differential Amplifier	19.1-19.65
20. Modulation and Demodulation	20.1-20.50
21. Communication Systems (Digital and Optical Communication)	21.1-21.82
22. Microwave Tubes	22.1-22.42
23. Basic Power Electronics	23.1-23.36
24. Number Systems and Codes	24.1-24.38
25. Boolean Algebra and Logic Gates	25.1-25.62
26. Logic Circuits	26.1-26.34
27. Digital Logic Families	27.1-27.24
28. Memory, Microcomputers and Microprocessor	28.1-28.59
29. Sensors and Transducers	29.1-29.81
30. Thermionic Emission Valves and Electronic Instruments	30.1-30.60
31. Analog to Digital and Digital to Analog Converters	31.1-31.30

CONTENTS

1. ENERGY LEVELS AND ENERGY BANDS	1.1-1.20		
1.1 Atomic structure	1.1		
1.2 Bohr's theory of hydrogen atom	1.1		
1.3 Excitation and ionization of atoms	1.3		
1.4 The photon nature of light	1.4		
1.5 Collisions of photons with atoms	1.4		
1.6 Electronic structure of the elements	1.4		
1.7 Circuit parameters	1.6		
1.8 Voltage and current sources	1.7		
1.9 Independent and dependent sources ...	1.8		
1.10 Passive electrical / electronic components	1.9		
1.11 Energy bands in solids	1.15		
1.12 Valence band, conduction band and forbidden energy gap	1.16		
1.13 Insulators, semiconductors and conductors	1.16		
Exercises	1.18		
2. CONDUCTION IN SEMICONDUCTORS	2.1-2.28		
2.1 Semiconductors	2.1		
2.2 Chemical bonds in semiconductors like germanium and silicon	2.2		
2.3 Effect of temperature on semiconductors	2.3		
2.4 Mechanism of conduction of electrons and holes	2.4		
2.5 Carrier generation and recombination	2.5		
2.6 Pure or intrinsic semiconductor and impurity or extrinsic semiconductors	2.6		
2.7 N-type extrinsic semiconductor	2.7		
2.8 P-type extrinsic semiconductor	2.8		
2.9 Majority and minority charge carriers	2.10		
2.10 Mobile charge carriers and immobile ions	2.10		
2.11 The mass-action law	2.11		
2.12 Charge densities in a semiconductor	2.11		
2.13 Drift current, current density and conductivity in good conductors	2.12		
2.14 Electrical properties of semiconductor materials	2.13		
2.15 The Hall effect	2.15		
Exercises and Problems	2.22		
3. SEMICONDUCTOR DEVICE PHYSICS	3.1-3.32		
3.1 Fermi-Dirac energy distribution	3.1		
3.2 Fermi level	3.4		
3.3 Electron emission from metal	3.5		
3.4 Carrier concentration in an intrinsic semiconductor	3.7		
3.5 Carrier concentration in terms of band gap (E_g)	3.12		
3.6 Electrical conductivity	3.14		
3.7 Fermi-level in extrinsic semiconductor	3.15		
3.8 Energy band structure of an open-circuit P-N junction	3.16		
3.9 Generation and recombination of charges	3.18		
3.10 Diffusion	3.20		
3.11 The continuity equation	3.23		
3.12 Injected minority-carrier charge	3.24		
3.13 Continuously graded semiconductor and its potential variation	3.25		
Exercises and Problems	3.29		
4. P-N JUNCTION DIODE AND CLIPPING AND CLAMPING CIRCUITS APPLICATIONS	4.1-4.60		
4.1 P-N Junction diode	4.1		
4.2 Working of diode	4.3		
4.3 Volt-ampere characteristics of P-N Junction	4.6		

(viii)

4.4 D.C. Load lines	4.7
4.5 Diode equation (V-I equation for diode)	4.8
4.6 Important terms	4.10
4.7 Potential barrier and width of depletion layer across P-N junction	4.14
4.8 Effect of temperature on P-N Junction diodes	4.17
4.9 Capacitive effects in P-N junction diode	4.18
4.10 Diode resistance	4.21
4.11 P-N diode switching times	4.22
4.12 Current components in P-N diode	4.25
4.13 Quantitative theory of P-N diode currents	4.26
4.14 P-N diode Clipping circuits	4.29
4.15 P-N diode Clamping circuits	4.32
Exercises and Problems	4.52
5. SPECIAL SEMICONDUCTOR DEVICES	5.1-5.64
5.1 Thermistors, Sensistors and Barretters	5.1
5.2 Gunn effect and diodes	5.3
5.3 Zener diode	5.7
5.4 Tunnel diode	5.15
5.5 Pin diode	5.19
5.6 Varactor diode	5.20
5.7 Schottky diode	5.23
5.8 Backward diodes	5.24
5.9 Thyristors	5.25
5.10 Silicon controlled rectifier (SCR)	5.26
5.11 SCR switching	5.30
5.12 The Triac	5.32
5.13 Applications of Triac	5.34
5.14 The Diac	5.35
5.15 Application of Diac as lamp dimmer	5.36
5.16 Silicon controlled switch (SCS)	5.36
5.17 Unijunction transistor (UJT)	5.38
5.18 Applications of UJT	5.43
5.19 Optoelectronic devices	5.45
5.20 Photoconductive sensors	5.46
5.21 Photo voltaic or Solar cell	5.52
5.22 Light Emitting Diode (LED)	5.53
5.23 Liquid Crystal Display (LCD)	5.55
Exercises and Problems	5.57

6. TRANSISTORS	6.1-6.40
6.1 The bipolar junction transistor	6.1
6.2 Operation of PNP transistor	6.5
6.3 Operation of NPN transistor	6.6
6.4 Current components in a transistor	6.6
6.5 Transistor as an Amplifier	6.7
6.6 Transistor circuit configurations	6.9
6.7 Common-Base (CB) configuration	6.10
6.8 Common-Emitter (CE) configuration	6.12
6.9 Early effect	6.14
6.10 Common-Collector (CC) configuration	6.16
6.11 Characteristics of common base circuit	6.17
6.12 Characteristics of common emitter circuit	6.20
6.13 D.C. load line	6.22
6.14 D.C. equivalent circuit	6.25
6.15 Another way of drawing transistor circuit	6.26
6.16 Beta rule	6.27
6.17 Transistor construction	6.28
6.18 Transistor current and voltage notation	6.30
Exercises and Problems	6.32
7. FIELD EFFECT TRANSISTORS ...	7.1-7.62
7.1 Introduction	7.1
7.2 Junction Field Effect Transistor (JFET)	7.2
7.3 Static characteristic curves of JFET	7.5
7.4 Transfer characteristics	7.7
7.5 FET parameters	7.8
7.6 FET on an IC chip	7.11
7.7 Biasing of FET circuits	7.11
7.8 Small signal models for FET	7.17
7.9 Common Source (CS) FET amplifier with self bias	7.19
7.10 Common Drain (CD) or source follower amplifier	7.24
7.11 Common Gate (CG) amplifier	7.27
7.12 Applications of FETs	7.29
7.13 Depletion MOSFET OR IGFET	7.37
7.14 Enhancement only MOSFET	7.41
7.15 Dual-gate MOSFET	7.48
7.16 Comparison of JFETS and MOSFETS	7.48
7.17 Comparison of P-channel and N-channel MOSFETS	7.49

CONTENTS**(ix)**

7.18 Biasing of MOSFET using constant-current source	7.49	9.10 Superposition theorem	9.25
7.19 Small-signal equivalent circuit model ...	7.50	9.11 Thevenin's theorem	9.29
7.20 The T-equivalent circuit model	7.50	9.12 Norton's theorem	9.36
Exercises and Problems	7.51	9.13 Maximum power-transfer theorem	9.37
		Exercises and Problems	9.40
8. RECTIFYING CIRCUITS AND D.C. POWER SUPPLIES	8.1-8.62	10. TRANSISTOR BIASING AND THERMAL STABILIZATION	10.1-10.38
8.1 Load line analysis of a diode circuit	8.1	10.1 Transistor biasing	10.1
8.2 Half-wave rectifier	8.3	10.2 Stabilisation	10.1
8.3 Centre-tap fullwave rectifier	8.12	10.3 Stability factor	10.2
8.4 Full-wave bridge rectifier	8.21	10.4 Different methods for transistor biasing	10.4
8.5 Filters	8.26	10.5 Base resistor method	10.4
8.6 Fullwave rectifier with series inductor filter	8.26	10.6 Collector to base bias	10.7
8.7 Shunt capacitor filter	8.30	10.7 Base bias with collector and emitter feedbacks	10.10
8.8 Choke input filter or L-C filter	8.36	10.8 Self bias or emitter bias (voltage divider bias)	10.13
8.9 The CLC or PI filter	8.39	10.9 Bias compensation	10.25
8.10 Voltage regulation	8.41	10.10 Thermal resistance and condition of thermal stability	10.28
8.11 Complete power supply	8.48	10.11 Heat sink	10.30
8.12 Switched mode power supply (SMPS)	8.49	Exercises and Problems	10.32
8.13 Voltage multipliers	8.50		
8.14 Voltage tripler and quadrupler circuits or voltage multiplier	8.52	11. SMALL SIGNAL AMPLIFIERS ...	11.1-11.48
8.15 SCR halfwave rectifier (phase control of SCR)	8.53	11.1 Practical circuit of transistor amplifier	11.1
8.16 SCR full-wave rectifier	8.55	11.2 Load line analysis	11.3
Exercises and Problems	8.56	11.3 Calculation of gain	11.6
		11.4 Phase reversal	11.7
		11.5 Ebers-moll model	11.8
		11.6 Simplified CE hybrid model	11.9
		11.7 Generalised approximate model	11.10
		11.8 Classification of amplifiers	11.11
		11.9 Common Emitter (CE) amplifier	11.11
		11.10 Analysis of a transistor amplifier using h -parameters	11.12
		11.11 Common Base (CB) amplifier	11.16
		11.12 Common Collector (CC) amplifier ...	11.18
		11.13 Comparison of CE, CB and CC amplifiers	11.20
		11.14 Effect of emitter bypass capacitor (CE) on low frequency response	11.20
		11.15 Effect of coupling capacitor C_C on low frequency response	11.23
		11.16 Multistage transistor amplifier	11.24
		11.17 R-C coupled transistor amplifier	11.25
9. FOUR-TERMINAL ACTIVE NETWORK, DIFFERENT PARAMETERS (Z, Y and h) AND NETWORK THEOREMS	9.1-9.46		
9.1 Transistor as a four pole	9.1		
9.2 Impedance parameters or Z-parameters	9.1		
9.3 Admittance parameters or Y-parameters	9.3		
9.4 Hybrid parameters or h -parameters	9.4		
9.5 Performance of a linear circuit in h -parameters	9.8		
9.6 Voltage gain, current gain and output impedance taking into account the source resistance (R_S)	9.10		
9.7 Conversion of hybrid parameters	9.13		
9.8 Determination of h -parameters from static characteristics	9.14		
9.9 Experimental determination of hybrid parameters	9.16		

(x)		
11.18	Lower cut-off frequency (f_1)	11.30
11.19	Upper cut-off frequency f_2	11.32
11.20	Frequency response curve and band-width	11.33
11.21	Transformer coupled amplifier	11.35
11.22	Cascode or CE-CB configuration	11.37
11.23	Hybrid parameters of cascode amplifier	11.38
11.24	Analysis of cascode amplifier using h -parameters	11.40
11.25	Analysis of cascode amplifier using hybrid- π model	11.41
	Exercises and Problems	11.44
12.	FEEDBACK AMPLIFIERS	12.1-12.36
12.1	General theory of feedback	12.1
12.2	Negative feedback circuit	12.4
12.3	Sampling and mixing networks	12.5
12.4	Gain of different types of amplifiers ...	12.5
12.5	Different topologies	12.6
12.6	Gains in different topologies	12.7
12.7	Disadvantages of negative feedback	12.10
12.8	Advantages of negative feedback ...	12.10
12.9	Analysis of different feedback circuits (feedback topologies)	12.18
12.10	Negative current feedback circuit	12.24
12.11	Emitter follower	12.26
12.12	Darlington emitter follower	12.29
12.13	Boot strapping	12.30
	Exercises and Problems	12.31
13.	LARGE SIGNAL OR POWER AMPLIFIERS	13.1-13.46
13.1	Introduction	13.1
13.2	Difference between voltage amplifier and power amplifier	13.2
13.3	Terms used in power amplifiers	13.3
13.4	Class A power amplifier	13.4
13.5	Transformer coupled class A amplifier	13.10
13.6	Harmonic distortion in amplifiers	13.15
13.7	Class A push-pull power amplifier ...	13.16
13.8	Class B power amplifier	13.18
13.9	Class B push-pull amplifier	13.20
13.10	Class C amplifier	13.23
13.11	High frequency π model for common emitter transistor	13.24
13.12	Transistor cutoff frequencies	13.25
13.13	Common emitter short circuit current gain (β cut-off frequency)	13.26
13.14	High frequency CE current gain with resistive load	13.29
13.15	FET common source (CS) amplifier at high frequencies	13.31
13.16	Need for tuned amplifier	13.33
13.17	Few fundamentals about tuned circuits	13.33
13.18	Single tuned amplifier	13.37
13.19	Effect of cascading single tuned amplifiers on bandwidth	13.39
13.20	Double tuned amplifier	13.40
	Exercises and Problems	13.41
14.	SINUSOIDAL OSCILLATORS ...	14.1-14.37
14.1	Introduction	14.1
14.2	Types of oscillators	14.2
14.3	The oscillatory circuit	14.3
14.4	Essentials of transistor oscillator	14.4
14.5	Tuned collector oscillator	14.5
14.6	Tuned-base oscillator	14.8
14.7	Hartley oscillator	14.9
14.8	Hartley oscillator using JFET	14.13
14.9	Colpitt's oscillator	14.15
14.10	Colpitt's oscillator using FET	14.17
14.11	Clapp's oscillator	14.17
14.12	Phase shift oscillator	14.18
14.13	Wien-bridge oscillator	14.21
14.14	Frequency stability of oscillator	14.23
14.15	Crystal oscillators	14.23
14.16	Frequency stability of oscillator	14.26
	Exercises and Problems	14.32
15.	SWITCHING CIRCUITS (MULTIVIBRATORS)	15.1-15.34
15.1	Switching action of a transistor	15.2
15.2	Switching times in a transistor	15.5
15.3	Multivibrators	15.6
15.4	Astable multivibrator	15.7
15.5	Monostable multivibrator	15.12
15.6	Bistable multivibrator	15.19
15.7	Triggering of bistable multivibrator	15.23
15.8	Self biased binary	15.26

CONTENTS

(xi)

15.9 Schmitt trigger (Emitter Coupled Binary)	15.27	17.16 Large-signal operation of Op-Amps ...	17.35
15.10 Blocking oscillator	15.29	17.17 Adder or Summing amplifier	17.42
Exercises and Problems	15.31	17.18 Subtractor	17.48
16. INTEGRATED CIRCUITS	16.1-16.22	17.19 Integrator	17.49
16.1 Integrated circuit	16.1	17.20 Differentiator	17.52
16.2 Advantages and limitations	16.1	17.21 Low pass filter	17.52
16.3 IC classifications	16.2	17.22 Voltage to current converter	17.53
16.4 Production process of monolithic IC ...	16.3	17.23 Current to voltage converter	17.54
16.5 Fabrication of components on monolithic IC	16.4	17.24 Comparator	17.54
16.6 IC packings	16.8	17.25 Hartley oscillator	17.55
16.7 General integrated circuit technology	16.9	17.26 Colpitt's oscillator	17.56
16.8 Photolithographic process	16.9	17.27 R-C phase shift oscillator using Op-Amp	17.57
16.9 Monolithic IC with more components	16.10	17.28 Wien bridge oscillator using Op-Amp.	17.58
16.10 Unipolar ICs (MOS ICs)	16.12	17.29 Square wave generator	17.60
16.11 IC symbols	16.12	17.30 Pulse generator	17.62
16.12 IC voltage regulators	16.13	17.31 Triangular wave generator	17.64
16.13 Three terminal voltage regulators	16.13	17.32 Saw-tooth wave generator	17.65
16.14 Adjustable voltage regulators	16.16	17.33 IC-555 timer	17.66
16.15 IC 723 monolithic negative voltage regulator	16.19	17.34 IC-555 timer as astable multivibrator	17.67
Exercises	16.21	17.35 IC-555 timer as monostable multivibrator	17.69
17. OPERATIONAL AMPLIFIERS, APPLICATIONS AND WAVEFORM GENERATORS	17.1-17.78	Exercises and Problems	17.71
17.1 Circuit symbol of an Op-Amp	17.1	18. ACTIVE FILTERS	18.1-18.24
17.2 Equivalent circuit of Op-Amp	17.3	18.1 Introduction	18.1
17.3 Packaging and pin outs	17.3	18.2 Classification of filters	18.1
17.4 Characteristics of an ideal Op-Amp ...	17.4	18.3 Active versus passive filters	18.2
17.5 Operational amplifier stages	17.5	18.4 Definitions related to filters	18.3
17.6 Transfer characteristic of Op-Amp ...	17.6	18.5 Frequency response characteristics of filters	18.5
17.7 Open-loop and closed-loop gains ...	17.6	18.6 First order Butterworth low pass filter	18.6
17.8 Open-loop Op-Amp configurations ...	17.7	18.7 Second order low-pass Butterworth filter	18.9
17.9 Limitations of open-loop Op-Amp configuration	17.9	18.8 First order high-pass Butterworth filter	18.11
17.10 Inverting Op-Amp (Negative Scaler) [Closed Loop]	17.10	18.9 Second order high-pass Butterworth filter	18.12
17.11 Non-inverting amplifier (positive scaler)	17.13	18.10 Higher-order filters	18.13
17.12 Operational amplifier parameters	17.24	18.11 Band-pass filters	18.14
17.13 Difference amplifier	17.26	18.12 Band-stop or band-reject or band-elimination filter	18.17
17.14 The instrumentation amplifier	17.29	18.13 All-pass filter	18.20
17.15 Effect of finite open-loop gain and bandwidth on circuit performance	17.32	Exercises and Problems	18.21

(xii)

19. DIFFERENTIAL AMPLIFIER	19.1-19.65	21. COMMUNICATION SYSTEMS (DIGITAL AND OPTICAL COMMUNICATION)	21.1-21.82
19.1 The MOS differential pair	19.3	21.1 Analog and digital signals	21.1
19.2 Small-signal operation of the MOS differential pair	19.8	21.2 Pulse modulation	21.2
19.3 The BJT differential pair	19.14	21.3 Pulse Amplitude Modulation (PAM) ...	21.3
19.4 Large-signal operation (D.C. transfer characteristics)	19.17	21.4 Pulse Time Modulation (PTM)	21.6
19.5 Small-signal operation	19.18	21.5 Pulse Code Modulation (PCM)	21.11
19.6 Other non-ideal characteristics of the differential amplifier	19.27	21.6 Delta Modulation (DM)	21.15
19.7 The MOS differential amplifier with active load	19.35	21.7 Modem	21.17
19.8 The bipolar differential pair with active load	19.43	21.8 Fax (facsimile)	21.17
Exercise and Problems	19.56	21.9 Propagation of electromagnetic waves in atmosphere	21.18
20. MODULATION AND DEMODULATION	20.1-20.50	21.10 Satellite communication	21.20
20.1 Modulation	20.2	21.11 Remote sensing	21.21
20.2 Need for Modulation	20.3	21.12 Transmission medium or communication channel	21.22
20.3 Modulation index	20.4	21.13 Line communication	21.22
20.4 Amplitude Modulation (AM)	20.6	21.14 Telephone links	21.23
20.5 Analysis and frequency spectrum of AM wave	20.7	21.15 Optical communication	21.24
20.6 Power relations in the AM wave	20.9	21.16 Fibre optics	21.24
20.7 Methods of generation of AM	20.14	21.17 Principle of optical fibre	21.25
20.8 Carrier suppressor and SSB systems	20.20	21.18 Structure of optical fibres	21.25
20.9 DBSC generation by balanced modulator	20.22	21.19 Types of optical fibres	21.26
20.10 Single Sideband generation (SSB)	20.24	21.20 Acceptance angle and numerical aperture	21.28
20.11 Comparison of AM systems	20.26	21.21 V number	21.32
20.12 Frequency modulation	20.26	21.22 Collection of light from the diffuse source by fibre	21.33
20.13 Generation of FM	20.32	21.23 Attenuation or transmission loss	21.34
20.14 Comparison of FM and AM	20.35	21.24 Attenuation losses in fibre	21.35
20.15 Phase modulation	20.36	21.25 Dispersion and dispersion losses ...	21.36
20.16 Demodulation of AM	20.37	21.26 Fibre optics communication system ...	21.37
20.17 Linear envelope type diode detector	20.39	21.27 Advantages of communication with optical fibre	21.39
20.18 FM detection/demodulation	20.40	21.28 Detectors	21.39
20.19 Elementary principles of radio transmission and reception	20.43	21.29 Connectors	21.41
20.20 Superheterodyne radio receiver	20.44	21.30 Multiplexers	21.42
Exercises and Problems	20.45	21.31 Couplers	21.43
		21.32 Fabrication of optical fibres	21.44
		21.33 Applications and uses	21.45
		21.34 Introduction to transmission lines ...	21.46
		21.35 Types of transmission lines	21.47
		21.36 Transmission line parameters	21.48

CONTENTS

(xiii)

21.37	Transmission line equations	21.48	23.5	Silicon Controlled Rectifier (SCR)	23.3
21.38	Solution of transmission line equations	21.51	23.6	Mechanism of operation of SCR	23.5
21.39	Characteristic impedance	21.52	23.7	Characteristics of SCR	23.11
21.40	Propagation constant and phase velocity	21.54	23.8	Ratings and specifications of SCR	23.13
21.41	Introduction to waveguides	21.56	23.9	Series-parallel connection of SCRs	23.17
21.42	Waves between parallel planes	21.56	23.10	Protection circuits	23.21
21.43	Transverse Electric waves (TE) between planes ($E_z = 0$)	21.59	23.11	Phase control	23.25
21.44	Cut-off frequency, phase velocity and group velocity between parallel plane (TE mode)	21.61	23.12	Applications of SCR	23.27
21.45	Transverse Electromagnetic (TM) waves between parallel planes ($H_z = 0$)	21.64		Exercises and Problems	23.30
21.46	Cut-off frequency and phase velocity	21.65	24. NUMBER SYSTEMS AND CODES 24.1-24.38		
21.47	Transverse Electromagnetic waves (TEM waves)	21.66	24.1	Introduction	24.1
21.48	Rectangular waveguide	21.67	24.2	The decimal number system	24.4
21.49	Transverse magnetic waves in rectangular guide	21.68	24.3	Binary number system	24.6
21.50	Cut-off wavelength and guide wavelength in TM wave (Rectangular Waveguide)	21.71	24.4	The octal number system	24.7
21.51	Transverse Electric (TE) waves in rectangular waveguide	21.73	24.5	Hexadecimal number system	24.8
21.52	Cut-off wavelength and guide wavelength in 'TE' mode of rectangular waveguide	21.75	24.6	Decimal to binary conversion	24.9
	Exercises and Problems	21.76	24.7	Binary to decimal conversion	24.10
22. MICROWAVE TUBES 22.1-22.42			24.8	Conversion of octal number into decimal number	24.11
22.1	Two cavity klystron	22.1	24.9	Conversion of decimal number into octal number	24.12
22.2	Reflex klystron	22.13	24.10	Conversion of octal number into binary number	24.12
22.3	Magnetron oscillator	22.21	24.11	Conversion of binary number into octal number	24.13
22.4	Travelling-wave tube (TWT)	22.30	24.12	Conversion of hexadecimal number into decimal number	24.13
22.5	Backward wave oscillator	22.37	24.13	Conversion of decimal number into hexadecimal number	24.14
	Exercises	22.38	24.14	Conversion of binary number into hexadecimal number	24.14
	Problems	22.39	24.15	Conversion of hexadecimal into binary number	24.15
23. BASIC POWER ELECTRONICS 23.1-23.36			24.16	Binary addition	24.15
23.1	Comparison of thyatron with thyristors	23.1	24.17	Binary subtraction	24.17
23.2	Comparison of transistors and thyristors	23.1	24.18	Binary multiplication and division	24.17
23.3	Applications of thyristors	23.2	24.19	Complements of a number	24.18
23.4	Thyristor family	23.3	24.20	1's complemental subtraction	24.19
			24.21	2's complemental subtraction	24.20
			24.22	9's and 10's complements in decimal number system	24.21
			24.23	Other number systems	24.23
			24.24	Floating point representation	24.25
			24.25	Binary codes	24.26
			24.26	Binary Coded Decimal (BCD) code	24.27

(xiv)

24.27 Excess-3 code (non-weighted code)	24.31
24.28 Gray code	24.32
24.29 Cyclic codes	24.33
Exercises and Problems	24.35
25. BOOLEAN ALGEBRA AND LOGIC GATES	25.1-25.62
25.1 Boolean algebra	25.1
25.2 Laws of boolean algebra	25.2
25.3 Basic logic gates	25.9
25.4 OR gate (OR addition)	25.9
25.5 AND gate (AND multiplication)	25.12
25.6 The NOT gate	25.15
25.7 De-Morgan's theorem	25.21
25.8 NAND gate	25.25
25.9 NAND gate is a universal gate	25.27
25.10 NOR gate	25.28
25.11 NOR gate is a universal gate	25.30
25.12 Exclusive-OR gate (Ex-OR gate)	25.31
25.13 Exclusive-NOR gate (Ex-NOR gate)	25.33
25.14 Logic gates at a glance	25.35
25.15 Meaning of minimization	25.39
25.16 Meaning of minterms (standard product) and maxterms (standard sums)	25.39
25.17 Canonical forms (SOP and POS)	25.40
25.18 Karnaugh map <i>4 variables</i>	25.43
25.19 Reduction of boolean expression	25.45
25.20 Map rolling	25.48
25.21 Overlapping and redundant groups ...	25.48
25.22 Don't care condition	25.49
Exercises and Problems	25.56
26. LOGIC CIRCUITS	26.1-26.34
26.1 Introduction to logic circuits	26.1
26.2 Arithmetic circuits	26.2
26.3 Half-adder	26.2
26.4 Full-adder	26.4
26.5 Half subtractor	26.5
26.6 Full subtractor	26.7
26.7 Sequential logic circuits	26.8
26.8 Flip-flop <i>J.K.D.T</i>	26.9
26.9 Multiplexer (Data selector)	26.16
26.10 Demultiplexer	26.21
26.11 Counters	26.23

26.12 Ripple counters [Asynchronous counters]	26.25
26.13 Synchronous counter	26.26
26.14 3-BIT synchronous counter	26.27
26.15 MOD-8 binary ripple counter	26.29
26.16 Registers	26.30
26.17 Buffer registers	26.31
Exercises	26.32
27. DIGITAL LOGIC FAMILIES	27.1-27.24
27.1 Main logic families	27.1
27.2 Characteristics of logic families	27.2
27.3 Resistor-Transistor Logic (RTL)	27.3
27.4 Diode-Transistor Logic (DTL)	27.4
27.5 Transistor-Transistor Logic (TTL)	27.6
27.6 TTL NOR gate	27.7
27.7 TTL inverter	27.9
27.8 TTL sub-families	27.9
27.9 Emitter-Coupled Logic (ECL)	27.11
27.10 Integrated Injection Logic (IIL or I ² L)	27.12
27.11 Metal Oxide Semiconductor (MOS) circuits	27.13
27.12 PMOS circuit	27.13
27.13 NMOS circuits	27.16
27.14 Complementary MOS logic (CMOS)	27.18
27.15 Comparison of logic families	27.22
Exercises	27.22
28. MEMORY, MICROCOMPUTERS AND MICROPROCESSOR	28.1-28.59
28.1 Classification of memories	28.2
28.2 Internal construction of a memory cell	28.3
28.3 Block diagram of a memory unit	28.4
28.4 Random Access Memory (RAM)	28.6
28.5 Memory addressing	28.7
28.6 Memory decoding	28.8
28.7 Coincident decoding	28.9
28.8 Address multiplexing	28.10
28.9 Memory expansion	28.11
28.10 Read-Only Memory (ROM)	28.13
28.11 Combinational circuit implementation	28.17
28.12 Combinational programmable logic devices (PLDs)	28.20
28.13 Programmable Logic Array (PLA)	28.21

CONTENTS

(xv)

28.14 Programmable Array Logic (PAL)	28.24	29.27 Selection of transducer	29.74
28.15 Comparison between PROM, PLA and PAL	28.27	Exercises	29.75
28.16 Introduction to computers	28.27	Numerical Problems	29.77
28.17 Basic computer organisation	28.28	30. THERMIONIC EMISSION VALVES AND ELECTRONIC INSTRUMENTS	30.1-30.60
28.18 Classification of computers	28.29	30.1 Thermionic emission and work function	30.1
28.19 Overview of microcomputer	28.31	30.2 Richardson's equation	30.2
28.20 Introduction to microprocessors	28.32	30.3 Thermionic diode	30.3
28.21 8085 microprocessor	28.34	30.4 Rectification of alternating current by diode	30.5
28.22 Instruction set	28.39	30.5 The triode	30.6
28.23 Addressing modes	28.46	30.6 Triode as an amplifier	30.8
28.24 Microcontroller	28.51	30.7 Tetrode valve	30.11
28.25 Programmable Logic Controller (PLC)	28.53	30.8 Pentode valve	30.14
Exercises	28.54	30.9 Cathode ray oscilloscope	30.15
Problems	28.56	30.10 Basic oscilloscope patterns	30.24
29. SENSORS AND TRANSDUCERS	29.1-29.81	30.11 Measurements with C.R.O	30.28
29.1 Introduction	29.1	30.12 Dual trace CRO (General)	30.31
29.2 Requirements of transducer	29.2	30.13 Dual beam CRO	30.34
29.3 Transducer classification	29.3	30.14 Vacuum Tube Voltmeter (VTVM)	30.35
29.4 Resistive transducer	29.6	30.15 Block diagram of a simple digital voltmeter	30.36
29.5 Potentiometer	29.6	30.16 Ramp type digital voltmeter	30.37
29.6 Strain gauges	29.10	30.17 Dual slope integrating type digital voltmeter	30.39
29.7 Resistance Temperature Detectors (RTD) and thermistors	29.19	30.18 Potentiometer type digital voltmeter	30.40
29.8 Inductive transducer	29.26	30.19 Successive approximation type digital voltmeter	30.41
29.9 Linear Variable Differential Transformer (LVDT)	29.29	30.20 Multimeter	30.43
29.10 Capacitive transducer	29.33	30.21 Digital Multimeter (DMM)	30.47
29.11 Thermocouples	29.39	30.22 LCR meter	30.48
29.12 Piezoelectric transducer	29.43	30.23 LCR-Q meter and its applications	30.49
29.13 Photo electric transducer	29.47	Exercises and Problems	30.55
29.14 Photo multiplier tube	29.48	31. ANALOG TO DIGITAL AND DIGITAL TO ANALOG CONVERTERS	31.1-31.30
29.15 Light Dependent Resistor (LDR) or photoconductive cell	29.49	31.1 Analog-to-digital (A/D) converter or ADC	31.2
29.16 Photovoltaic or solar cells	29.51	31.2 Sample and hold circuit	31.4
29.17 Photodiode	29.53	31.3 A/D conversion techniques	31.6
29.18 Phototransistor	29.55	31.4 Performance characteristics of ADC	31.17
29.19 Optical pyrometers	29.57	31.5 Digital to Analog Converter (DAC) ...	31.20
29.20 Pyroelectric sensors — motion sensor	29.58	31.6 D/A conversion techniques	31.22
29.21 Optical encoders	29.59	31.7 Performance characteristics of DAC	31.26
29.22 Hall effect transducer	29.61	Exercises	31.28
29.23 Proximity sensors	29.62	Problems	31.29
29.24 Tactile sensors	29.65		
29.25 Micro sensors	29.66		
29.26 Characterization of transducers	29.68		