

Roll No.

(05/24)

11833

M.Sc. EXAMINATION

(For Batch 2017 to 2020 Only)

(Second Semester)

PHYSICS

PHY-203

Electronics-II

Time : Three Hours

Maximum Marks : 70

Note : Attempt *Five* questions in all, selecting *one* question from each Unit. Q. No. 1 is compulsory.

1. (a) Explain gain bandwidth product in brief. 2
- (b) Give the characteristics of an ideal op-amp. 2

(3-28/5) B-11833

P.T.O.

- (c) Find out the closed loop gain of an amplifier in which negative feedback has been applied with $A = 4000$ and $\beta = 0.2$. 2
- (d) Give the advantages of active filter over the passive filter. 2
- (e) Comment on arithmetic operation of 8085 microprocessor. 2

Unit I

2. (a) What do you mean by noise figure ? Prove that overall noise figure of a multistage amplifier is primarily dependent on the noise figure of the first stage ? 8
- (b) State and explain the frequency response of the RC coupled amplifier. 7

3. (a) Prove that there is a wider response band for CB connections as compared to the same transistor in the CE connections. 9
- (b) Define and bandwidth describe the bandwidth of cascaded amplifiers. 6

Unit II

4. (a) Draw the circuit diagram for summing, scaling and averaging amplifier using op-amp. Explain their working also. 7
- (b) Discuss the AC analysis of a differential amplifier. 8
5. (a) Describe op-amp as integrator along with input and output waveforms and its frequency response also. 10
- (b) Discuss the disadvantages of open loop op-amp. 5

Unit III

6. (a) Explain construction and working of a square wave generator with the help of an op-amp. 9
- (b) Discuss first-order low-pass Butterworth filter and explain its design also. 6
7. (a) Explain the construction and operation of Phase shift oscillator. 8
- (b) Define analog to digital converters and explain counting A/D converter along with tracking converter also. 7

Unit IV

8. (a) Explain the data addressing mode and programme memory addressing mode in a microcomputer. 7

B-11833

4

- (b) Discuss rotate and compare instructions in detail. 8

9. (a) Explain the working of 8085 microprocessor with the help of architecture. 9
- (b) Explain the term stack and subroutines in detail. 6

B-11833

5

110