

Also available as  Book



4e



# *Millman's* ELECTRONIC DEVICES AND CIRCUITS

Jacob Millman  
Christos C Halkias  
Satyabrata Jit

Outcomes Based Learning

Follows Bloom's Taxonomy

Interactive Quizzes through QR code integration



For sale in India and the other international territories, except North America

Mc  
Graw  
Hill  
Education

# Contents

<i>Preface to the Fourth Edition</i>	xiii	<i>Open-Book Exam Questions</i>	1.43
<i>Preface to the First Edition</i>	xix	<i>Multiple-Choice Questions</i>	1.43
<b>1. Electron Ballistics and Applications</b>	<b>1.1–1.44</b>	<b>2. Energy Levels and Energy Bands 2.1–2.22</b>	
<i>Learning Objectives</i>	1.1	<i>Learning Objectives</i>	2.1
1.1 Charged Particles	1.1	2.1 The Nature of the Atom	2.1
1.2 The Force on Charged Particles in an Electric Field	1.2	2.2 Atomic Energy Levels	2.4
1.3 Constant Electric Field	1.3	2.3 The Photon Nature of Light	2.5
1.4 Potential	1.5	2.4 Ionization	2.6
1.5 The eV Unit of Energy	1.6	2.5 Collisions of Electrons with Atoms	2.6
1.6 Relationship between Field Intensity and Potential	1.7	2.6 Collisions of Photons with Atoms	2.7
1.7 Two-dimensional Motion	1.7	2.7 Metastable States	2.8
1.8 Electrostatic Deflection in a Cathode-Ray Tube	1.11	<i>Problems Linked to LO 1</i>	2.9
1.9 The Cathode-Ray Oscilloscope	1.14	<i>Checkpoints</i>	2.10
1.10 Relativistic Variation of Mass with Velocity	1.15	2.8 Wave Properties of Matter	2.11
<i>Problems Linked to LO 1</i>	1.17	2.9 Electronic Structure of the Elements	2.14
<i>Checkpoints</i>	1.19	<i>Problems Linked to LO 2</i>	2.16
1.11 Force in a Magnetic Field	1.19	<i>Checkpoints</i>	2.17
1.12 Current Density	1.20	2.10 The Energy-band Theory of Crystals	2.17
1.13 Motion in a Magnetic Field	1.21	2.11 Insulators, Semiconductors, and Metals	2.19
1.14 Magnetic Deflection in a Cathode-Ray Tube	1.23	<i>Checkpoints</i>	2.20
1.15 Magnetic Focusing	1.25	<i>References</i>	2.20
<i>Problems Linked to LO 2</i>	1.27	<i>Open-Book Exam Questions</i>	2.21
<i>Checkpoints</i>	1.29	<i>Multiple-Choice Questions</i>	2.21
1.16 Parallel Electric and Magnetic Fields	1.30	<b>3. Conduction in Metals 3.1–3.28</b>	
<i>Problems Linked to LO 3</i>	1.31	<i>Learning Objectives</i>	3.1
1.17 Perpendicular Electric and Magnetic Fields	1.32	3.1 Mobility and Conductivity	3.1
<i>Problems Linked to LO 4</i>	1.36	3.2 The Energy Method of Analyzing the Motion of a Particle	3.4
<i>Checkpoints</i>	1.39	3.3 The Potential-energy Field in a Metal	3.6
1.18 The Cyclotron	1.39	<i>Problems Linked to LO 1</i>	3.8
<i>Problems Linked to LO 5</i>	1.41	<i>Checkpoints</i>	3.9
<i>Checkpoints</i>	1.42	3.4 Bound and Free Electrons	3.9
<i>References</i>	1.42	<i>Problems Linked to LO 2</i>	3.10
		<i>Checkpoints</i>	3.11
		3.5 Energy Distribution of Electrons	3.11
		3.6 The Density of States	3.14
		3.7 Work Function	3.17
		<i>Problems Linked to LO 3</i>	3.18

3.8	<i>Checkpoints</i>	3.18	5.5	Quantitative Theory of the <i>p-n</i> Diode Currents
3.9	Thermionic Emission	3.19	5.6	The Volt-Ampere Characteristic
3.10	Contact Potential	3.20	5.7	The Temperature Dependence of <i>p-n</i> Characteristics
3.11	Energies of Emitted Electrons	3.21	5.7	<i>Problems Linked to LO 2</i>
3.12	Accelerating Fields	3.22	5.8	<i>Checkpoints</i>
3.13	High-field Emission	3.23	5.9	Diode Resistance
	Secondary Emission	3.24	5.9	Space-Charge, or Transition, Capacitance $C_T$
	<i>Problems Linked to LO 4</i>	3.24	5.10	Diffusion Capacitance
	<i>Checkpoints</i>	3.25	5.11	<i>p-n</i> Diode Switching Times
	<i>References</i>	3.26		<i>Problems Linked to LO 3</i>
	<i>Open-Book Exam Questions</i>	3.26		<i>Checkpoints</i>
	<i>Multiple-Choice Questions</i>	3.26		Breakdown Diodes
<b>4. Conduction in Semiconductors</b>		<b>4.1–4.32</b>		
	<i>Learning Objectives</i>	4.1	5.12	The Tunnel Diode
4.1	Electrons and Holes in an Intrinsic Semiconductor	4.1	5.13	Characteristics of a Tunnel Diode
4.2	Conductivity of a Semiconductor	4.3	5.14	<i>Problems Linked to LO 4</i>
	<i>Problem Linked to LO 1</i>	4.5		<i>Checkpoints</i>
	<i>Checkpoints</i>	4.5	5.15	The <i>p-i-n</i> Diode
4.3	Carrier Concentrations in an Intrinsic Semiconductor	4.5	5.16	Characteristics of a <i>p-i-n</i> Diode
	<i>Problems Linked to LO 2</i>	4.14	5.17	The Point Contact Diode
	<i>Checkpoints</i>	4.14	5.18	The Schottky Barrier Diode
4.4	Donor and Acceptor Impurities	4.14	5.19	The Schottky Effect
4.5	Charge Densities in a Semiconductor with Impurities	4.16	5.20	Current-Voltage Relation of a Schottky Barrier Diode
4.6	Fermi Level in a Semiconductor having Impurities	4.19		<i>Problems Linked to LO 5</i>
	<i>Problems Linked to LO 3</i>	4.21		<i>Checkpoints</i>
	<i>Checkpoints</i>	4.22		<i>References</i>
4.7	Diffusion	4.22		<i>Open-Book Exam Questions</i>
4.8	Carrier Lifetime	4.23		<i>Multiple-Choice Questions</i>
	<i>Checkpoints</i>	4.24		
4.9	The Continuity Equation	4.24	<b>6. Applications of Diodes</b>	<b>6.1–6.78</b>
4.10	The Hall Effect	4.27	<i>Learning Objectives</i>	6.1
	<i>Checkpoints</i>	4.30	6.1	A Half-Wave Rectifier
	<i>References</i>	4.30	6.2	Ripple Factor
	<i>Open-Book Exam Questions</i>	4.31	6.3	A Full-Wave Rectifier
	<i>Multiple-Choice Questions</i>	4.31	6.4	A Bridge Rectifier
<b>5. Semiconductor-Diode Characteristics</b>		<b>5.1–5.79</b>	6.5	The Rectifier Voltmeter
	<i>Learning Objectives</i>	5.1	6.6	<i>Checkpoints</i>
5.1	Qualitative Theory of the <i>p-n</i> Junction	5.1		The Harmonic Components in Rectifier Circuits
5.2	The <i>p-n</i> Junction as a Diode	5.3	6.7	Inductor Filters
5.3	Band Structure of an Open-Circuited <i>p-n</i> Junction	5.5	6.8	Capacitor Filters
	<i>Problem Linked to LO 1</i>	5.9	6.9	Approximate Analysis of Capacitor Filters
	<i>Checkpoints</i>	5.9	6.10	L-Section Filter
5.4	The Current Components in a <i>p-n</i> Diode	5.9	6.11	Multiple L-Section Filter
			6.12	II-Section Filter
			6.13	II-Section Filter with a Resistor Replacing the Inductor
			6.14	Summary of Filters

<i>Problems Linked to LO 2</i>	6.38	7.18	Transistor as a Switch	7.47
<i>Checkpoints</i>	6.40	7.19	Transistor Switching Times	7.52
6.15 Voltage Regulation Using Zener Diode	6.40	7.20	Maximum Voltage Rating	7.54
<i>Problems Linked to LO 3</i>	6.50		<i>Problem Linked to LO 4</i>	7.56
<i>Checkpoints</i>	6.51		<i>Checkpoints</i>	7.56
6.16 Clipping Circuits	6.51		<i>References</i>	7.56
6.17 Clamper Circuits	6.63		<i>Open-Book Exam Questions</i>	7.57
6.18 The Envelope Detector Circuit	6.66		<i>Multiple-Choice Questions</i>	7.57
6.19 The Peak-To-Peak Detector Circuit	6.67			
6.20 Voltage Multipliers	6.68			
6.21 Variable Tuning Circuit Using a Varactor Diode	6.71			
<i>Problems Linked to LO 4</i>	6.73			
<i>Checkpoints</i>	6.75			
<i>References</i>	6.75			
<i>Open-Book Exam Questions</i>	6.76			
<i>Multiple-Choice Questions</i>	6.76			
<b>7. Transistor Characteristics</b>	<b>7.1–7.58</b>			
<i>Learning Objectives</i>	7.1			
7.1 The Junction Transistor	7.1			
7.2 Transistor Current Components	7.3	8.1	The Operating Point	8.1
7.3 The Transistor as an Amplifier	7.5	8.2	<i>Checkpoints</i>	8.4
7.4 Transistor Construction	7.6	8.3	Bias Stability	8.5
7.5 Detailed Study of the Currents in a Transistor	7.7	8.4	Collector-to-Base Bias or Collector-Feedback-Bias	8.7
7.6 The Transistor Alpha	7.9	8.5	Emitter-Feedback-Bias	8.9
<i>Problems Linked to LO 1</i>	7.10	8.6	Collector-Emitter Feedback-Bias	8.13
<i>Checkpoints</i>	7.11	8.7	Self-Bias, Emitter Bias, or Voltage-Divide Bias	8.15
7.7 The Common-Base Configuration	7.11	8.8	Stabilization Against Variations in $V_{BE}$ and $\beta$ for the Self-Bias Circuit	8.19
7.8 The Common-Emitter Configuration	7.14	8.9	General Remarks on Collector-Current Stability	8.22
7.9 The CE Cut-off Region	7.16	8.10	<i>Problem Linked to LO 2</i>	8.25
7.10 The CE Saturation Region	7.18	8.11	<i>Checkpoints</i>	8.27
7.11 Large-Signal, dc, and Small-Signal CE Values of Current Gain	7.20	8.12	Bias Compensation	8.27
7.12 The Common-Collector Configuration	7.21	8.13	Biasing Circuits for Linear Integrated Circuits	8.28
<i>Problems Linked to LO 2</i>	7.22	8.14	<i>Problem Linked to LO 3</i>	8.30
<i>Checkpoints</i>	7.22		<i>Checkpoints</i>	8.30
7.13 Graphical Analysis of the CE Configuration	7.23		Thermistor and Sensistor Compensation	8.31
7.14 Analytical Expressions for Transistor Characteristics	7.25		Thermal Runaway	8.31
7.15 Analysis of Cut-off and Saturation Regions	7.29		Thermal Stability	8.33
7.16 Typical Transistor-Junction Voltage Values	7.33		Some General Design Guidelines for Self-Bias Circuits	8.35
7.17 Determination of the Cut-off, Saturation, and Active Regions of a Generalized Transistor Circuit	7.34		<i>Problem Linked to LO 4</i>	8.42
<i>Problems Linked to LO 3</i>	7.43		<i>Checkpoints</i>	8.43
<i>Checkpoints</i>	7.46		<i>References</i>	8.43
			<i>Open-Book Exam Questions</i>	8.43
			<i>Multiple-Choice Questions</i>	8.44
			<b>9. Small-Signal Low-Frequency ac Models of Transistors</b>	<b>9.1–9.54</b>
			<i>Learning Objectives</i>	9.1
			9.1 The ac Analysis of a Small-Signal Low-Frequency Common-Emitter Transistor Amplifier	9.1
			<i>Checkpoints</i>	9.10
			9.2 The ac Model of Transistors Based on $r'$ -Parameter	9.11

9.3 Analysis of a Generalized Amplifier Circuit using $\pi$ -Model <i>Problems Linked to LO 2</i> <i>Checkpoints</i>	9.12 9.25 9.25	10.11 The Cascode Transistor Configuration 10.12 Difference Amplifiers <i>Problems Linked to LO 4</i> <i>Checkpoints</i> <i>References</i> <i>Open-Book Exam Questions</i> <i>Multiple-Choice Questions</i>	10.37 10.38 10.43 10.43 10.44 10.44 10.44
9.4 Drawbacks, Limitations, and Modifications of $r'_e$ -Parameter Based ac Models 9.5 Two-Port Devices and the Hybrid Model 9.6 Transistor Hybrid Model 9.7 Determination of the $h$ -Parameters from the Characteristics 9.8 Measurement of $h$ -Parameters 9.9 Conversion Formulas for the Parameters of the Three-Transistor Configurations 9.10 Analysis of a Transistor Amplifier Circuit using $h$ -Parameters <i>Problems Linked to LO 3</i> <i>Checkpoints</i>	9.25 9.26 9.27 9.29 9.32 9.35 9.37 9.41 9.44	11.1 The High-Frequency Transistor <b>11.1-11.28</b> <i>Learning Objectives</i> 11.1 The High-Frequency T-Model <i>Problems Linked to LO 1</i> <i>Checkpoints</i> 11.2 The Common-Base Short-Circuit-Current Frequency Response 11.3 The Alpha Cut-off Frequency 11.4 The Common-Emitter Short-Circuit-Current Frequency Response <i>Problems Linked to LO 2</i> <i>Checkpoints</i> 11.5 The Hybrid-pi (II) Common-Emitter Transistor Model 11.6 Hybrid-pi Conductances in Terms of Low-Frequency $h$ -Parameters <i>Problems Linked to LO 3</i> <i>Checkpoints</i> 11.7 The CE Short-Circuit Current Gain Obtained with the Hybrid-pi Model 11.8 Current Gain with Resistive Load 11.9 Transistor Amplifier Response, Taking Source Resistance into Account <i>Problems Linked to LO 4</i> <i>Checkpoints</i> <i>References</i> <i>Open-Book Exam Questions</i> <i>Multiple-Choice Questions</i>	11.1 11.1 11.3 11.3 11.4 11.5 11.5 11.8 11.8 11.10 11.10 11.11 11.16 11.17
<b>10. Low-Frequency Transistor Amplifier Circuits</b> <i>10.1-10.46</i> <i>Learning Objectives</i> 10.1 Cascading Transistor Amplifiers 10.2 $n$ -Stage Cascaded Amplifier 10.3 The Decibel <i>Problems Linked to LO 1</i> <i>Checkpoints</i>	10.1 10.1 10.5 10.8 10.9 10.11	<b>12. Field-Effect Transistors</b> <i>12.1-12.44</i> <i>Learning Objectives</i> 12.1 The Junction Field-Effect Transistor 12.2 The Pinch-Off Voltage $V_P$ 12.3 The JFET Volt-Ampere Characteristics 12.4 The FET Small-Signal Model <i>Problems Linked to LO 1</i> <i>Checkpoints</i> 12.5 The Insulated-Gate FET (MOSFET) <i>Checkpoints</i> 12.6 The Common-Source Amplifier 12.7 The Common-Drain Amplifier, or Source Follower	12.1 12.2 12.4 12.6 12.8 12.12 12.13 12.16 12.16 12.20
10.4 Simplified Common-Emitter Hybrid Model 10.5 Simplified Calculations for the Common-Collector Configuration 10.6 Simplified Calculations for the Common-Base Configuration <i>Problems Linked to LO 2</i> <i>Checkpoints</i>	10.12 10.17 10.20 10.20 10.21		
10.7 The Common-Emitter Amplifier with an Emitter Resistance 10.8 The Emitter Follower 10.9 Miller's Theorem 10.10 High-Input-Resistance Transistor Circuits <i>Problems Linked to LO 3</i> <i>Checkpoints</i>	10.21 10.25 10.28 10.29 10.35 10.37		

12.8	A Generalized FET Amplifier <i>Problems Linked to LO 3</i>	12.21	14.7	<i>Checkpoints</i>	14.12
	<i>Checkpoints</i>	12.27	14.8	Cascaded CE Transistor Stages	14.12
12.9	Biasing the FET <i>Problems Linked to LO 4</i>	12.30	14.9	Step Response of an Amplifier	14.17
	<i>Checkpoints</i>	12.30	14.10	Bandpass of Cascaded Stages	14.20
12.10	Unipolar-Bipolar Circuit Applications	12.35		Effect of an Emitter (or a Source) Bypass	
12.11	The FET as a Voltage-Variable Resistor (VVR)	12.37		Capacitor on Low-Frequency Response	14.22
12.12	The Unijunction Transistor	12.39	14.11	<i>Problems Linked to LO 3</i>	14.27
	<i>Checkpoints</i>	12.40		<i>Checkpoints</i>	14.28
	<i>References</i>	12.41		Noise	14.29
	<i>Open-Book Exam Questions</i>	12.41		<i>Problems Linked to LO 4</i>	14.32
	<i>Multiple-Choice Questions</i>	12.42		<i>Checkpoints</i>	14.33
		12.42		<i>References</i>	14.33
				<i>Open-Book Exam Questions</i>	14.34
				<i>Multiple-Choice Questions</i>	14.34
<b>13. Integrated Circuits</b>		<b>13.1-13.32</b>	<b>15. Feedback Amplifiers and Oscillators</b>		<b>15.1-15.82</b>
	<i>Learning Objectives</i>	13.1		<i>Learning Objectives</i>	15.1
13.1	Basic Monolithic Integrated Circuits	13.1	15.1	Classification of Amplifiers	15.1
	<i>Checkpoints</i>	13.5	15.2	The Feedback Concept	15.4
13.2	Epitaxial Growth	13.5		<i>Problems Linked to LO 1</i>	15.8
13.3	Masking and Etching	13.6		<i>Checkpoints</i>	15.9
13.4	Diffusion of Impurities	13.7	15.3	General Characteristics of Negative-Feedback Amplifiers	15.10
	<i>Problems Linked to LO 2</i>	13.11		<i>Problems Linked to LO 2</i>	15.12
	<i>Checkpoints</i>	13.12		<i>Checkpoints</i>	15.12
13.5	Transistors for Monolithic Circuits	13.12	15.4	Effect of Negative Feedback Upon Output and Input Resistances	15.13
13.6	Monolithic Diodes	13.15	15.5	Voltage-Series Feedback	15.14
13.7	Integrated Resistors	13.17	15.6	A Voltage-Series Feedback Pair	15.22
13.8	Integrated Capacitors and Inductors	13.19	15.7	Current-Series Feedback	15.24
	<i>Problems Linked to LO 3</i>	13.20	15.8	Current-Shunt Feedback	15.27
	<i>Checkpoints</i>	13.21	15.9	Voltage-Shunt Feedback	15.30
13.9	Monolithic Circuit Layout	13.21		<i>Problems Linked to LO 3</i>	15.33
13.10	Integrated Field-Effect Transistors	13.25		<i>Checkpoints</i>	15.37
13.11	Additional Isolation Methods	13.26	15.10	The Operational Amplifier	15.38
	<i>Problems Linked to LO 4</i>	13.28	15.11	Basic Characteristics of Practical Operational Amplifiers	15.45
	<i>Checkpoints</i>	13.29	15.12	Basic Applications of Operational Amplifier	15.48
	<i>References</i>	13.29	15.13	Electronic Analog Computation	15.56
	<i>Open-Book Exam Questions</i>	13.30		<i>Problems Linked to LO 4</i>	15.57
	<i>Multiple-Choice Questions</i>	13.30		<i>Checkpoints</i>	15.60
<b>14. Untuned Amplifiers</b>		<b>14.1-14.36</b>	15.14	Feedback And Stability	15.60
	<i>Learning Objectives</i>	14.1	15.15	Gain and Phase Margins	15.62
14.1	Classification of Amplifiers	14.2		<i>Problems Linked to LO 5</i>	15.63
14.2	Distortion in Amplifiers	14.2		<i>Checkpoints</i>	15.64
	<i>Problems Linked to LO 1</i>	14.3	15.16	Sinusoidal Oscillators	15.64
	<i>Checkpoints</i>	14.3	15.17	The Phase-Shift Oscillator	15.66
14.3	Frequency Response of an Amplifier	14.4	15.18	Resonant-Circuit Oscillators	15.69
14.4	The RC-Coupled Amplifier	14.6	15.19	A General Form of Oscillator Circuit	15.70
14.5	Low-Frequency Response of an RC-Coupled Stage	14.6			
14.6	High-Frequency Response of a FET Stage	14.10			
	<i>Problems Linked to LO 2</i>	14.11			

15.20 Crystal Oscillators	15.72	Checkpoints	17.23
15.21 Frequency Stability	15.74	17.11 The <i>p-i-n</i> Photodetector	17.24
15.22 Negative Resistance in Oscillators	15.75	17.12 The Avalanche Photodiode (APD)	17.29
<i>Problems Linked to LO 6</i>	15.76	<i>Problems Linked to LO 5</i>	17.34
<i>Checkpoints</i>	15.79	<i>Checkpoints</i>	17.35
<i>References</i>	15.80	<i>References</i>	17.36
<i>Open-Book Exam Questions</i>	15.80	<i>Open-Book Exam Questions</i>	17.36
<i>Multiple-Choice Questions</i>		<i>Multiple-Choice Questions</i>	17.36
<b>16. Large-Signal Amplifiers</b>	<b>16.1-16.30</b>	<b>18. Regulated Power Supplies</b>	<b>18.1-18.22</b>
<i>Learning Objectives</i>	16.1	<i>Learning Objectives</i>	18.1
16.1 Class A Large-Signal Amplifiers	16.2	18.1 Elements of a Regulated Power Supply	18.2
16.2 Second-Harmonic Distortion	16.3	System	18.3
16.3 Higher-Order Harmonic Generation	16.5	18.2 Stabilization	18.3
<i>Problems Linked to LO 1</i>	16.8	<i>Checkpoints</i>	18.4
<i>Checkpoints</i>	16.8	18.3 Emitter-follower Regulator	18.4
16.4 The Transformer-Coupled Audio Power	16.9	18.4 Series Voltage Regulation	18.8
Amplifier	16.13	18.5 Practical Considerations	18.9
16.5 Shift of Dynamic Load Line	16.13	<i>Problems Linked to LO 2</i>	18.10
16.6 Efficiency	16.19	<i>Checkpoints</i>	18.11
<i>Problems Linked to LO 2</i>	16.20	Monolithic Linear Regulators	18.14
<i>Checkpoints</i>	16.21	Performance Parameters of 3-Terminal	
16.7 Push-Pull Amplifiers	16.22	IC Regulators	
16.8 Class B Amplifiers	16.26	18.8 LM723/LM723C General Purpose	18.15
16.9 Class AB Operation	16.26	Voltage Regulator	18.17
<i>Problems Linked to LO 3</i>	16.27	18.9 Shunt Voltage Regulators	18.19
<i>Checkpoints</i>	16.28	<i>Problems Linked to LO 3</i>	18.20
<i>References</i>	16.28	<i>Checkpoints</i>	18.20
<i>Open-Book Exam Questions</i>	16.28	<i>References</i>	18.21
<i>Multiple-Choice Questions</i>		<i>Open-Book Exam Questions</i>	18.21
<b>17. Photoelectric Devices</b>	<b>17.1-17.38</b>	<i>Multiple-Choice Questions</i>	18.21
<i>Learning Objectives</i>	17.1	<b>Appendix A: Probable Values of General Physical Constants</b>	A.1
17.1 Photoemissivity	17.2	<b>Appendix B: Conversion Factors and Prefixes</b>	A.2
17.2 Photoelectric Theory	17.3	<b>Appendix C: Periodic Table of the Elements</b>	A.3
17.3 Definitions of Some Radiation Terms	17.6	<b>Appendix D: Data Sheets of General Purpose Transistors 2N3903/3904</b>	A.4
<i>Problems Linked to LO 1</i>	17.7	<b>Appendix E: Data Sheets of Some Commonly Used Voltage ICs</b>	A.11
<i>Checkpoints</i>	17.7	<b>Appendix F: Answers to Selected Open-Book Exam Questions</b>	A.22
17.4 Phototubes	17.8		I.1
17.5 Applications of Photodevices	17.10		
17.6 Multiplier Phototubes	17.11		
<i>Problems Linked to LO 2</i>	17.13		
<i>Checkpoints</i>	17.14		
17.7 Photoconductivity	17.16		
17.8 The Semiconductor Photodiode	17.19		
17.9 Multiple-Junction Photodiodes	17.20		
<i>Problems Linked to LO 3</i>	17.20		
<i>Checkpoints</i>	17.21		
17.10 The Photovoltaic Effect	17.23	<b>Index</b>	
<i>Problems Linked to LO 4</i>			